




Digital Circuits and Systems

Lecture 4 Modeling Combinational Logic

Tian Sheuan Chang

SYSTEM VIEW


A12

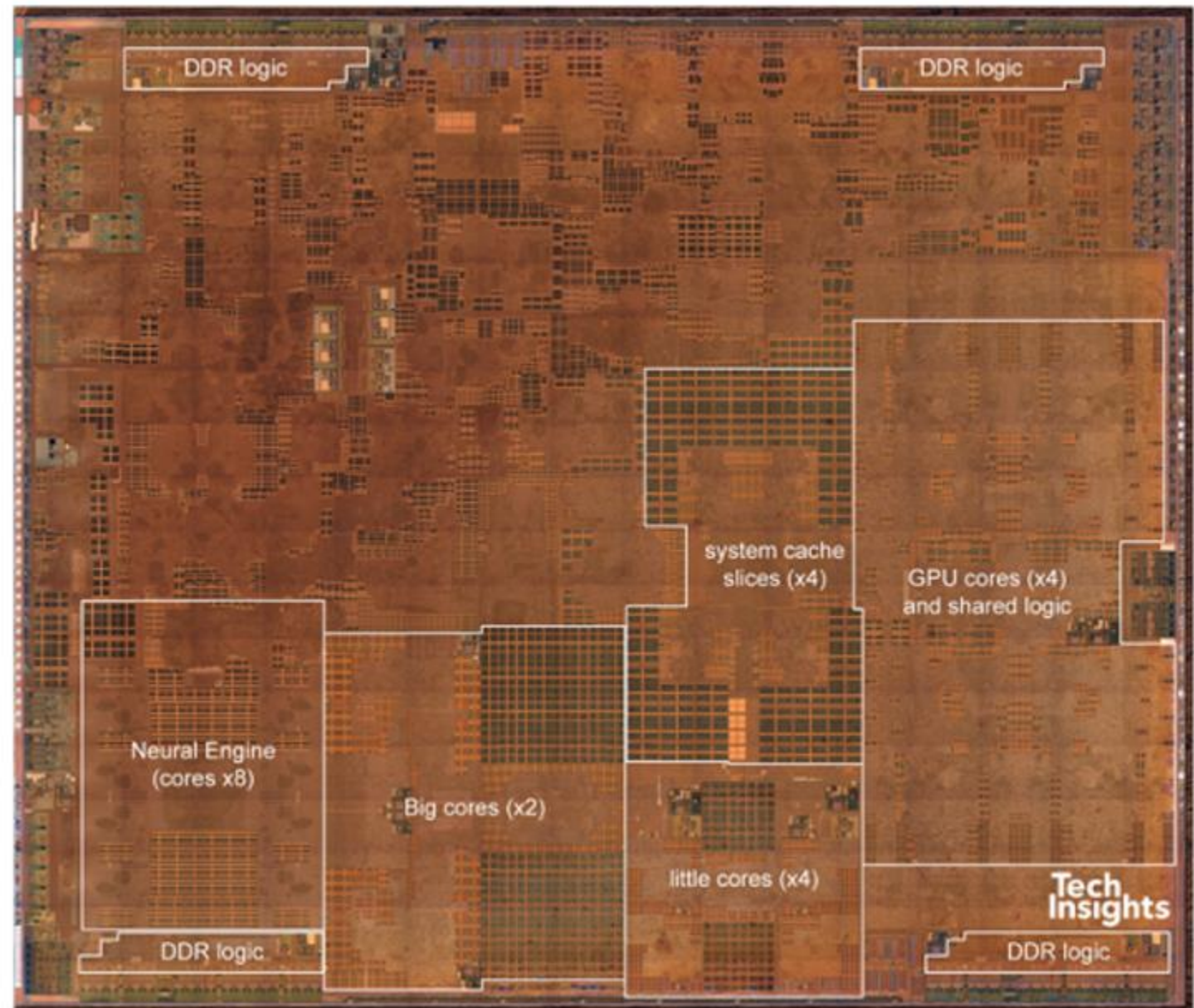

https://www.phonearena.com/news/Apples-A12-chip-packed-with-70-percent-more-transistors_id109291


<https://www.loveios.net/2018/08/tsmc-virus-attack-may-affect-a12-production.html>

Mapping Onto System-on-Chip (SoC)

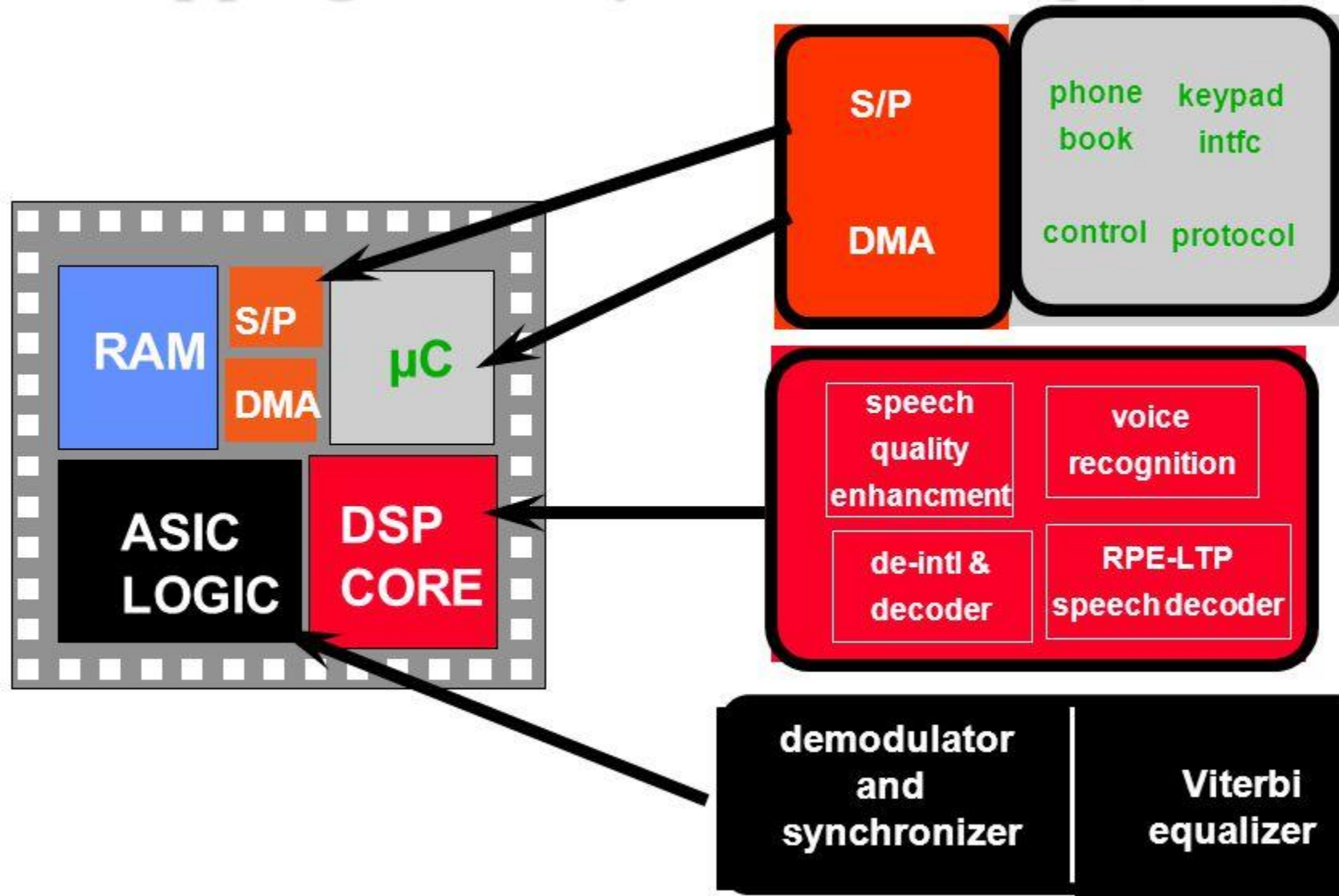


System on a Chip (SOC)

Source: ARM

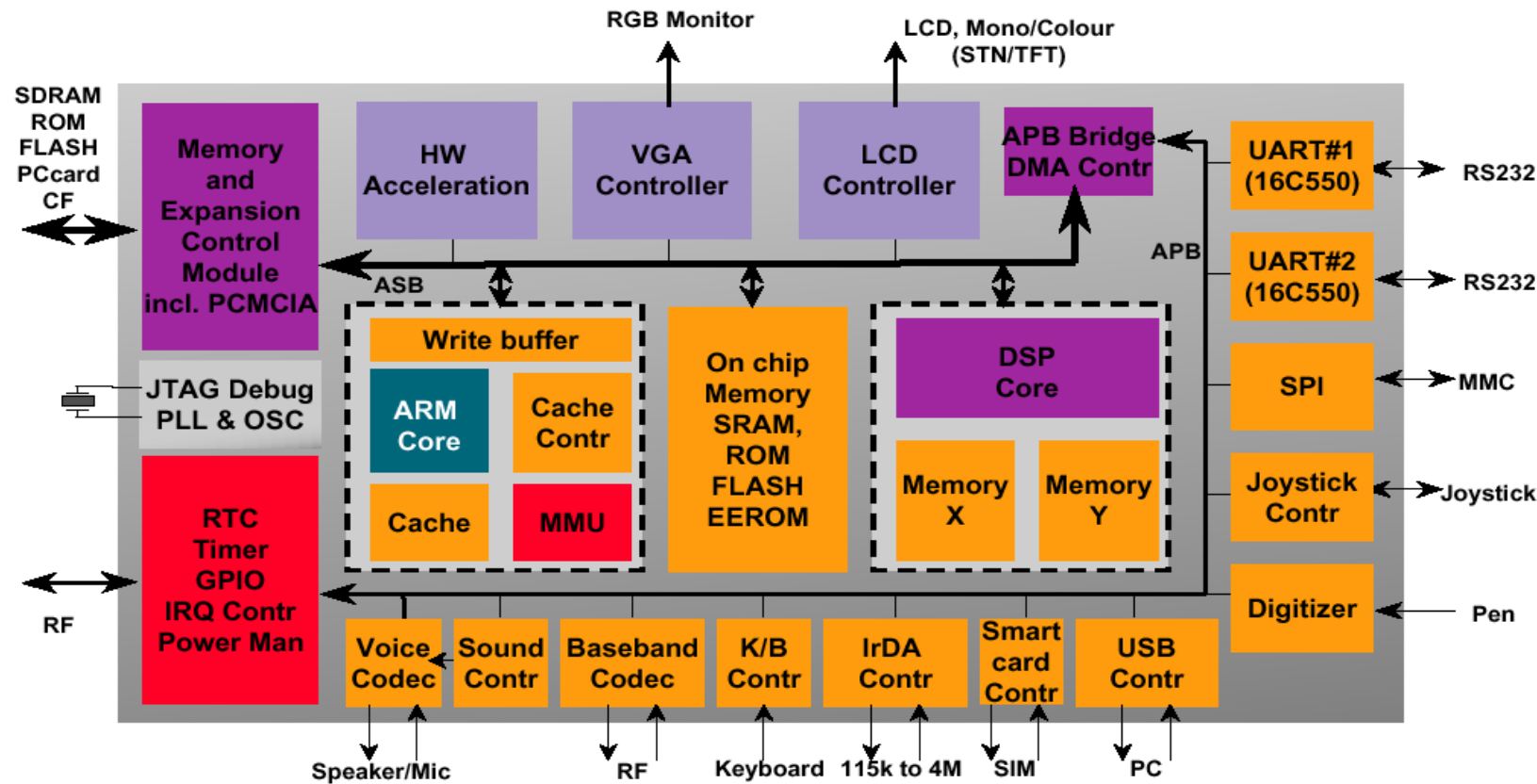


PYNQ

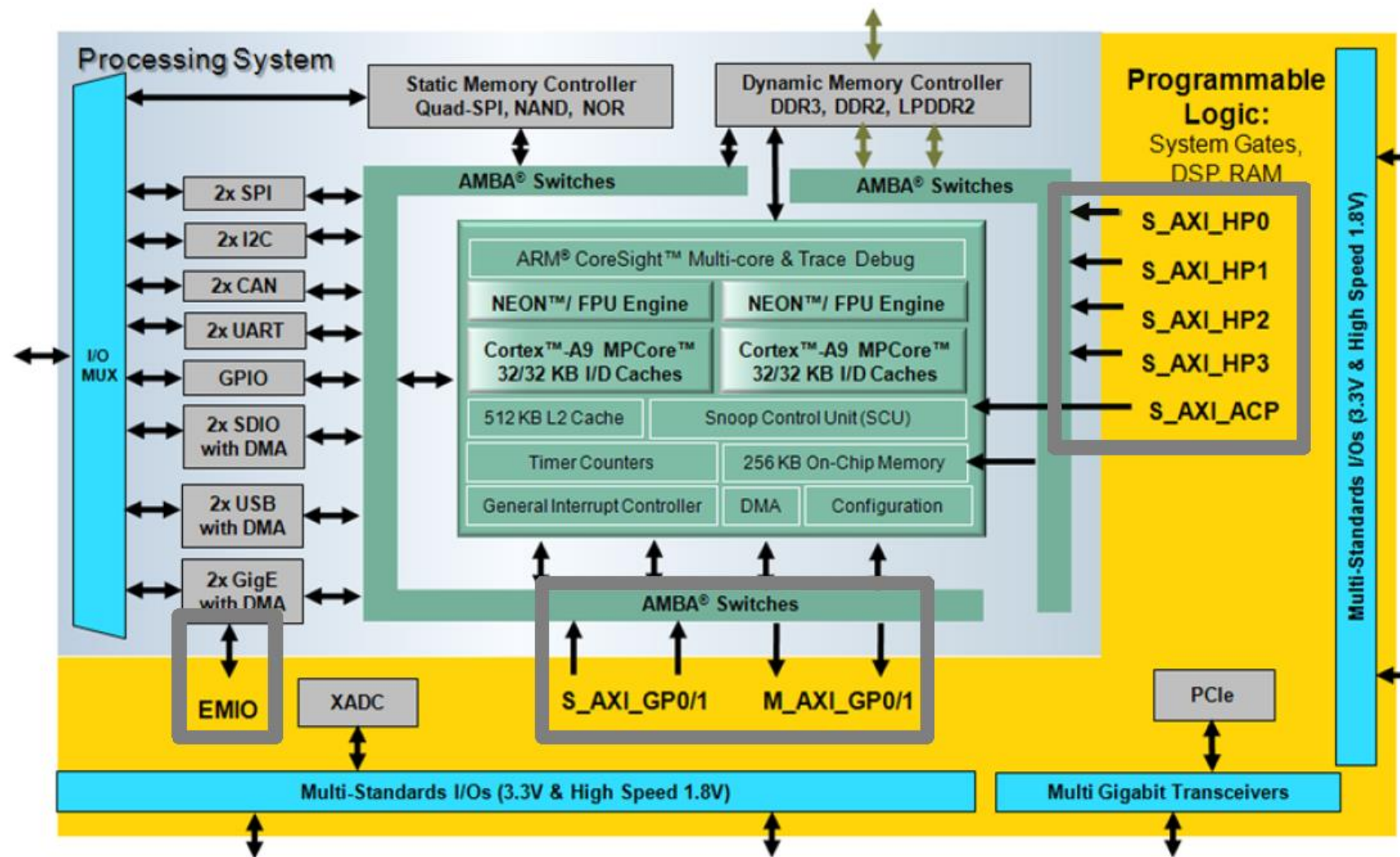

Breakdown of Modern SOC Design

- Core
 - CPU/DSPs/GPUs
 - Hardware accelerators (AI engine/video codec/MP3 codec)
 - Complex data path + FSMs (pipeline/parallel)
- Bus
 - Connect core and peripherals
 - MUX/arbiters
- Peripheral
 - Interface from/to the external
 - speech/audio, camera/display, I2S/I2C, GPIO
 - Serial to parallel, parallel to serial + FSM

An Example AMBA System

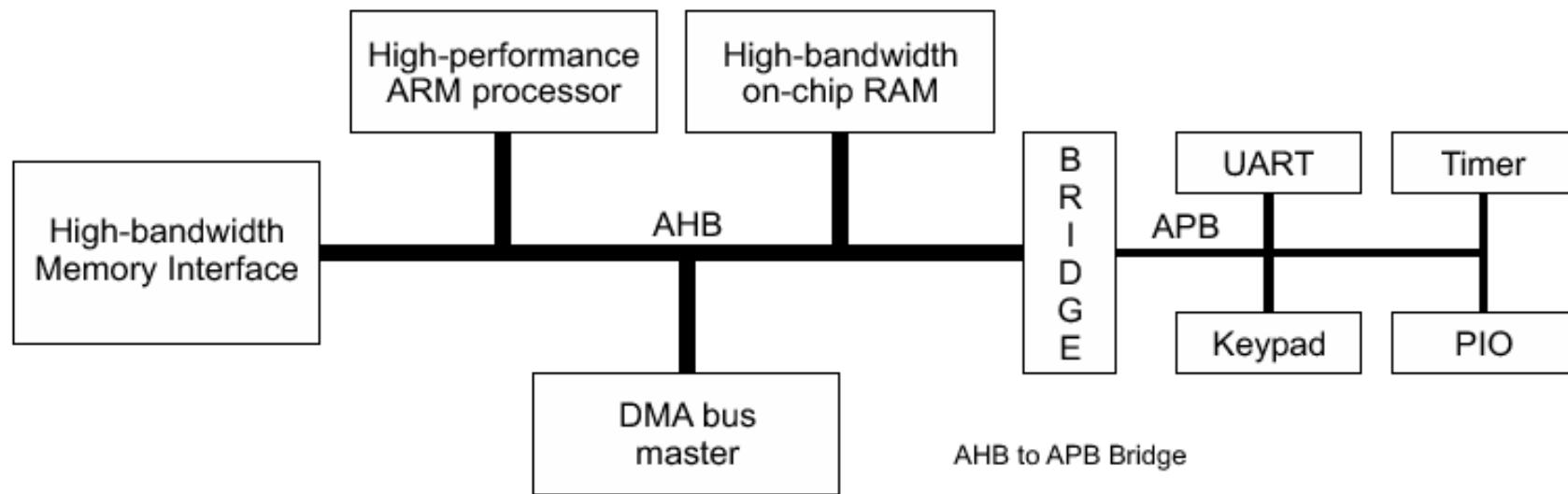

AMBA Advanced High-performance Bus (AHB)


- * High performance
- * Pipelined operation
- * Burst transfers
- * Multiple bus masters
- * Split transactions

AMBA Advanced Peripheral Bus (APB)

- * Low power
- * Latched address and control
- * Simple interface
- * Suitable for many peripherals


From C Array to Memory Access

Memory [125] = 0

 

Memory Write Operation



CPU = Memory [125]

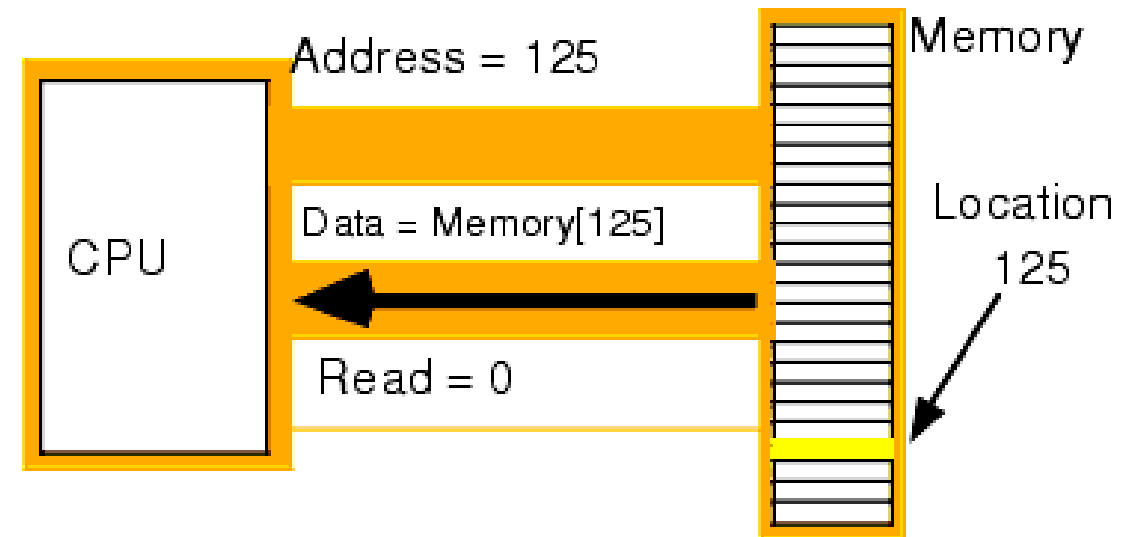

Memory Read Operation

How CPU access these I/O interface?

 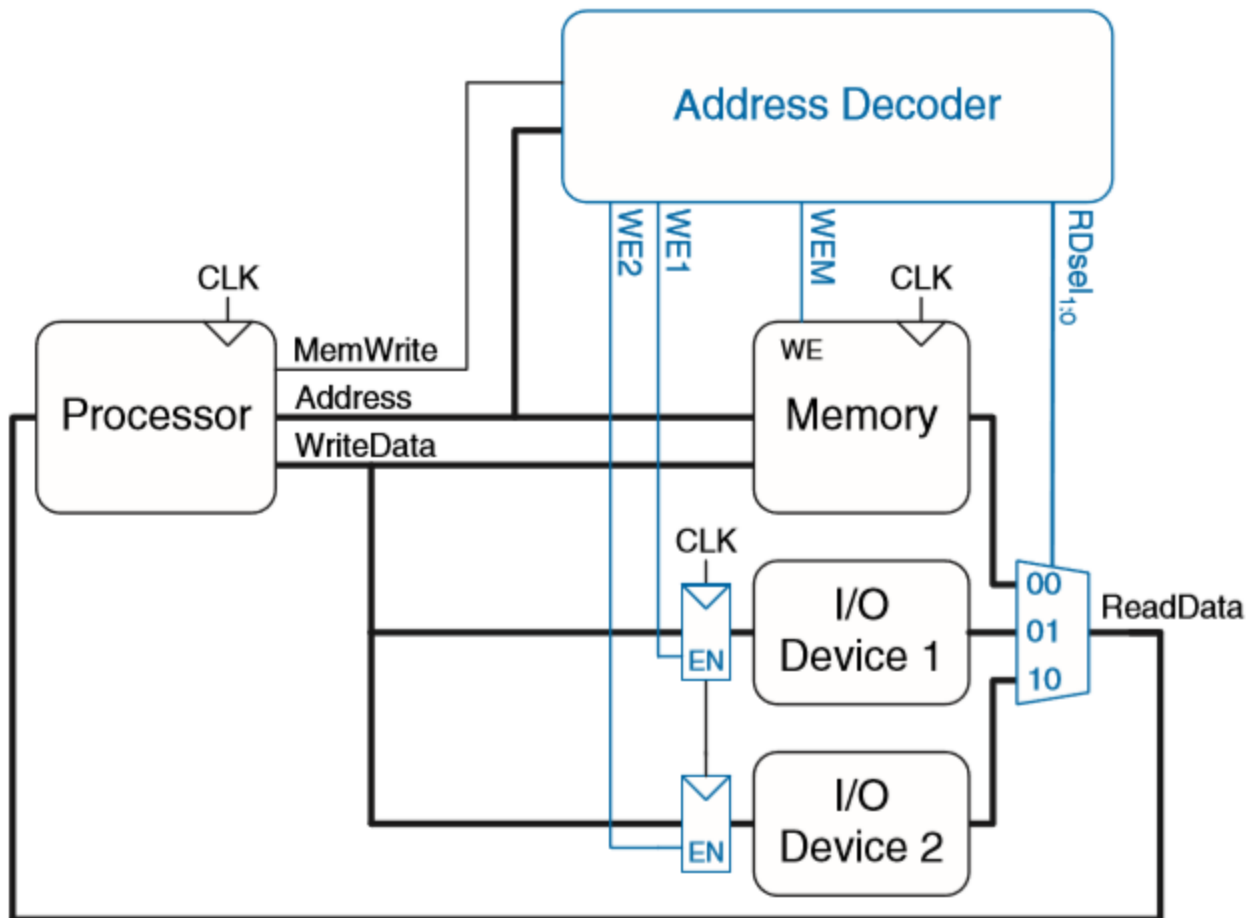- Memory mapped I/O (treat other components as memory)





Example: USB sub system memory map in Beagle board


- I/O與memory共用記憶體空間，不用特別的指令來存取I/O，以記憶體讀寫的方式來進行I/O port的存取，在本文中使用的ARM的核心，TI AM335X，便提供這種方式來進行I/O port的存取。

Block Name	Start_address (hex)	End_address (hex)	Size	Description
USBSS	0x4740_0000	0x4740_0FFF	20KB	USB Subsystem Registers
USB0	0x4740_1000	0x4740_12FF		USB0 Controller Registers
USB0_PHY	0x4740_1300	0x4740_13FF		USB0 PHY Registers
USB0 Core	0x4740_1400	0x4740_17FF		USB0 Core Registers
USB1	0x4740_1800	0x4740_1AFF		USB1 Controller Registers
USB1_PHY	0x4740_1B00	0x4740_1BFF		USB1 PHY Registers
USB1 Core	0x4740_1C00	0x4740_1FFF		USB1 Core Registers
USB CPPI DMA Controller	0x4740_2000	0x4740_2FFF		USB CPPI DMA Controller Registers
USB CPPI DMA Scheduler	0x4740_3000	0x4740_3FFF		USB CPPI DMA Scheduler Registers
USB Queue Manager	0x4740_4000	0x4740_4FFF		USB Queue Manager Registers

AHB-Lite

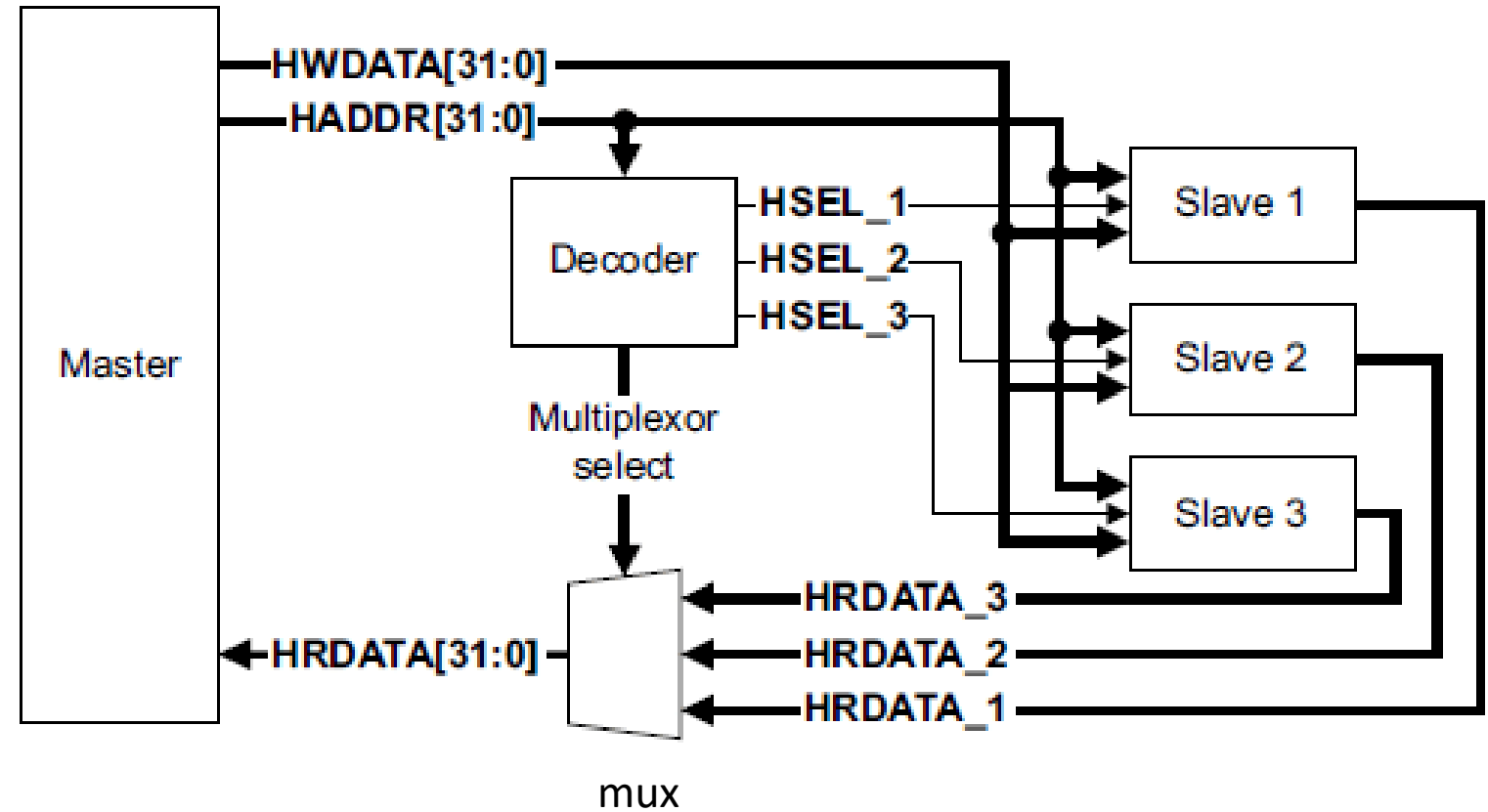 

AHB Interconnect

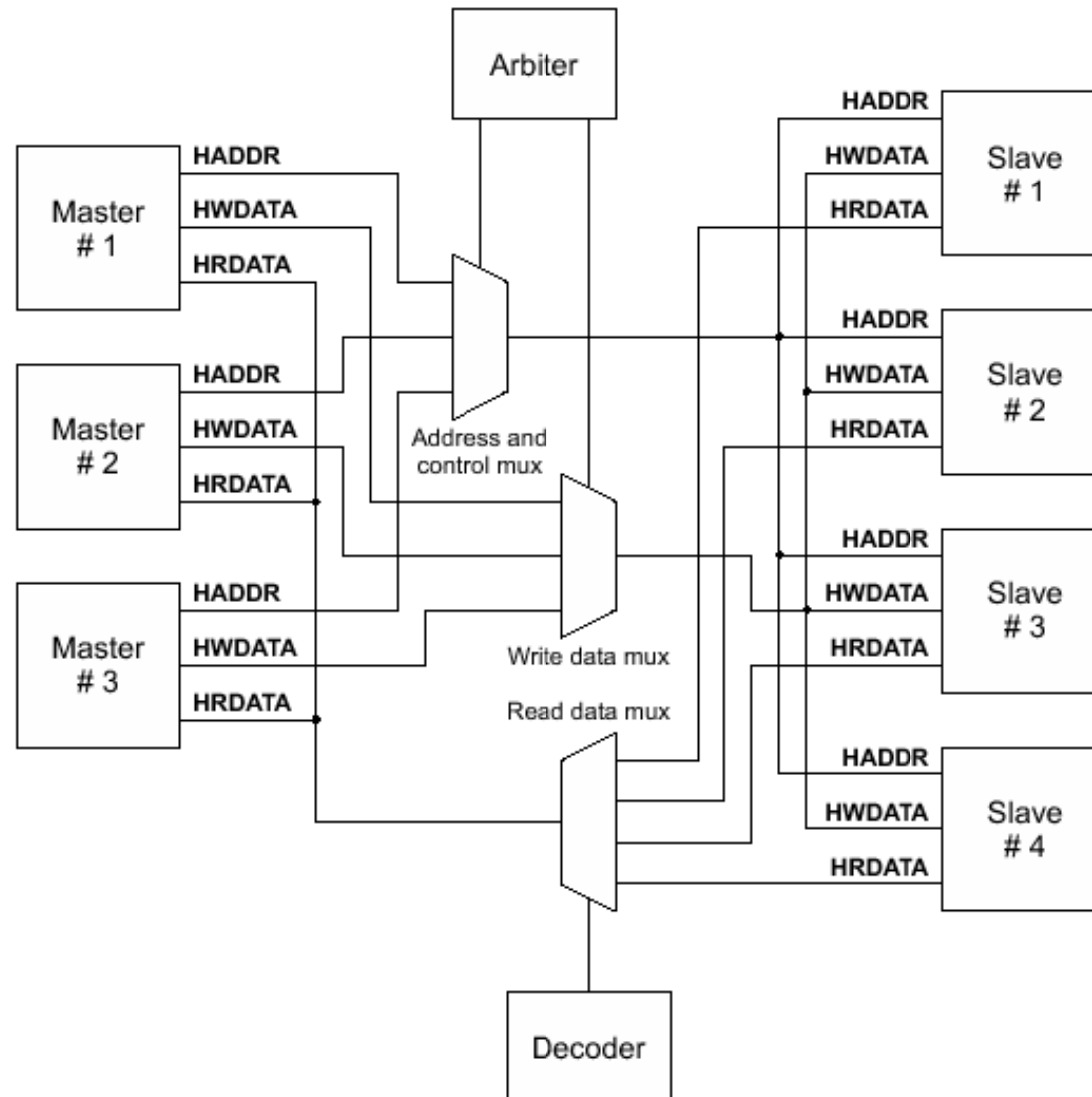

Basic components:

- Master
- Slave
- Arbiter
- Decoder
- Mux

Outline

- From K-Map to Verilog [Dally 7.1]
- Combinational building blocks – the idioms of digital design [Dally 8]
 - Decoder (binary to one-hot)
 - Encoder (one-hot to binary)
 - Multiplexer (select one of N)
 - Arbiter (pick first of N, 找第一個1) and priority encoder
 - Comparators
 - Read-only memories (ROM) / random access memory (RAM)

學習重點

- 知道如何對應基本硬體與Verilog code
 - 寫法很多種，哪一個比較好？
 - Verilog語法的差別
- 從2-bit 到 16bit 怎麼設計？怎麼寫？
 - Iterative circuit
 - Behavior level Verilog

FROM K-MAP TO VERILOG

從手動化簡到自動化電路

CASE/CASEZ/CASEX


Prime Number Detection

- $F(d,c,b,a)$ is true if input d,c,b,a is prime




$$f = \sum_{dcba} m(1,2,3,5,7,11,13)$$

No	dcba	q
0	0000	0
1	0001	1
2	0010	1
3	0011	1
4	0100	0
5	0101	1
6	0110	0
7	0111	1
8	1000	0
9	1001	0
10	1010	0
11	1011	1
12	1100	0
13	1101	1
14	1110	0
15	1111	0


Schematic Logic Diagram:

 

Karnaugh Map of 4-bit Prime Number

   

NAND for CMOS

 

更進一步化簡 Decimal Prime: includes don't cares

$$f = \sum_{dcba} m(1,2,3,5,7) + D(10,11,12,13,14,15)$$

ba		a			
		00	01	11	10
dc	00	0	1	1	1
	01	0	1	1	0
c	11	x	x	x	x
	10	0	0	x	x
		b			
		00	01	11	10




ba		a			
		00	01	11	10
dc	00	0	1	1	1
	01	0	1	1	0
c	11	x	x	x	x
	10	0	0	x	x
		b			
		00	01	11	10

Annotations: 0XX1 (points to row 00), XX11 (points to column 11), X1X1 (points to row 10), X01X (points to column 01).

Cover:
0XX1
X01X
 
$$f = (a \wedge \bar{d}) \vee (b \wedge \bar{c})$$



4-bit Prime Number Function in Verilog Code – Using **case**

```
module prime(in, isprime) ;  
    input [3:0] in ;           // 4-bit input  
    output      isprime ;      // true if input is prime  
    logic       isprime ;  
  
    always_comb begin  
        case(in)  
            1,2,3,5,7,11,13: isprime = 1'b1 ;  
            default:         isprime = 1'b0 ;  
        endcase  
    end  
endmodule
```

$$f = \sum_{dcba} m(1,2,3,5,7,11,13)$$

You can have a simplified Verilog coding if with don't care input
這很好，可是若有DON'T CARE INPUT，寫法可以更化簡

4-bit Prime Number Function in Verilog Code – Using **casez**

```

module prime1(in, isprime) ;
  input [3:0] in ;           // 4-bit input
  output      isprime ;      // true if input is prime
  logic       isprime ;

```

```

always_comb begin

```

```

  casez (in)

```

```

    4'b0??1: isprime = 1 ;

```

```

    4'b001?: isprime = 1 ;

```

```

    4'b?011: isprime = 1 ;

```

```

    4'b?101: isprime = 1 ;

```

```

    default: isprime = 0 ;

```

```

  endcase

```

```

end


```

```

endmodule

```

dcba
0xx1
001x
x101
x011

 

	case	casez	casex
比對的值	0, 1, Z, X	0, 1, X	0, 1
當作do't care		Z	X, Z
電路合成	0, 1	0, 1	0, 1

X: unknown, Z: high impedance, ?: Z

當輸入有X，以下電路會全部X

使用**casez** 利用到DON'T CARE INPUT，
但避免X propagation，造成
Simulation-synthesis mismatch

http://www.sunburst-design.com/papers/CummingsSNUG1999SJ_SynthMismatch.pdf

<http://www.cnblogs.com/poiu-elab/archive/2012/11/02/2751323.html>

Priority encoder

4-bit Prime Number Function in Verilog Code – Using **assign**

```
module prime(in, isprime) ;  
    input [3:0] in ;           // 4-bit input  
    output      isprime ;      // true if input is prime  
  
    wire isprime = (in[0] & ~in[3]) |  
                   (in[1] & ~in[2] & ~in[3]) |  
                   (in[0] & ~in[1] & in[2]) |  
                   (in[0] & in[1] & ~in[2]) ;  
  
endmodule
```

簡單的化簡就留給**EDA tools** 做

複雜的架構才值得花時間


**You don't need to simplify logic
by yourself, Left this to EDA
tools**

4-bit Prime Number Function in Verilog Code – Result of synthesizing description using case

```

module prime ( in, isprime );
input  [3:0] in;
output isprime;
    wire n1, n2, n3, n4;
    OAI13 U1 ( .A1(n2), .B1(n1), .B2(in[2]), .B3(in[3]), .Y(isprime) );
    INV U2 ( .A(in[1]), .Y(n1) );
    INV U3 ( .A(in[3]), .Y(n3) );
    XOR2 U4 ( .A(in[2]), .B(in[1]), .Y(n4) );
    OAI12 U5 ( .A1(in[0]), .B1(n3), .B2(n4), .Y(n2) );
endmodule

```

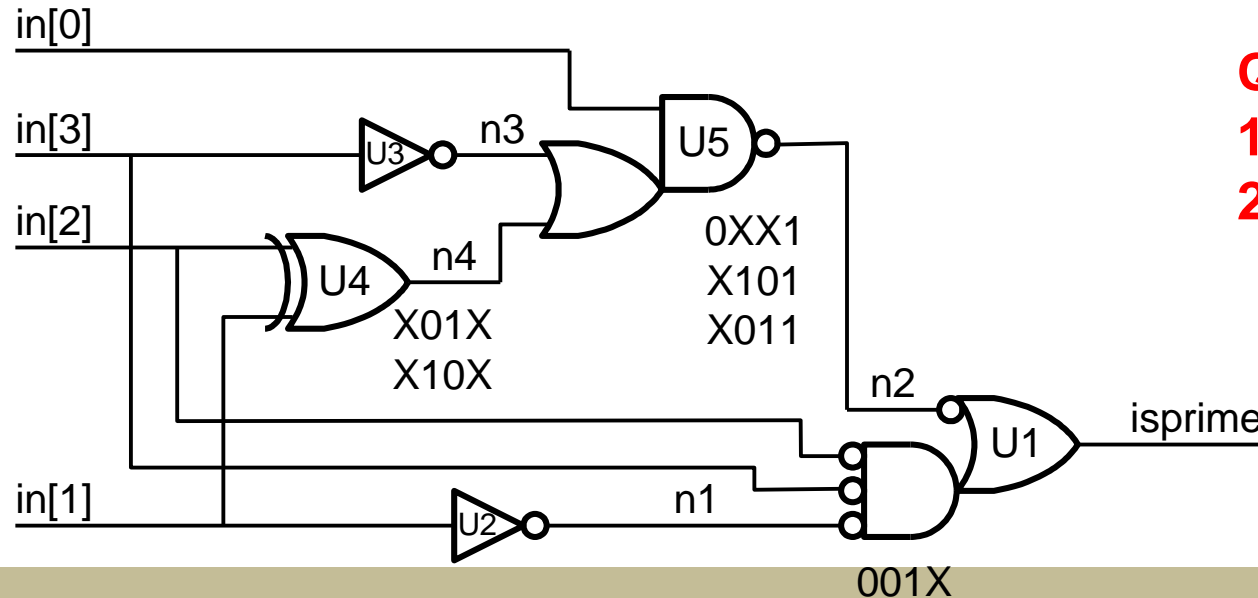

Quiz:

- 1) Where are these gates?
- 2) Identify the critical path?

Synthesis Reports

```
*****
Report : area
Design : prime
Version: 2003.06
Date   : Sat Oct  4 11:38:08 2003
*****

Library(s) Used:

XXXXX

Number of ports:      5
Number of nets:      9
Number of cells:      5
Number of references: 4

Combinational area:   7.000000
Noncombinational area: 0.000000
Net Interconnect area: undefined (Wire load has zero
                             net area)

Total cell area:      7.000000
Total area:           undefined
```

Left part: area report
 Right part: timing report

```
*****
Report : timing
        -path full
        -delay max
        -max_paths 1
Design : prime
Version: 2003.06
Date   : Sat Oct  4 11:38:08 2003
*****

Operating Conditions:
Wire Load Model Mode: enclosed

Startpoint: in[2] (input port)
Endpoint: isprime (output port)
Path Group: (none)
Path Type: max

Des/Clust/Port      Wire Load Model      Library
-----
prime              2K_5LM                XXXXX

Point              Incr              Path
-----
-
input external delay      0.000      0.000 r
in[2] (in)                0.000      0.000 r
U4/Y (EX210)              0.191      0.191 f
U5/Y (BF051)              0.116      0.307 r
U1/Y (BF052)              0.168      0.475 f
isprime (out)             0.000      0.475 f
data arrival time                0.475
-----
-
(Path is unconstrained)
```

Constraint File

```
//設定clock, I/O 限制  
create_clock "clk" -name clk -period 2 -waveform {0 1.7}  
set_clock_uncertainty 0.2 clk  
set_fix_hold all_clocks()  
set_input_delay 0.5 -clock clk {in}  
set_output_delay -max 0.8 -clock clk {isprime}  
//設定 loading  
set_load -pin_load 5 {isprime}
```

**//Note: these commands are for practical applications to include
// clock jitter, input/output loading capacitances**

Test bench

```
module test_prime ;  
    reg [3:0] in ;  
    wire isprime ;  
  
    // instantiate module to test  
    prime p0(in, isprime) ;  
  
    initial begin  
        in = 0 ;  
        repeat (16) begin  
            #100  
            $display("in = %2d isprime = %1b",in,isprime) ;  
            in = in+1 ;  
        end  
    end  
endmodule
```


**//this test module is included to
//simulate the behavior of your
//Verilog-HDL description
//Note: very often input data
//will be limited**

**Quiz: Why “divide-and-conquer”
Is often exploited in DCS design?**

```

# in = 0 isprime = 0
# in = 1 isprime = 1
# in = 2 isprime = 1
# in = 3 isprime = 1
# in = 4 isprime = 0
# in = 5 isprime = 1
# in = 6 isprime = 0
# in = 7 isprime = 1
# in = 8 isprime = 0
# in = 9 isprime = 0
# in = 10 isprime = 0
# in = 11 isprime = 1
# in = 12 isprime = 0
# in = 13 isprime = 1
# in = 14 isprime = 0
# in = 15 isprime = 0


```

 

0 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15

Summary

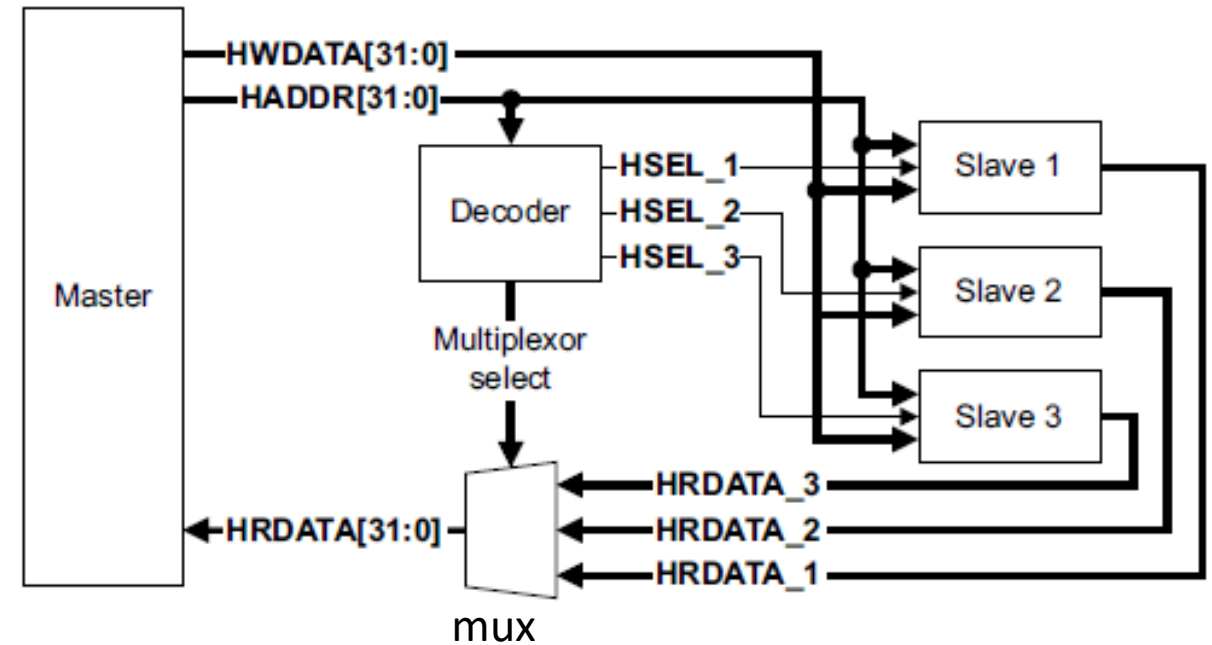- K-Map helps you understand how logic synthesizer works
 - But no need to do it by yourself
 - Synthesis tool will do the optimization
- Use case
- Or **casez** if you have don't care input



DECODER AND ENCODER (BINARY <-> ONE HOT)

Binary to One-Hot Representation (Decoder)


Binary	One-hot
000	00000001
001	00000010
010	00000100
...	...
110	01000000
111	10000000

常用於記憶體のaddress decoder
Used in address decoder for memory

Binary input a to one-hot output b

$$b[i] = 1 \text{ if } a = i$$

$$b = 1 \ll a$$

 

***can be found in source and communication systems**

Verilog implementation of a decoder

```
// a - binary input    (n bits wide)
// b - one hot output  (m bits wide)
```


```
module dec(a, b) ;
  parameter n=2 ;
  parameter m=4 ;
```

```
  input  [n-1:0] a ;
  output [m-1:0] b ;
```

```
  wire [m-1:0] b;
```

```
  assign b = 1<<a ;
endmodule
```

**//this is a parameterized design
//you need to assign parameters
//when exploited.**

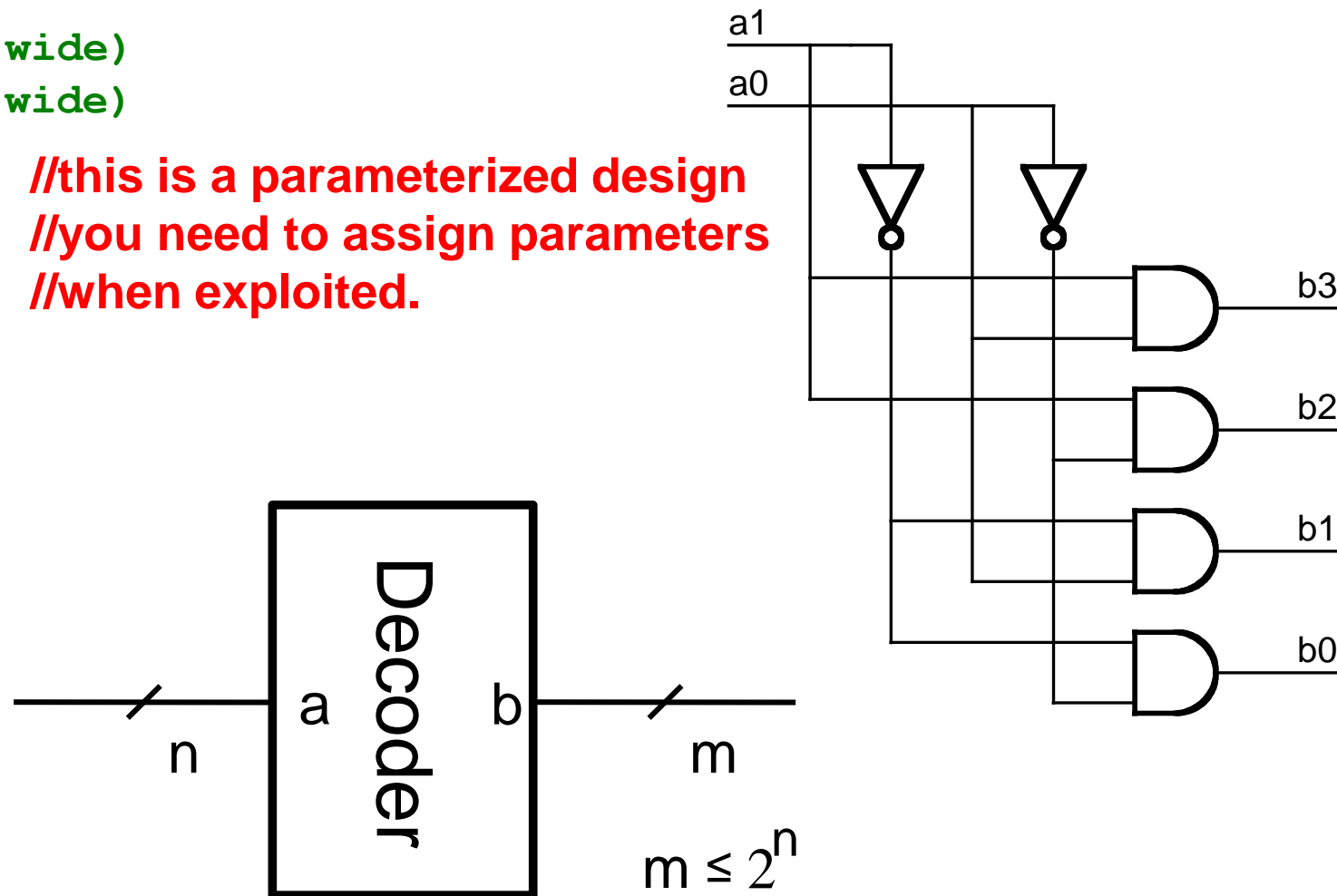


From 2->4 decoder to 6->64 Decoder

大的Decoder 如何又快又省

- **Need hierarchical design 階層式設計**
- 6->64 decoder requires:
 - 64 6-input AND gates (384 inputs)
- 6->64 decoder using 2->4 decoders requires:
 - 12 2-input AND gates (24 inputs)
 - 64 3-input AND gates (192 inputs)
- **Faster, smaller, lower power performances can be achieved.**


2-Stage decoders – the picture

 

Encoder

a 4 -> 2 encoder


a3	a2	a1	a0	b1	b0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

那大的Encoder呢? E.g. 16-> 4

16- \rightarrow 4 Encoder

One hot

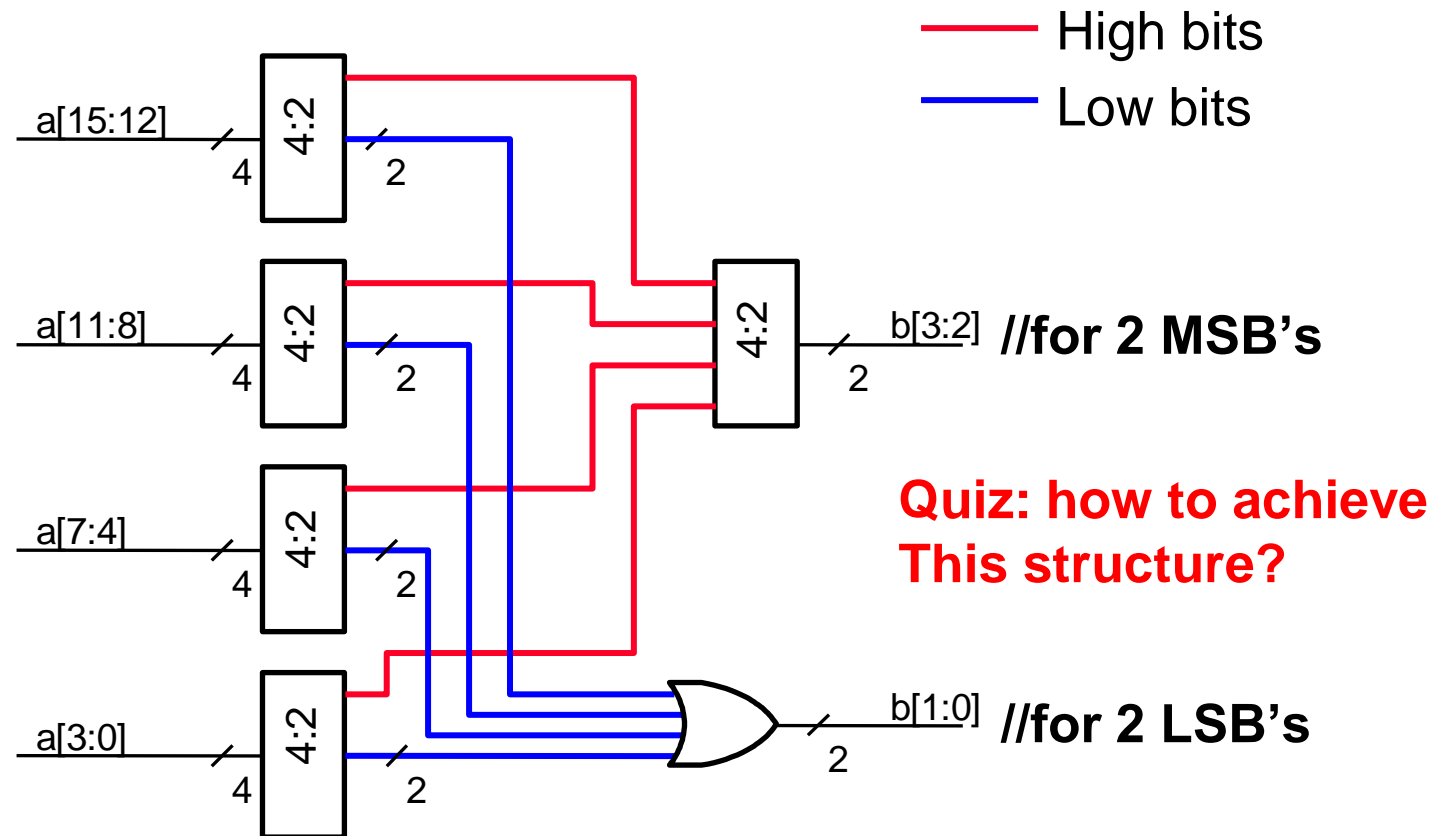

Two writing styles 兩種寫法

```
// encoder - fixed width
module Enc42a(a, b) ;
    input  [3:0] a ;
    output [1:0] b ;
    wire   [1:0] b ;

    assign b[1] = a[3] | a[2] ;
    assign b[0] = a[3] | a[1] ;
endmodule
```

More like schematic

```
// encoder - fixed width
module Enc42a(a, b) ;
    input  [3:0] a ;
    output [1:0] b ;
    wire   [1:0] b ;

    always_comb begin
        case (a)
            4'b0001: b = 2'd0;
            4'b0010: b = 2'd1;
            4'b0100: b = 2'd2;
            4'b1000: b = 2'd3;
            4'b0000: b = 2'd0; // to facilitate large encoder
            default: b = 2'dxx;
        endcase
    end
endmodule
```

To avoid simulation and synthesis mismatch,
Set default value to one of the options. E.g. b = 2'd0;

Behavior level

Vote

Binary Encoder

- Input is 1-hot


```
// Simple binary encoder (input is 1-hot)
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg     [2:0] Y;          // target of assignment

always @(A)
  case (A)
    8'b00000001: Y = 0;
    8'b00000010: Y = 1;
    8'b00000100: Y = 2;
    8'b00001000: Y = 3;
    8'b00010000: Y = 4;
    8'b00100000: Y = 5;
    8'b01000000: Y = 6;
    8'b10000000: Y = 7;
    default:      Y = 3'bXXX; // Don't care when input is not 1-hot
  endcase
endmodule
```

- Cases are executed sequentially

```
// Priority encoder
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg      [2:0] Y;         // target of assignment

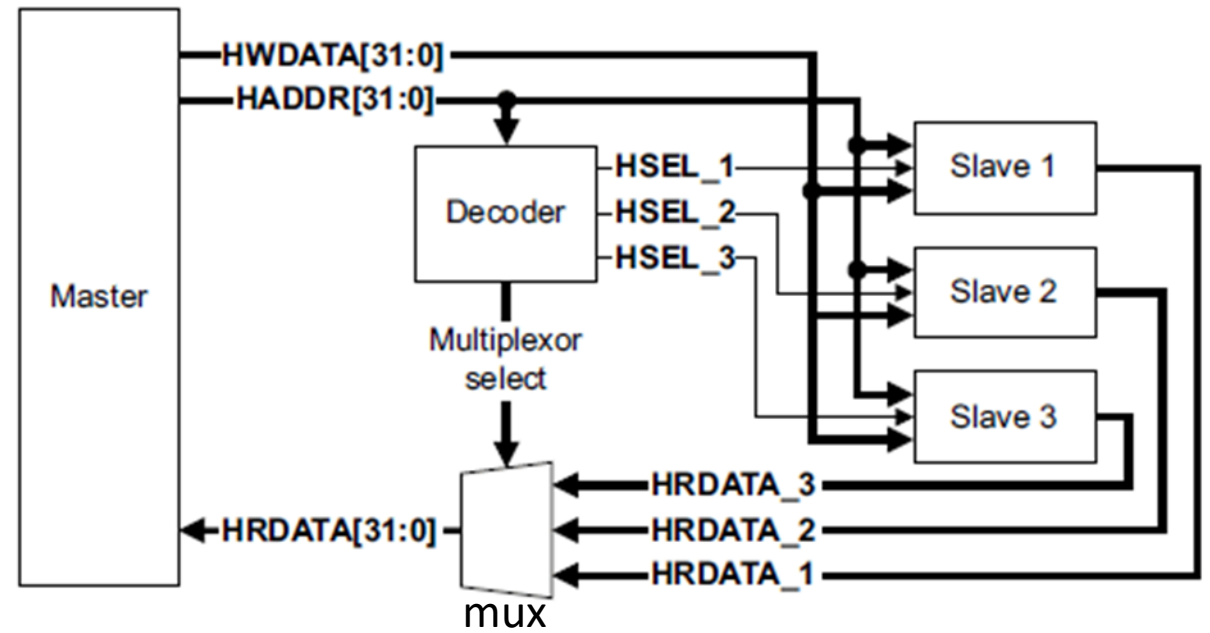always @(A)
  case (1'b1)
    A[0]: Y = 0;
    A[1]: Y = 1;
    A[2]: Y = 2;
    A[3]: Y = 3;
    A[4]: Y = 4;
    A[5]: Y = 5;
    A[6]: Y = 6;
    A[7]: Y = 7;
    default: Y = 3'bXXX; // Don't care when input is all 0's
  endcase
endmodule
```



MULTIPLEXER


Multiplexer (one-hot selection signals)

- Multiplexer:
 - n k -bit inputs
 - n -bit one-hot select signal s
 - Multiplexers are commonly used as *data selectors*

Selects one of n k -bit inputs


s must be one-hot

$b = a[i]$ if $s[i] = 1$

 


兩種架構，哪個好？

AND-OR structure

 

Tri-state structure

 

Quiz: What's the difference between these two implementations?

MUX4 v.s. MUX3

```
Mux4(a3, a2, a1, a0, s, b) ;
parameter k = 1 ;
input [k-1:0] a0, a1, a2, a3 ;
input [3:0] s ; // one-hot select
output[k-1:0] b ;
wire [k-1:0] b = ({k{s[0]}} & a0) |
                  ({k{s[1]}} & a1) |
                  ({k{s[2]}} & a2) |
                  ({k{s[3]}} & a3) ;
endmodule
```

More like schematic



```
module mux3a(a2, a1, a0, s, b) ;
parameter k = 1 ;
input [k-1:0] a0, a1, a2 ; // inputs
input [2:0] s ; // one-hot select
output[k-1:0] b ;
logic [k-1:0] b ;

always_comb begin
    case(s)
        3'b001: b = a0 ;
        3'b010: b = a1 ;
        3'b100: b = a2 ;
        default: b = {k{1'bX}} ; //don't care "X"
    endcase
end
endmodule
```

Behavior level

Vote

Binary Select MUX

  


兩種寫法

```
// 3:1 multiplexer with binary select (arbitrary width)
module Muxb3(a2, a1, a0, sb, b) ;
    parameter k = 1 ;
    input [k-1:0] a0, a1, a2 ; // inputs
    input [1:0] sb ; // binary select
    output[k-1:0] b ;
    wire [2:0] s ;

    dec #(2,3) d(sb,s) ; // Decoder converts binary to one-hot
    mux3 #(k) m(a2, a1, a0, s, b) ; // multiplexer selects input
endmodule
```

```
always_comb begin
    case (sb)
        0: b = a0;
        1: b = a1;
        2: b = a2;
        default: b = {k{1'b0}};
    end
end
```

那大的MUX怎麼辦?

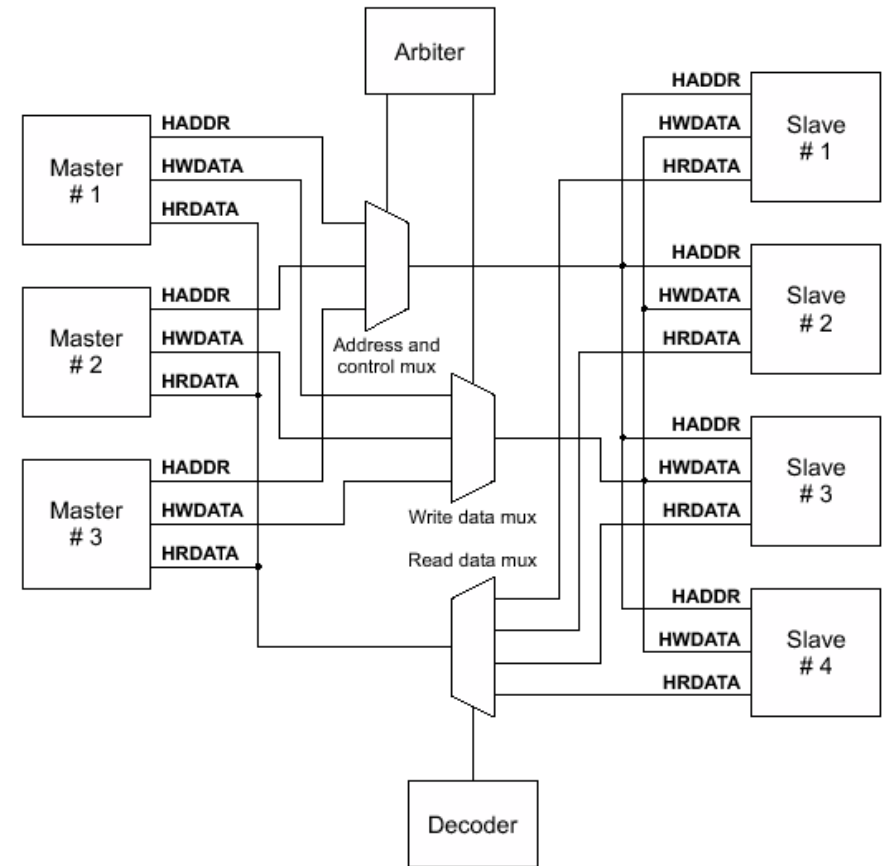


ARBITER AND PRIORITY ENCODER

找第一個1

0000**1**0111

Arbiter

 - Arbiter handles requests from multiple devices to use a single resource
 - For bus arbitration
 - Normalization in floating point operations



e.g. **LSB has the higher priority**



input	0101_1 1 00
Output	0000_0100

Finds first “1” bit in r

Leading one detector


$g[i]=1$ if $r[i]=1$ and $r[j]=0$ for $j \geq i$

1-Bit and 4-bit Arbiters

  

$G0=r0,$
 $G1=\text{none} \ \& \ r1 = r0' \ \& \ r1;$

Using Look-Ahead

 

Quiz: What's the difference between These two?

Implementing Arbitrary Width Arbiter Using Verilog

```
// arbiter (arbitrary width),
// LSB is the highest priority
```


```
module Arb(r, g) ;
  parameter n=8 ;
  input  [n-1:0] r ;
  output [n-1:0] g ;
  wire   [n-1:0] c ;
  wire   [n-1:0] g ;

  assign c = { (~r[n-2:0] & c[n-2:0]), 1'b1 } ;
  assign g = r & c ;
endmodule
```

```
always_comb begin
  casez (r)
    4'b0000: g = 4'b0000;
    4'b???1: g = 4'b0001;
    4'b??10: g = 4'b0010;
    4'b?100: g = 4'b0100;
    4'b1000: g = 4'b1000;
    default: g = 4'hx;
  endcase
end
```

Bit-slice coding style using
concatenation {a, b}
index ranges c[n-2:0]
c is 1s up to first 1 in r, then 0s


 
$g[i]=1$ if $r[i]=1$ and $r[j]=0$ for $j \geq i$



Priority Encoder

- Priority Encoder:
 - n-bit input signal **a**
 - m-bit output signal **b**
 - **b** indicates the position of the first 1 bit in **a**
  
```
always_comb begin
    casez (r)
        4'b???1: g = 2'd0;
        4'b??10: g = 2'd1;
        4'b?100: g = 2'd2;
        4'b1000: g = 2'd3;
        default: g = 2'dx;
    endcase
end
```




Check example 8.3 for programmable priority encoder

Priority Encoder with if-else

```

assign valid_in = |in; //檢查不合法輸入
always @(in) begin
    if (in[3]) y = 3; else
    if (in[2]) y = 2; else
    if (in[1]) y = 1; else
    if (in[0]) y = 0; else
        y = 2'bxx;
    end

```

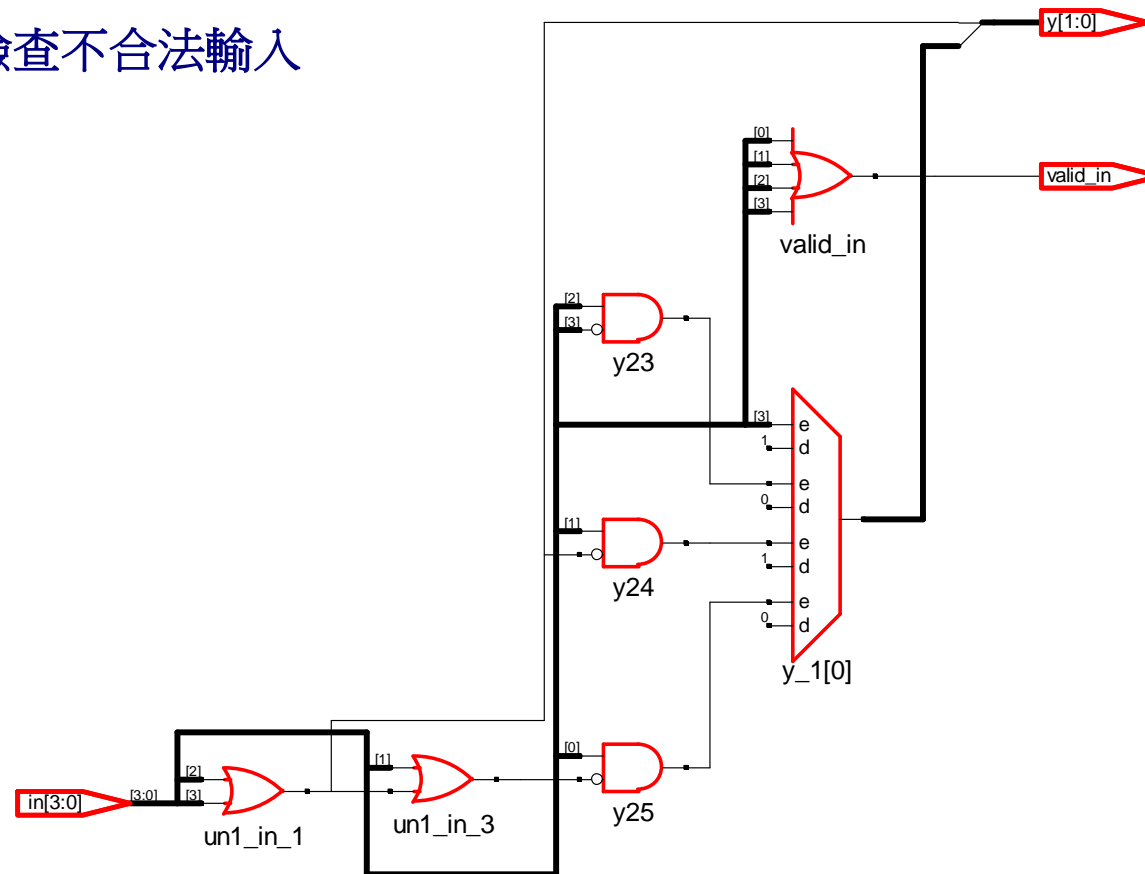

Priority Encoder with Priority if-else

- Priority (SystemVerilog syntax)
 - 告訴simulator/synthesizer 就照這個順序執行，沒列在上面的就當作don't care，可以被化簡

```
module encoder (  
    input in0 , in1 , in2 , in3 ,  
    output logic [3:0] encoded_output ;  
    always_comb  
        priority if ( in0 ) encoded_output = 4'b0001 ;  
            else if ( in1 ) encoded_output = 4'b0010 ;  
            else if ( in2 ) encoded_output = 4'b0100 ;  
            else if ( in3 ) encoded_output = 4'b1000 ;  
endmodule
```

Priority Encoder if-else (?:) v.s. case

```


module mux (in0, in1, in2, in3, sel, mux_out);
    input    in0, in1, in2, in3;
    input    [1:0] sel;
    output   mux_out;
    reg      mux_out;
    always @(in0 or in1 or in2 or in3 or sel) begin
        case (sel)
            2'b00: mux_out = in0;
            2'b01: mux_out = in1;
            2'b10: mux_out = in2;
            default: mux_out = in3;
        endcase
    end
endmodule

```

```


module p_encoder (in0, in1, in2, in3, sel, p_encoder_out);
    input    in0, in1, in2, in3;
    input    [1:0] sel;
    output   p_encoder_out;
    reg      p_encoder_out;
    always @(in0 or in1 or in2 or in3 or sel) begin
        if (sel == 2'b00)
            p_encoder_out = in0;
        else if (sel == 2'b01)
            p_encoder_out = in1;
        else if (sel == 2'b10)
            p_encoder_out = in2;
        else
            p_encoder_out = in3;
    end
endmodule

```

 

case 合成的電路比較快

 Generally, If-Else is **slower** unless you intend to build a priority encoder!




Priority Encoder “if-then-else”

When to use?

```

always_comb
begin
    if (sel == 3'h0)
        out = in[0];
    else if (sel == 3'h1)
        out = in[1];
    else if (sel == 3'h2)
        out = in[2];
    else if (sel == 3'h3)
        out = in[3];
    else if (sel == 3'h4)
        out = in[4];
    else
        out = in[5];
end

```


 


最慢到的輸入放在最靠近輸出

- Assign highest priority to a late arriving critical signal
- Nested “if-then-else” can increase area and delay
- Use “case” statement if possible to describe the same function

TLDR: if-then-else vs. case

 
 
- *If-then-else* often infers a cascaded encoder
 - inputs signals with different arrival time
- *case* infers a single-level mux
 - *case* is better if priority encoding is not required
 - *case* is generally simulated faster than *if-then-else*
- *conditional assignment* (? :)
 - infers a mux with slower simulation performance
 - better avoided



COMPARATORS

Magnitude Comparator

  //bit-slice design with leaf cell (from LSB)
 //note that initial value to be considered



```
// magnitude comparator
module MagComp(a, b, gt) ;
  parameter k=8 ;
  input  [k-1:0] a, b ;
  output gt ;
  wire  [k-1:0] eqi = a ^ b ;
  wire  [k-1:0] gti = a & ~b ;
  wire  [k:0]   gtb {((eqi[k-1:0] & gtb[k-1:0]) | gti[k-1:0]), 1'b0} ;
  wire  gt = gtb[k] ; //MSB is selected as output gt;
endmodule
```



assign gt = (a > b) ;

READ ONLY MEMORIES (ROM)


RANDOM ACCESS MEMORY (RAM)

Read-only memory (ROM)

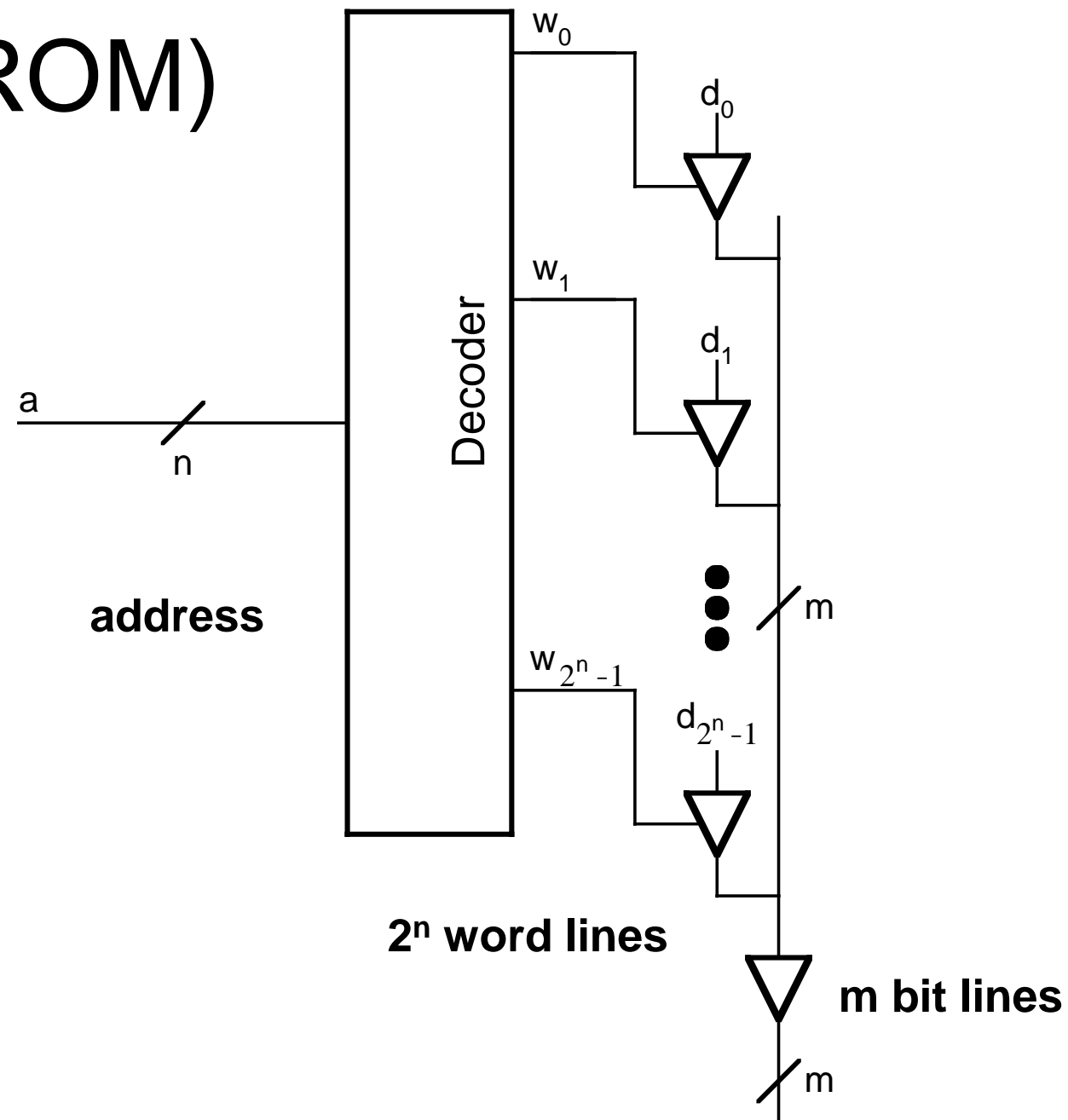 - 存常數值，
- 可實現任意函數
- 需要address decoder，所以大小夠大才划算



2-D array implementation

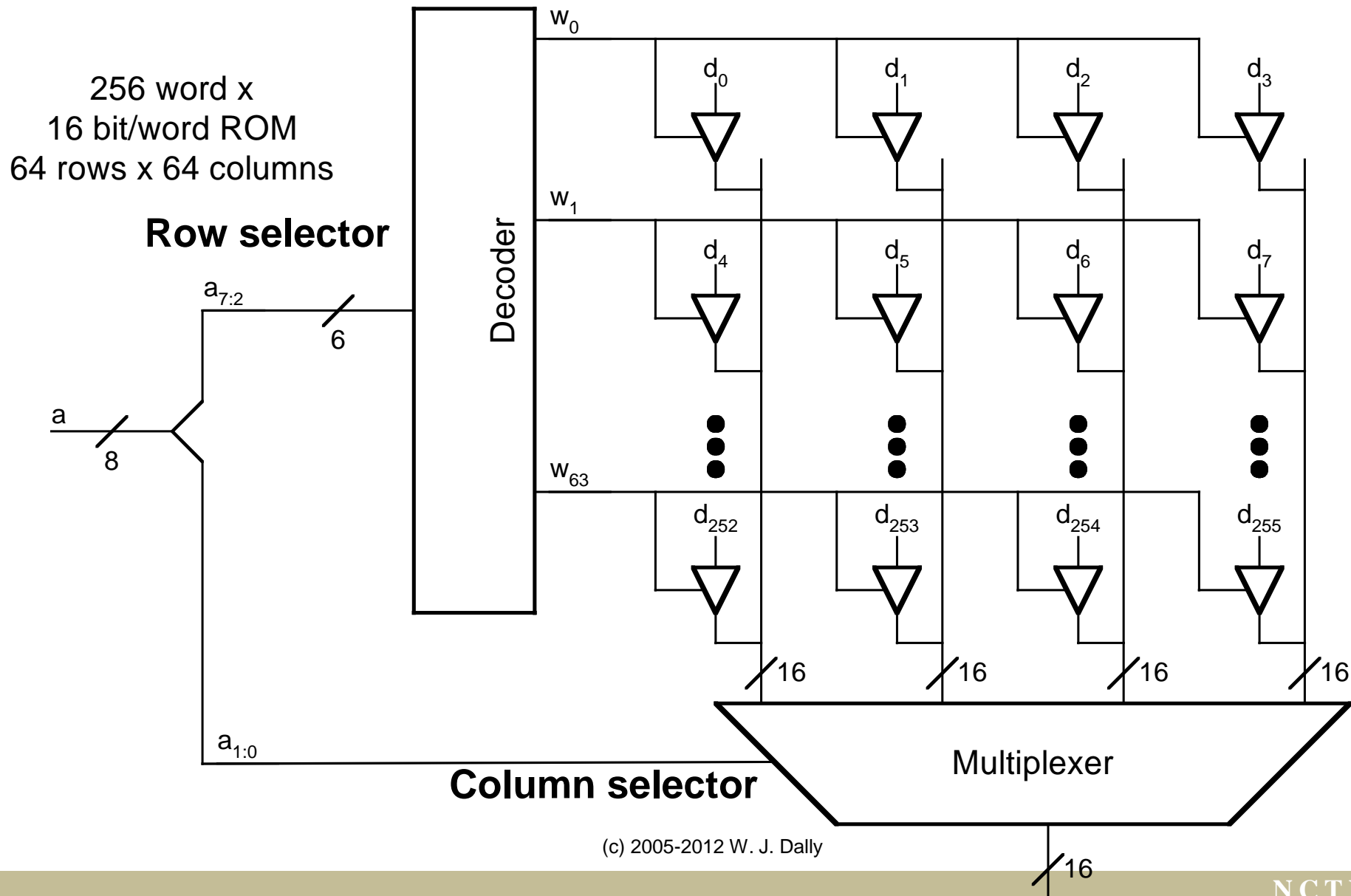

ROM Model: loading data from file

```

module rom_using_file (
  input  wire [7:0] address , // Address input
  output wire [7:0] data    , // Data output
  input  wire      read_en  , // Read Enable
  input  wire      ce       // Chip Enable
);

  reg [7:0] mem [0:255] ;

  assign data = (ce && read_en) ? mem[address] : 8'b0;

  initial begin
    $readmemb("memory.list", mem); // memory_list is memory file
  end

endmodule

```

memory.list

11001

11010

@5 11001000 // 将11001存入mem[5]

@2 11010000 //将11010存入mem[2]

@7 //直至7开始

11001000

00000000

11111111

適合大的ROM size

ROM with case

```
module rom_using_case (  
    input wire [7:0] address , // Address input  
    output reg [7:0] data , // Data output  
    input wire read_en , // Read Enable  
    input wire ce // Chip Enable  
);
```

```
always_comb  
begin  
    case (address)  
        0 : data = 10;  
        1 : data = 55;  
        2 : data = 244;  
        3 : data = 0;  
        4 : data = 1;  
  
        .....  
        13 : data = 8'h90;  
        14 : data = 8'h70;  
        15 : data = 8'h90;  
    endcase  
end  
endmodule
```

適合很小的ROM size

RAM Model

```

module ram_sp_sr_sw #(parameter DATA_WIDTH = 8,
                      parameter ADDR_WIDTH = 8,
                      parameter RAM_DEPTH = (1 << ADDR_WIDTH)) (
    input  wire      clk      , // Clock Input
    input  wire [ADDR_WIDTH-1:0] address , // Address Input
    inout  wire [DATA_WIDTH-1:0] data    , // Data bi-directional
    input  wire      cs      , // Chip Select
    input  wire      we      , // Write Enable/Read Enable
    input  wire      oe      , // Output Enable
);
//-----Internal variables-----
reg [DATA_WIDTH-1:0] data_out ;
// Use Associative array to save memory footprint
typedef reg [ADDR_WIDTH-1:0] mem_addr;
reg [DATA_WIDTH-1:0] mem [mem_addr];

```

```
//-----Code Starts Here-----  
// Tri-State Buffer control  
// output : When we = 0, oe = 1, cs = 1  
assign data = (cs && oe && !we) ? data_out : 8'bz;  
  
// Memory Write Block  
// Write Operation : When we = 1, cs = 1  
always @ (posedge clk)  
begin : MEM_WRITE  
    if ( cs && we ) begin  
        mem[address] = data;  
    end  
end  
  
// Memory Read Block  
// Read Operation : When we = 0, oe = 1, cs = 1  
always @ (posedge clk)  
begin : MEM_READ  
    if (cs && !we && oe) begin  
        data_out = mem[address];  
    end  
end  
  
endmodule // End of Module ram_sp_sr_sw
```

Reference

- [Dally] Ch. 7. 8. 9
- [Roth] Ch. 4
- <http://www.asic-world.com/index.html>