

# Lecture 7-2 Design For Area Minimization

---

# Outlines

- Analysis of area cost
- Algorithm: Complexity reduction
- Architecture: resource sharing

# **ANALYSIS OF AREA COSTS**

# Synthesis

- **Synthesis** = Translation + Logic Optimization + Technology Mapping

```
always @ (a, b)
  case ({a,b})
    2'b00: out = 1;
    2'b01: out = 1;
    2'b11: out = 1;
    default: out = 0;
  endcase
```



Translation

$$\text{out} = \bar{a}b + ab + \bar{a}\bar{b}$$

Logic  
Optimization

$$\text{out} = \bar{a} + b$$

Technology  
Mapping

  


# Synthesis is Constraint-Driven

You should  
specify your  
constraints


(Delay)

(Area)

(Power Consumption)

 

Area

 


# HDL for Synthesis


- “Bad” HDL code does not allow efficient optimization during synthesis
  - Garbage in, garbage out!
- Logic synthesizer doesn't do magic! designer has to take some responsibility in coding.

❖ Example:
 
```
input sub;  
input [3:0] a,b;  
output [3:0] y;  
assign y = sub ? (a-b) : (a+b)
```


 
```
input sub;  
input [3:0] a,b;  
output [3:0] y;  
wire [3:0] tmp;  
assign tmp = sub ? ~b : b;  
assign y = a + tmp + {3'b0,sub}
```



More efficient

# HDL for Synthesis (General Guidelines)

- Think Hardware:
  - Write HDL hardware descriptions
    - Think of the topology implied by the code
  - Do not write HDL simulation models
    - No explicit delays
    - No file I/O
- Think RTL:
  - Writing in an RTL coding style means describing:
    - Register architecture
    - Circuit topology
    - Functionality between registers
  - Synthesis tool optimizes logic between registers:
    - It does not optimize the register placement

# How to Read You Area Reports

```
*****
Report : area
Design : prime
Version: 2003.06
Date   : Sat Oct  4 11:38:08 2003
*****
```

Library(s) Used:

XXXXX

```
Number of ports:      5
Number of nets:       9
Number of cells:      5
Number of references: 4
```

```
Combinational area:    7.000000
Noncombinational area: 0.000000
Net Interconnect area: undefined (Wire load has zero
                             net area)
```

```
Total cell area:      7.000000
Total area:            undefined
```

Noncombinational part: DFF, SRAM, latch

**Left part: area report**

**Right part: timing report**

```
*****
Report : timing
        -path full
        -delay max
        -max_paths 1
Design : prime
Version: 2003.06
Date   : Sat Oct  4 11:38:08 2003
*****
```

Operating Conditions:

Wire Load Model Mode: enclosed

```
Startpoint: in[2] (input port)
Endpoint: isprime (output port)
Path Group: (none)
Path Type: max
```

Des/Clust/Port	Wire Load Model	Library
prime	2K_5LM	XXXXX

Point	Incr	Path
-		
input external delay	0.000	0.000 r
in[2] (in)	0.000	0.000 r
U4/Y (EX210)	0.191	0.191 f
U5/Y (BF051)	0.116	0.307 r
U1/Y (BF052)	0.168	0.475 f
isprime (out)	0.000	0.475 f
data arrival time		0.475

(Path is unconstrained)



# Area Estimation

- 1 DFF, 1 adder, 1 2:1 MUX:
  - 7 gate counts
- Multiplier: depends on architecture
  - $N \times N \Rightarrow N^2 * 7$
- Estimate data flow part first
  - How many adder/multiplier have been used
- Control part (FSM)
  - Extra 5 to 10% area cost

# Where your area goes?

- Use Synopsys Design Compiler to analyze this
  - Not covered in this course
- Code review
  - Sequential part: Count DFF numbers generated in each always\_ff
    - Unique output variables in the Verilog commands
    - Avoid unnecessary pipeline or DFF storages
  - Data path part
    - Count adder/multiplier and other and/or logic
  - Controller part
    - Simplify your FSM
- Rule of thumb
  - Controller: take 5 to 10% of area
  - Data path takes 40% to 70%, memory or buffers takes the rest

# Complexity Reduction

- Algorithm optimization
  - Application dependent
  - Something more like used in C program
  - E.g. assign  $y = a * b$ ;
  - If  $b = 4'h2$ ;
    - assign  $y = a \ll 1$ ;

# AREA OPTIMIZATION

# Concept

- Folding (or rolling up the pipeline)
  - Time sharing the same logic to save area
- Algorithm change

# Area-related Techniques:

- Area is the second primary factors of a digital design
  - A topology that targets area is one that reuses the logic resources to the greatest extent possible, often at the expense of throughput (speed).
  - This requires a recursive data flow, where the output of one stage is fed back to the input for similar processing.

# Area-related Techniques: Rolling Up the Pipeline

- Opposite to the unrolling the loop to increase throughput
  - Unrolling the loop achieved by adding more registers to hold intermediate values, i.e., more area
  - Thus to reduce the area the reversed action should be done (i.e., Sharing)
- **Resource Sharing** is used where there are functional blocks that can be used in other areas of the design or even in different modules
  - Sharing logic resources requires special control circuitry to determine which elements are input to the particular structure

# Rolling Up the Pipeline

- Calculation of  $P = A * B$ 
  - A: a normal integer with the fixed point just to the right of the LSB (8 bits)
  - B: a fractional number with a fixed point just to the left of the MSB (8 bits)
  - P: the product, which requires only 8-bits
- One implementation alternative:
  - Critical path: one multiplier (complex itself)
  - One product every clock cycle (high throughput)

```
module mult8(  
  output [7:0] P,  
  input [7:0] A,  
  input [7:0] B,  
  input clk);  
  reg [15:0] prod16;  
  assign P= prod16[15:8];  
  always @(posedge clk)  
    prod16 <= A * B;  
endmodule
```



# Rolling Up the Pipeline : Resource Sharing


- Rolling Up the Pipeline:
  - Using series of shift-and-add operations
  - Smaller critical path
  - Less area due to the simple operations and sharing
  - One product every 8 clock cycles! (low throughput)

```
module mult8(output done,output reg [7:0] product,
input [7:0] A, input [7:0] B, input clk, input start);
reg [4:0] multcounter; // number of shift/adds
reg [7:0] shiftB; // shift register for B
reg [7:0] shiftA; // shift register for A
wire adden; // enable addition
assign adden = shiftB[7] & !done;
assign done = multcounter[3];
always @(posedge clk) begin
if(start) multcounter <= 0;
else if(!done) multcounter <= multcounter + 1;
// shift register for B
if(start) shiftB <= B;
else shiftB[7:0] <= {shiftB[6:0], 1'b0};
```

```
// shift register for A
if(start) shiftA <= A;
else shiftA[7:0] <= {shiftA[7], shiftA[7:1]};
// calculate multiplication
if(start) product <= 0;
else if(adden) product <= product + shiftA;
end
endmodule
```

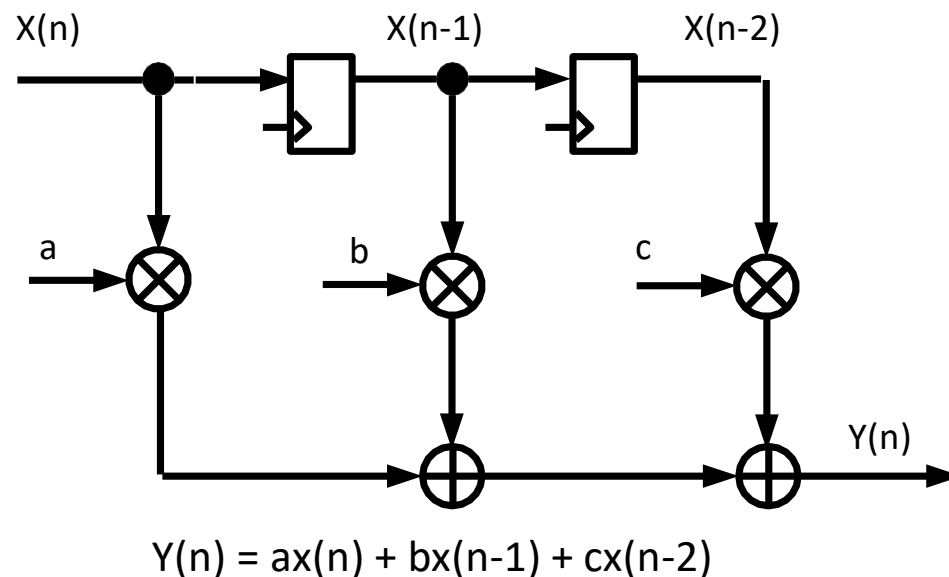
# Resource Sharing: Area Reduction Technique

- Back to FIR Filter:
  - Three multiplications, two adders, two registers


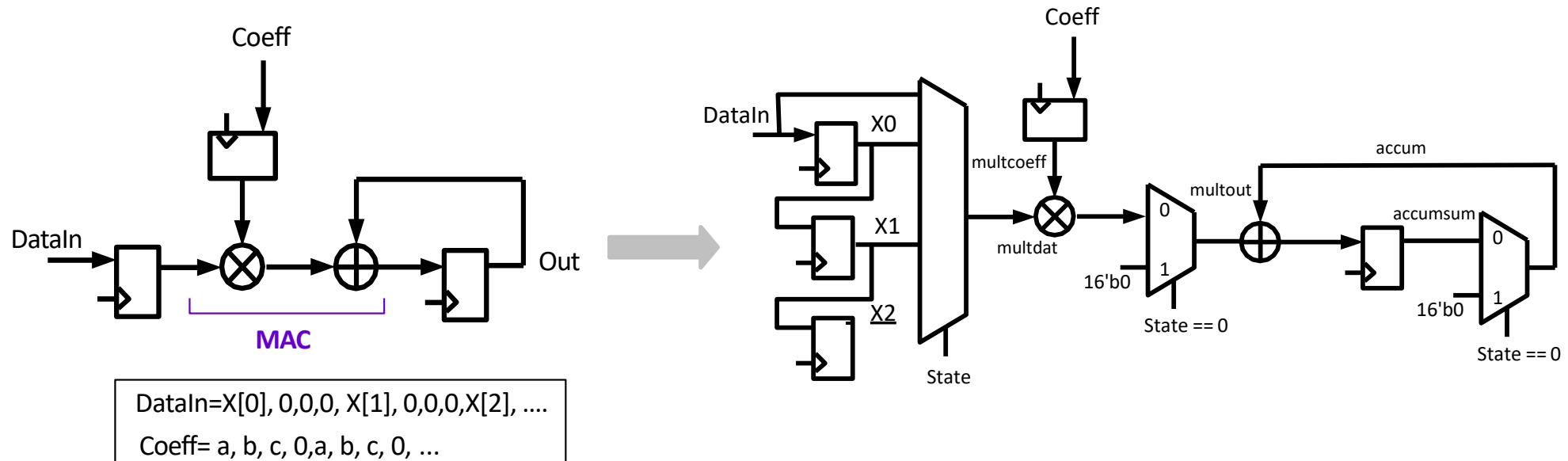
# Resource Sharing: Area Reduction Technique

- Sharing the Multiply-Accumulate (MAC) to reduce area:
  - One multiplication, one adder, one register
  - Requires some control logic to determine which input is inserted (FSM)




# Resource Sharing: Area Reduction Technique

```
module sharing(  
    output reg [15:0] Out,  
    input clk,  
    input [7:0] datain, // X[0]  
    input [7:0] coeffA, coeffB, coeffC; // coeffs for low pass filter  
    // define input/output samples  
    reg [7:0] X0, X1, X2;  
    reg [2:0] state; // holds state for sequencing through mults  
    wire [15:0] accum; // accumulates multiplier products  
    reg [15:0] accumsum;  
    wire [15:0] multout; // multiplier product  
    reg [7:0] multdat;  
    reg [7:0] multcoeff;  
  
    assign multout = (state==0)?16'b0:multcoeff * multdat;  
    // clearing and loading accumulator  
    assign accum = (state==0)?16'b0:accumsum;  
  
    always @(posedge clk)  
        accumsum <= accum + multout;
```


```
always @ (posedge clk) begin  
    case(state)  
        0: begin // load new data  
            X0 <= datain; X1 <= X0; X2 <= X1;  
            multdat <= datain; multcoeff <= coeffA;  
            state <= 1;  
            Out <= accumsum;  
        end  
        1: begin // A*X[0] is done, load B*X[1]  
            multdat <= X1; multcoeff <= coeffB;  
            state <= 2;  
        end  
        2: begin // B*X[1] is done, load C*X[2]  
            multdat <= X2; multcoeff <= coeffC;  
            state <= 3;  
        end  
        3: begin // C*X[2] is done, load output  
            state <= 0;  
        end  
        default  
            state <= 0;  
    endcase  
end  
endmodule
```
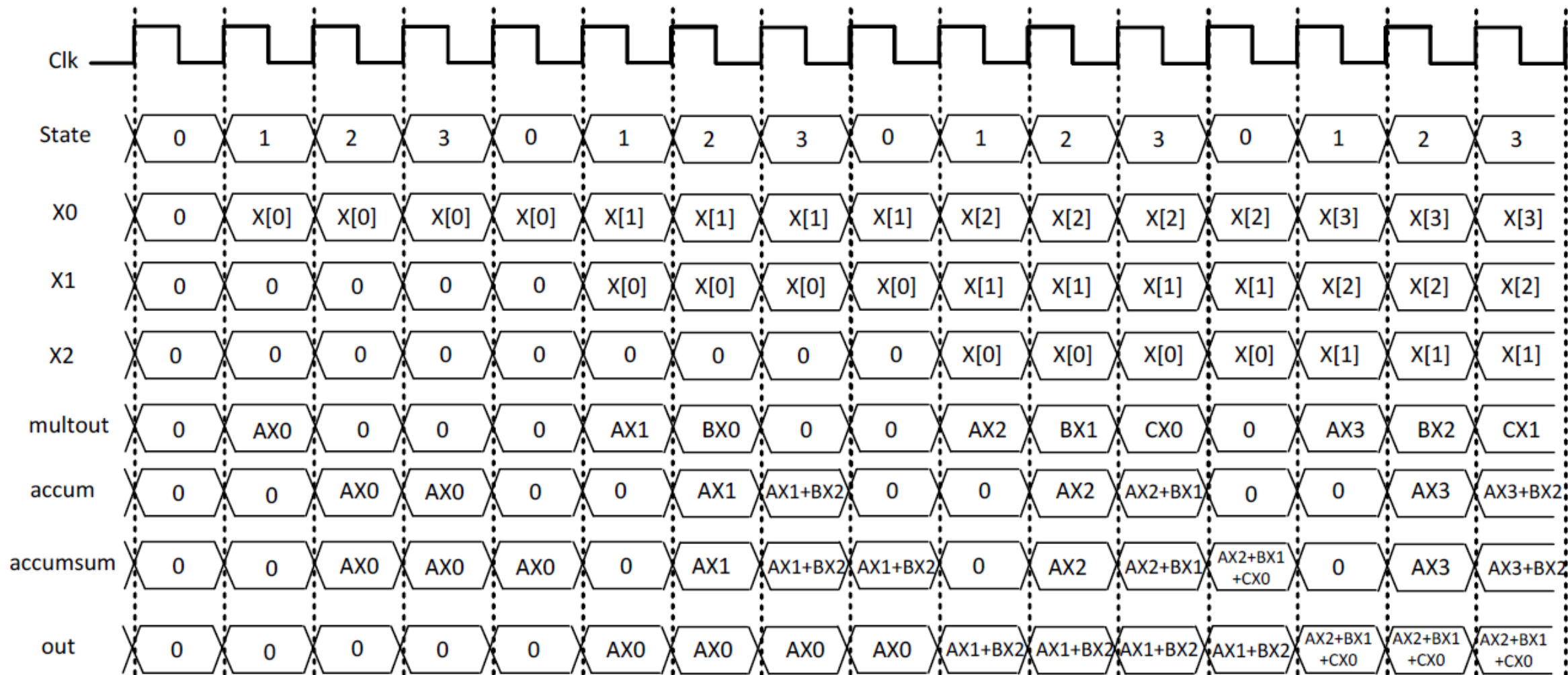
# Resource Sharing: Area Reduction Technique



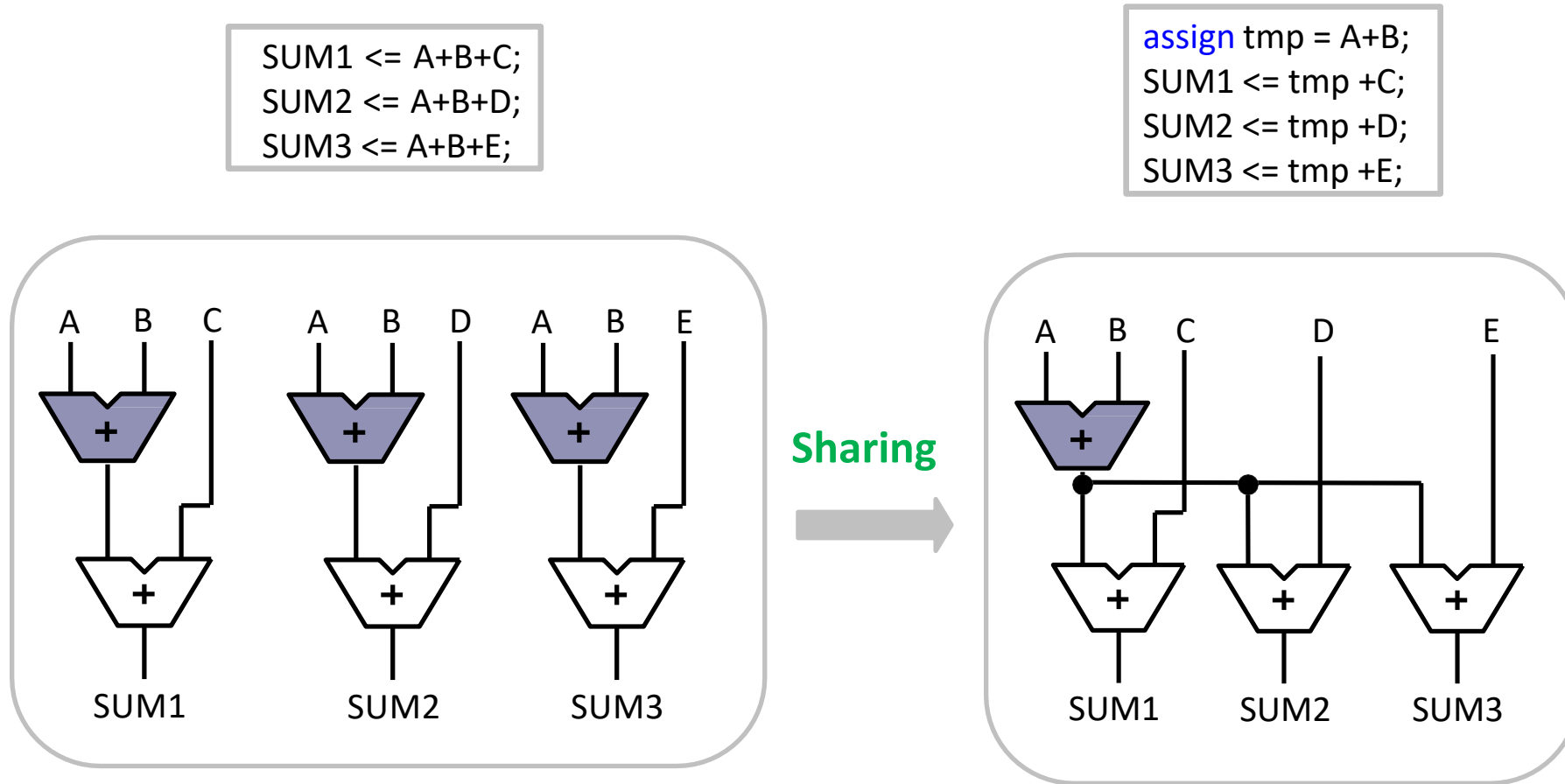
# Resource Sharing: Area Reduction Technique

- HDL coding style can force a specific topology to be synthesized


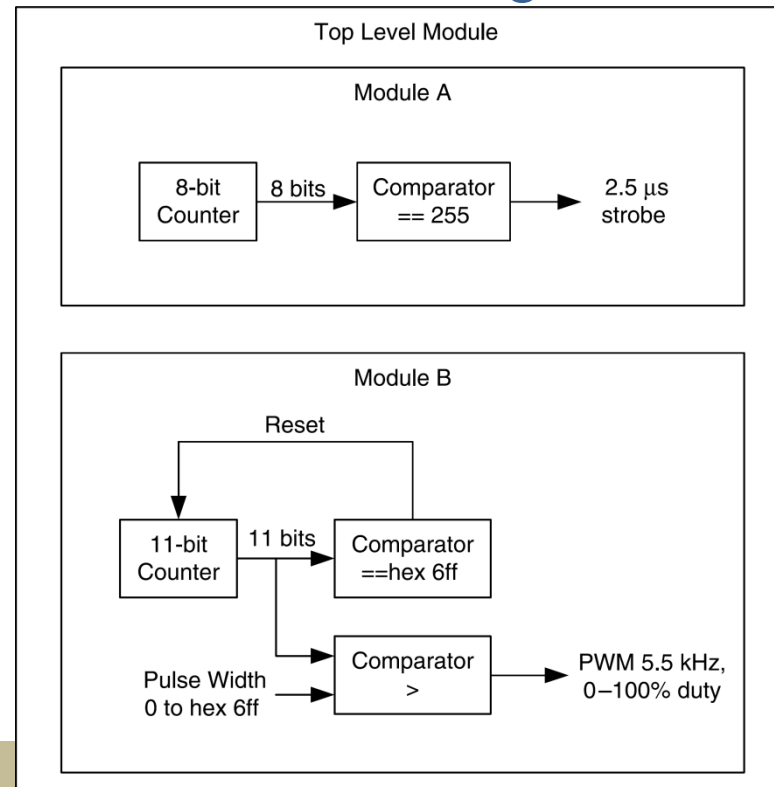
# Resource Sharing: Area Reduction Technique

- Let's assume we have two counters controlling different design sections
  - CounterA, a free running 8-bit counter
  - CounterB, an 11-bit counter, counting from 0 to 1666 and resets to zero




# Resource Sharing: Area Reduction Technique

- Resource-shared version of these two counters

For compact designs where area is the primary requirement, search for resources that have similar counterparts in other modules that can be brought to a global point in the hierarchy and shared between multiple functional areas.


**Shared Part**

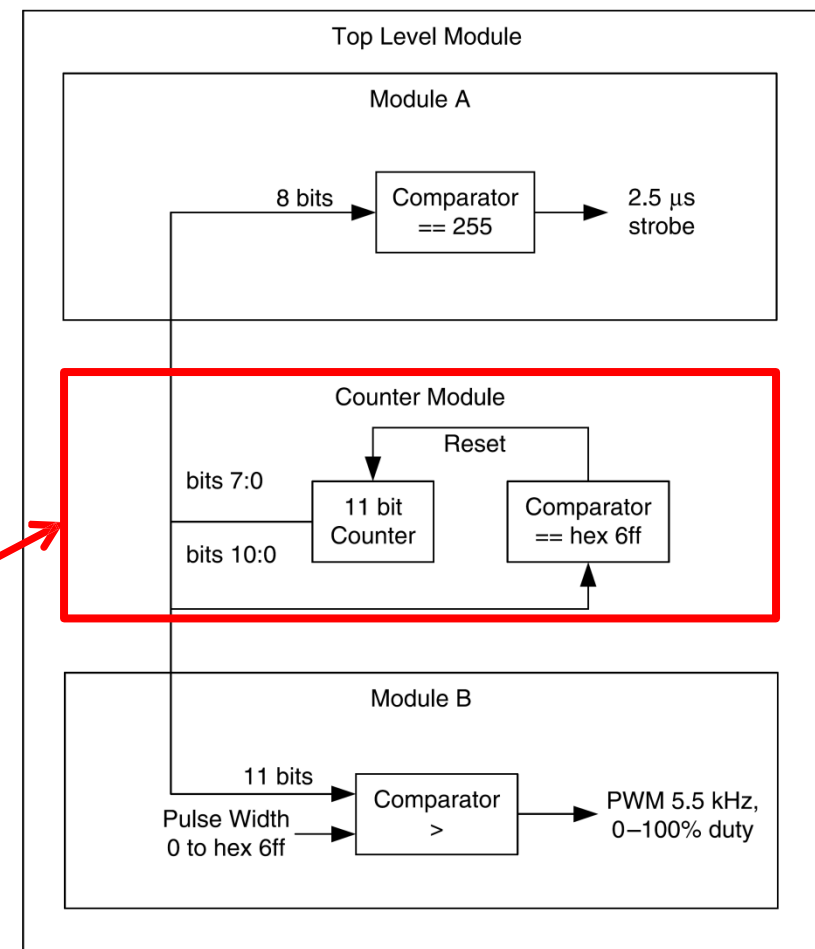



 
# Architectural Techniques : Resource Sharing

More than one RTL statement can utilize an expensive computational resource.


 
```
always @(a or b or c
        or d or s)
begin
    if (s)
        y = a + b;
    else
        y = c + d;
end
```



```
always @(a or b or c
        or d or s)
begin: newscope
    reg tmp1, tmp2;
    tmp1 = s ? a : c;
    tmp2 = s ? b : d;
    y = tmp1 + tmp2;
end
```

Some synthesis tools automatically share resources.

What if your synthesis tool does not automatically share resources?

You can write your RTL code to do its own resource sharing!