

Digital Circuits and Systems

Lecture 9 Factoring State Machines

Tian Sheuan Chang

大的FSM要如何設計?若其中state變化有規則，可以把有規則的部分獨立

Outline [Dally Ch.17]

- Light flasher
- Traffic light controller

大的FSM要如何設計? Design A Large FSM

先講結論 Short Summary

- 若其中state變化有規則，
 - 可以把有規則的部分，單獨分離開來 Separate the regular part
 - 形成階層式FSM, Design a hierarchical FSM
- 好處
 - 更簡單
 - 所需硬體更少

設計哲學：把大問題切割成小問題，比較好作

- **Divide and Conquer**: Divide a big problem into several smaller problems
- Last lecture - data/control partitioning
- **This lecture – factoring state machines**
- Later – system partitioning

Similar to factoring in logic design and constant multiplication

$$a(b+c)+bc = ab+ac+bc$$


$$X*(011011011011_2) = X*011*(2^0 + 2^3 + 2^6 + 2^9)$$

LIGHT FLASHER

Specification Of Light Flasher

- Inputs: **in**
- Outputs: **out**
- Operation:
 - When **in** = 1, FSM goes through 5 sequences:
 - *On-Off-On-Off-On*
 - Each *On* sequence:
 - **out** = 1
 - 6 cycles long
 - Each *Off* sequence:
 - **out** = 0
 - 4 cycles long
 - After 5 sequences, FSM goes back to OFF state to wait for new input


Light Flasher State Diagram

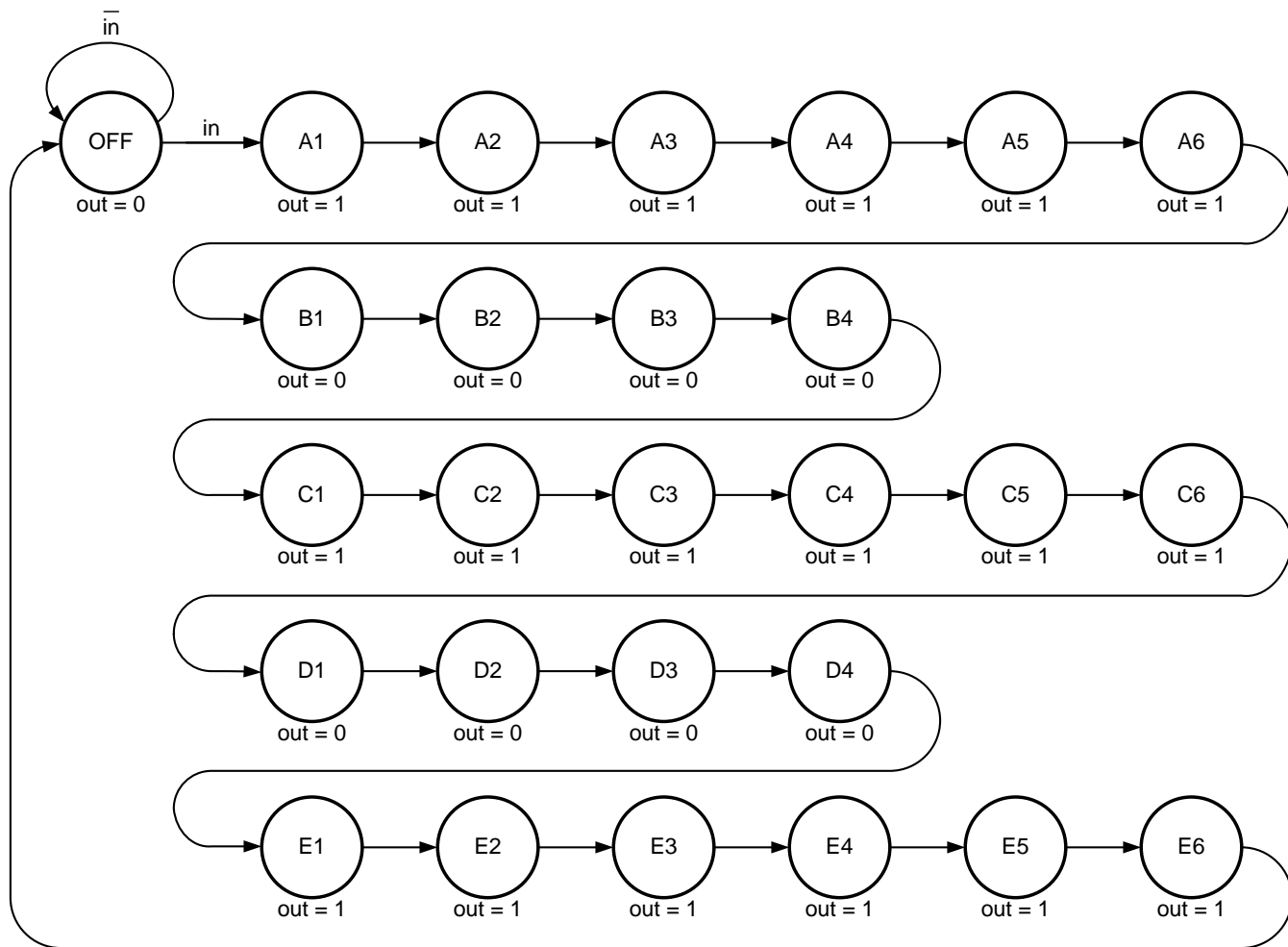

- *On-Off-On-Off-On*
- Each *On* sequence:
 - $out = 1$
 - 6 cycles long
- Each *Off* sequence:
 - $out = 0$
 - 4 cycles long

這很直接，但很多on 或 off 作的事情一樣，可以不用那麼多 State



Factored light flasher

 

把數on 或off cycle數量的電路獨立
以便共用

*Timer loads value 5 or 3,
based on tsel

State diagram of factored light flasher

  

- *On-Off-On-Off-On*
- Each *On* sequence:
 - $out = 1$
 - 6 cycles long
- Each *Off* sequence:
 - $out = 0$
 - 4 cycles long


```

module Flash(clk, rst, in, out) ;
  input clk, rst, in ; // in triggers start of flash sequence
  output out ;          // out drives LED
  reg out ;              // output
  wire [`SWIDTH-1:0] state, next ; // current state
  reg [`SWIDTH-1:0] next1 ; // next state without reset
  reg tload, tsel ;      // timer inputs
  wire done ;           // timer output

  // instantiate state register
  DFF #(`SWIDTH) state_reg(clk, next, state) ;

  // instantiate timer: data path
  Timer1 timer(clk, rst, tload, tsel, done) ;

```

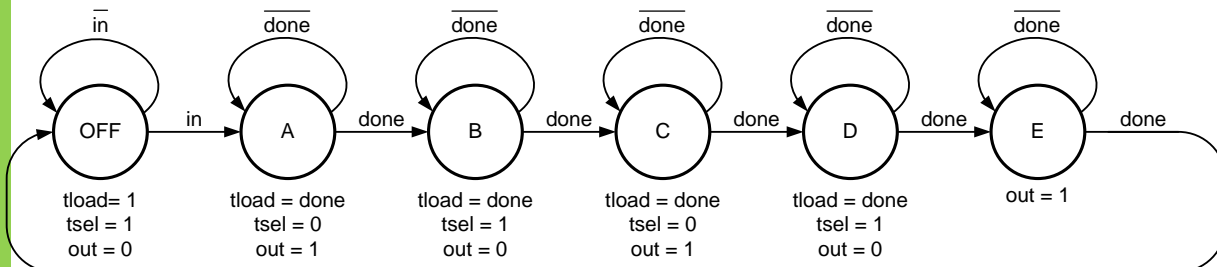


```

always @* begin
  case(state)
    `S_OFF: {out, tload, tsel, next1} =
      {1'b0, 1'b1, 1'b1, in ? `S_A : `S_OFF} ;
    `S_A: {out, tload, tsel, next1} =
      {1'b1, done, 1'b0, done ? `S_B : `S_A} ;
    `S_B: {out, tload, tsel, next1} =
      {1'b0, done, 1'b1, done ? `S_C : `S_B} ;
    `S_C: {out, tload, tsel, next1} =
      {1'b1, done, 1'b0, done ? `S_D : `S_C} ;
    `S_D: {out, tload, tsel, next1} =
      {1'b0, done, 1'b1, done ? `S_E : `S_D} ;
    `S_E: {out, tload, tsel, next1} =
      {1'b1, done, 1'b1, done ? `S_OFF : `S_E} ;
    default: {out, tload, tsel, next1} =
      {1'b1, done, 1'b1, done ? `S_OFF : `S_E} ;
  endcase
end


  assign next = rst ? `S_OFF : next1 ;
endmodule

```

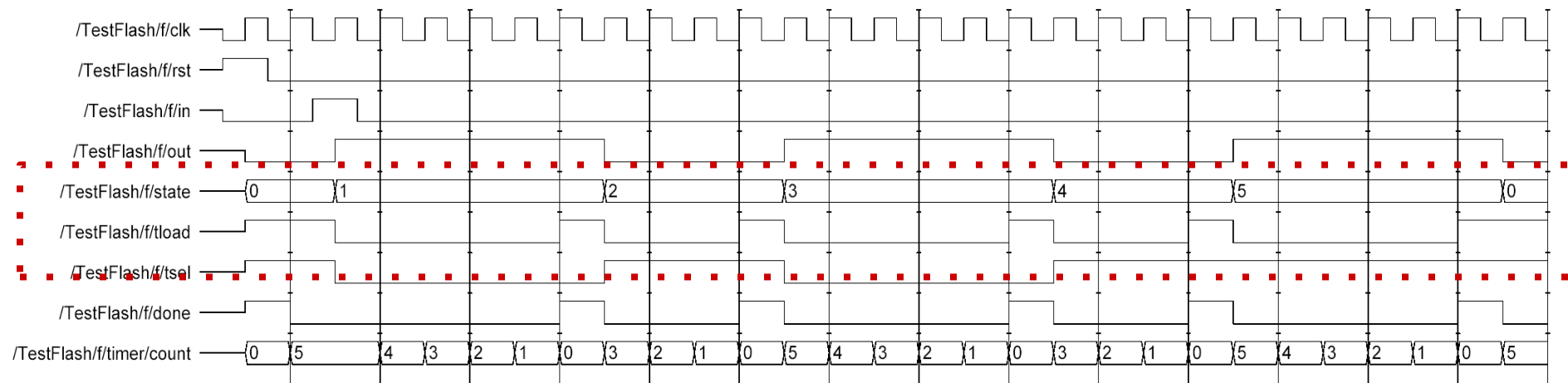Waveforms from simulation of light-flasher FSM



Still redundancy in state diagram

 

On-Off-On-Off-On

On-Off-On-Off-On

States A, C, E are similar (Flash on)


States B, D are similar (Flash off)

Can we reduce the state number by looking into these similar features?

還可以再化簡，除原來數on/off的cycle數外，用另一個算剩下的flash個數

=> Double factored FSM


Factor out “flash number”

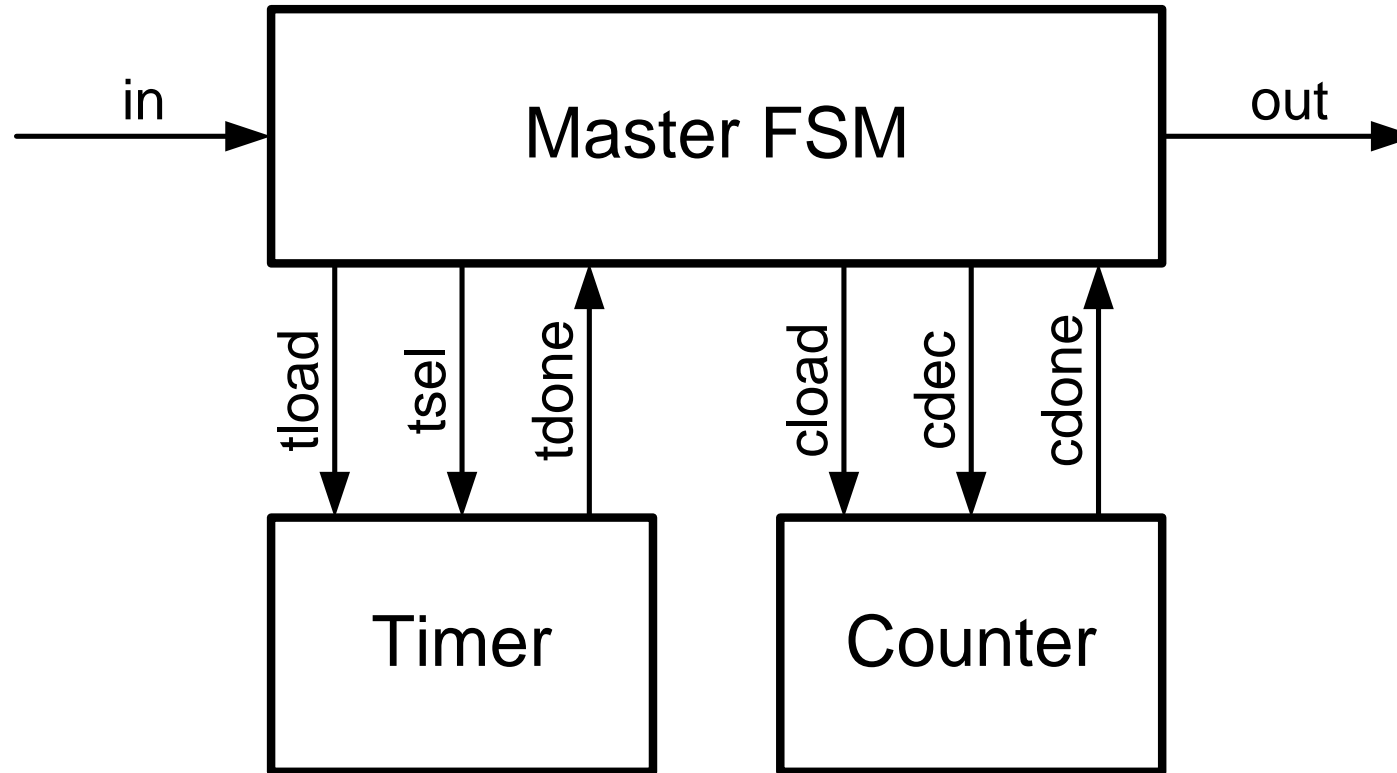


On-Off-On-Off-On

Why factoring out? Speed and programmability.

 State diagram of double-factored light flasher



On-Off-On-Off-On

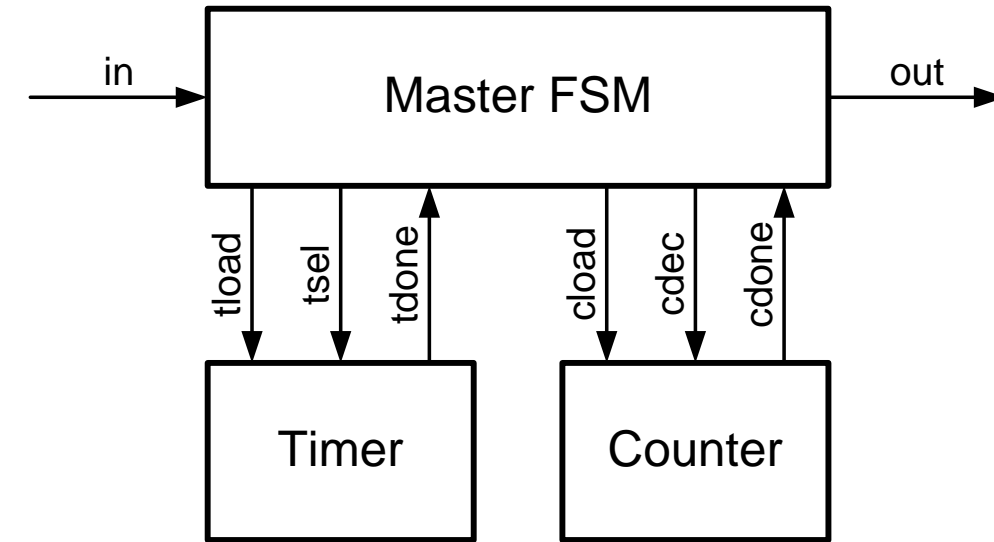

Off: timer, counter load 要倒數的值 (n-1: e.g 3 for four flashes)

FLASH: out = 1 (**on**), timer 開始倒數, counter 不數, 數到最後一個cycle, tdone = 1, 看cdone值進入space 或off

SPACE: out = 0 (**off**), timer 開始倒數, counter 不數, 數到最後一個cycle, tdone = 1, counter-1, 進入FLASH

```

module Flash2(clk, rst, in, out) ;
  input clk, rst, in ; // in triggers start of flash sequence
  output out ;          // out drives LED
  reg out ;              // output
  wire [`XWIDTH-1:0] state, next ; // current state
  reg [`XWIDTH-1:0] next1 ; // next state without reset
  reg tload, tsel, cload, cdec ; // timer and counter inputs
  wire tdone, cdone ; // timer and counter outputs


  // instantiate state register
  DFF #(`XWIDTH) state_reg(clk, next, state) ;

  // instantiate timer and counter
  Timer1 timer(clk, rst, tload, tsel, tdone) ;
  Counter1 counter(clk, rst, cload, cdec, cdone) ;


  always @(*) begin
    case(state)
      `X_OFF: {out, tload, tsel, cload, cdec, next1} =
        {1'b0, 1'b1, 1'b1, 1'b1, 1'b0,
         in ? `X_FLASH : `X_OFF} ;
      `X_FLASH: {out, tload, tsel, cload, cdec, next1} =
        {1'b1, tdone, 1'b0, 1'b0, 1'b0,
         tdone ? (cdone ? `X_OFF : `X_SPACE) : `X_FLASH} ;
      `X_SPACE: {out, tload, tsel, cload, cdec, next1} =
        {1'b0, tdone, 1'b1, 1'b0, tdone,
         tdone ? `X_FLASH : `X_SPACE} ;
    endcase
  end

  assign next = rst ? `X_OFF : next1 ;
endmodule

```

 

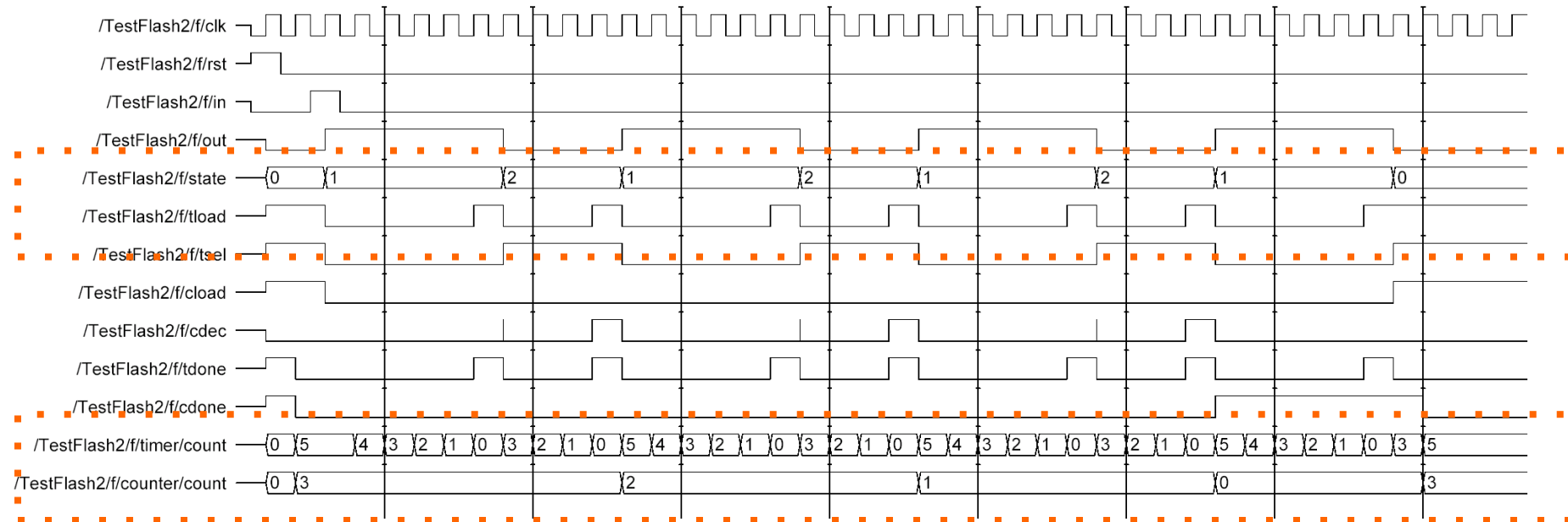Waveforms from simulation of twice- factored light flasher



Modifying the light flasher

- Making the light's "on" state last 7 cycles
- Adding 2 more "on" states
- The 3rd "on" lasts 15 cycles
- Making the light flash 206 times, which each flash lasting an arbitrary, predetermined number of cycles

Exercise: use the previous example to meet these requirements by changing parameters from the datapaths.

TRAFFIC LIGHT CONTROLLER

Cynical view of lecture up to now

- All we've done is build a counter with three subfields
 - Each field increments when previous field “wraps”
 - Most significant field is count
 - Next is on/off
 - Least is timer
- Lets look at a less trivial problem

Specification Of A New Traffic-Light Controller

- Inputs: `car_ew`, `car_lt` 東西向，左轉車輛
- Outputs: `nsgyr` `ewgyr` `ltgyr` 南北向，東西向，左轉燈號
- Operation:
 - Default: green light for north-south road
 - If `car_lt`: green light for left-turn
 - If $\sim \text{car_lt}$ & `car_ew`: green light for east-west road
 - Green light for left-turn and east-west roads stay on until either:
 - No more cars, or
 - Green light timer expires
 - Each green, yellow, and red light stay on for a time interval
 - Lighting sequence: green -> yellow -> red


Number of states required by 'flat' machine

- Sequences for NS, EW, LT (3)
- States in each sequence Yellow, Red, Green (3)
- Time in each state 9, 5, or 4 cycles (6)
- Time remaining before return to NS (13)
- Total states $3 \times 3 \times 6 \times 13 = 702$

階層式看法

- Sequences for NS, EW, LT (3)
 - States in each sequence Yellow, Red, Green (3)
 - Time in each state 9, 5, or 4 cycles (6)
- Time remaining before return to NS (13)


Block diagram of factored machine

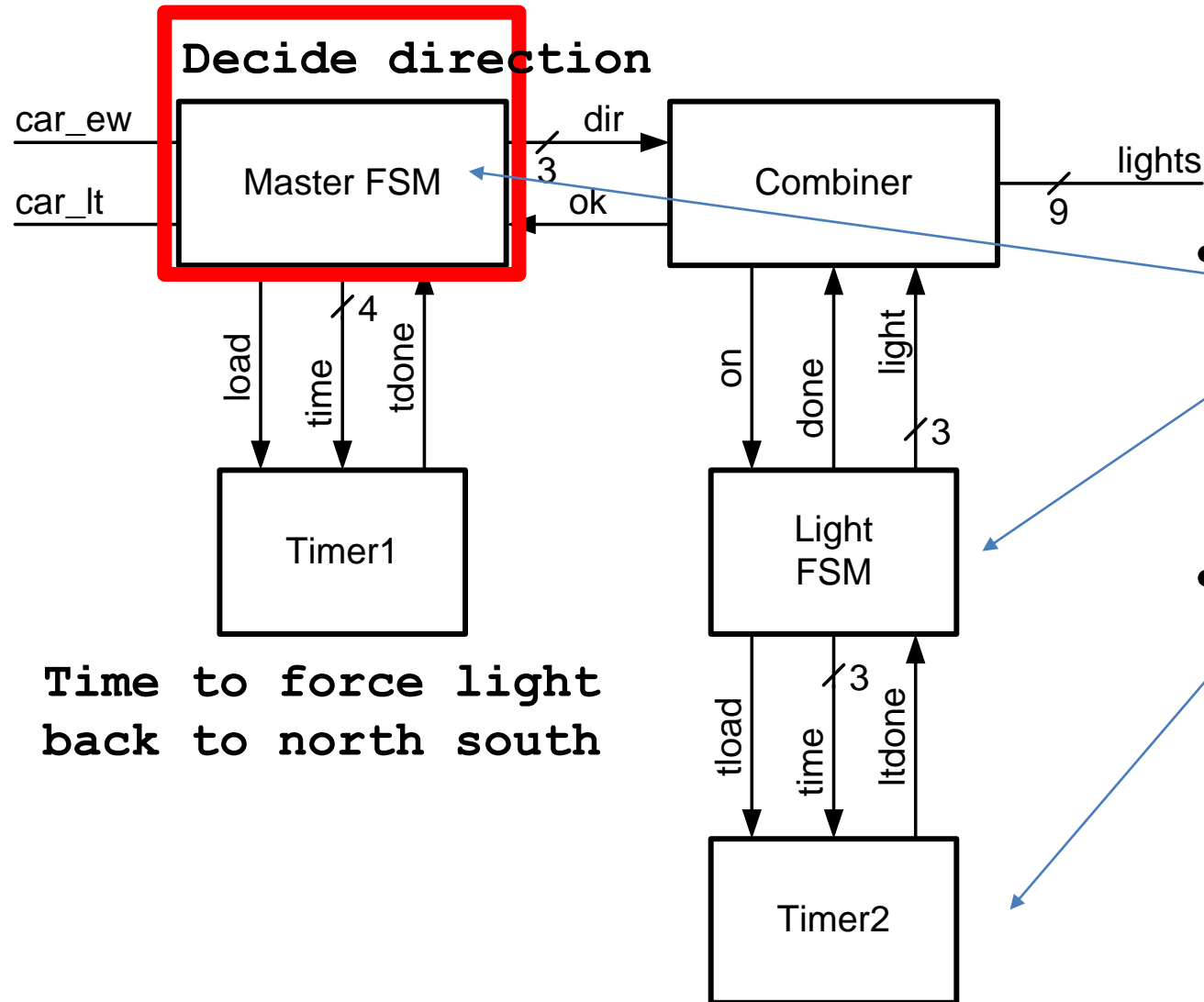

- Sequences for NS, EW, LT (3)
 - States in each sequence Yellow, Red, Green (3)
 - Time in each state 9, 5, or 4 cycles (6)
- Time remaining before return to NS (13)

Time to force light
back to north south

State diagram of master FSM

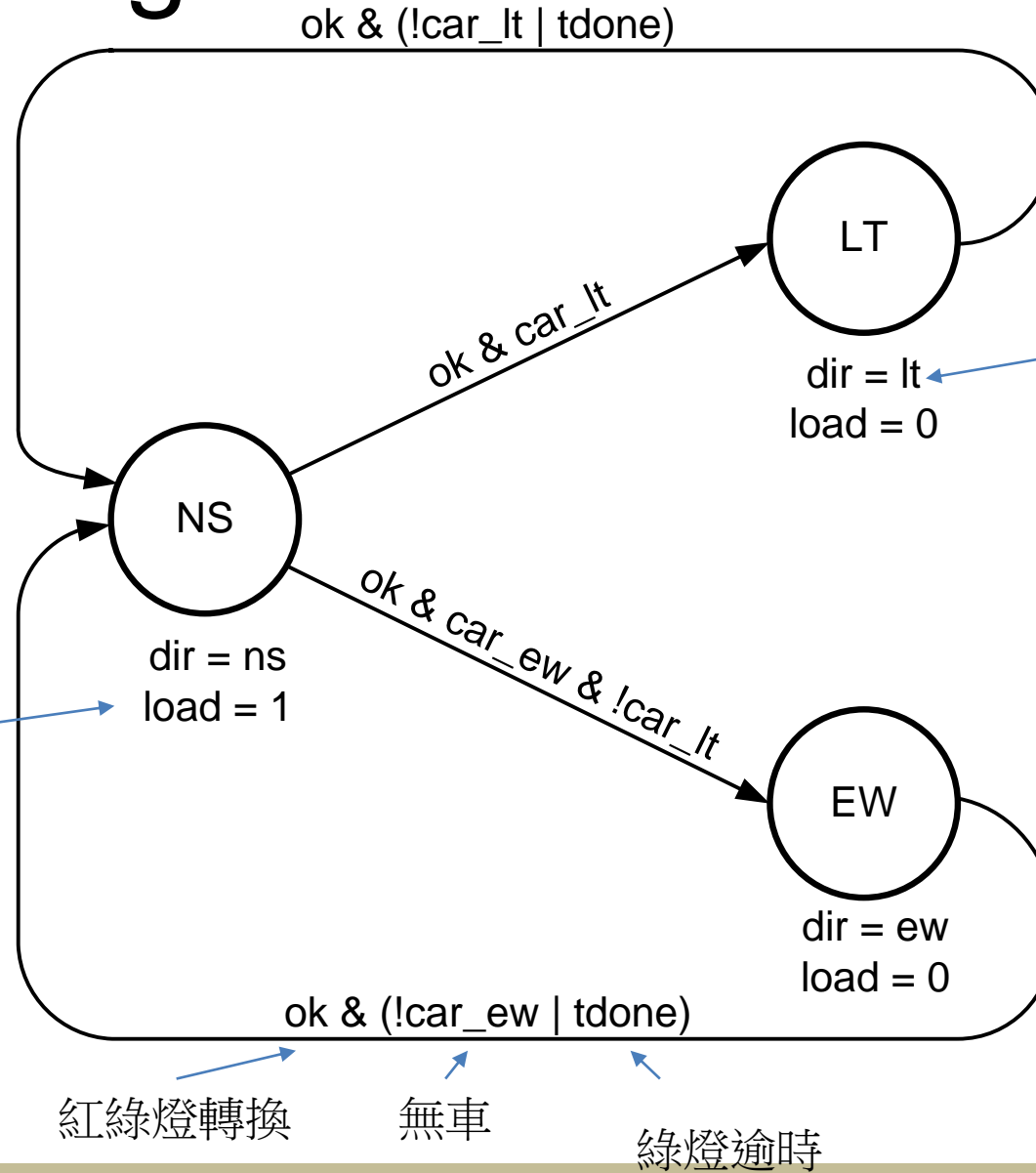

方向燈號

- Default: green light for north-south road
- If car_lt: green light for left-turn
 - If \sim car_lt & car_ew: green light for east-west road
- Green light for left-turn and east-west roads stay
 - No more cars, or
 - Green light timer expires

綠燈時間倒數

紅綠燈轉換

無車

綠燈逾時

```

//-----
//Master FSM
// car_ew - car waiting on east-west road
// car_lt - car waiting in left-turn lane
// ok      - signal that it is ok to request a new direction
// dir     - output signaling new requested direction
//-----
module TLC_Master(clk, rst, car_ew, car_lt, ok, dir) ;
    input clk, rst, car_ew, car_lt, ok ;
    output [1:0] dir ;


    wire [`MWIDTH-1:0] state, next ; // current state and next state
    reg  [`MWIDTH-1:0] next1 ;        // next state without reset
    reg  tload ;                      // timer load
    reg  [1:0] dir ;                  // direction output
    wire tdone ;                      // timer completion

    // instantiate state register
    DFF #(`MWIDTH) state_reg(clk, next, state) ;

    // instantiate timer
    Timer #(`TWIDTH) timer(clk, rst, tload, `T_EXP, tdone) ;


    always @(state or rst or car_ew or car_lt or ok or tdone) begin
        case(state)
            `M_NS: {dir, tload, next1} =
                {`M_NS, 1'b1, ok ? (car_lt ? `M_LT
                                     : (car_ew ? `M_EW : `M_NS))
                 : `M_NS} ;
            `M_EW: {dir, tload, next1} =
                {`M_EW, 1'b0, (ok & (!car_ew | tdone)) ? `M_NS : `M_EW} ;
            `M_LT: {dir, tload, next1} =
                {`M_LT, 1'b0, (ok & (!car_ew | tdone)) ? `M_NS : `M_LT} ;
            default: {dir, tload, next1} =
                {`M_LT, 1'b0, (ok & (!car_ew | tdone)) ? `M_NS : `M_LT} ;
        endcase
    end
    assign next = rst ? `M_NS : next1 ;
endmodule

```

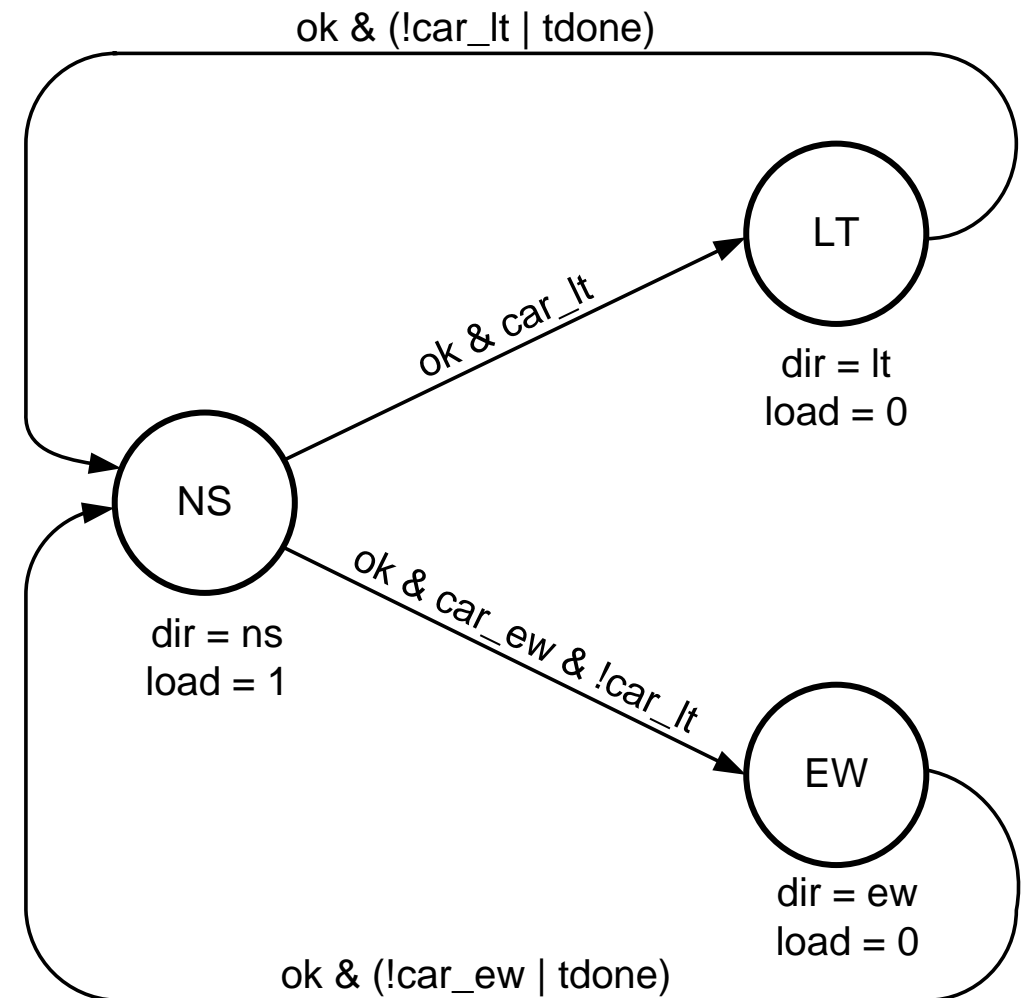

決定目前主要綠燈方向


Block diagram of factored machine

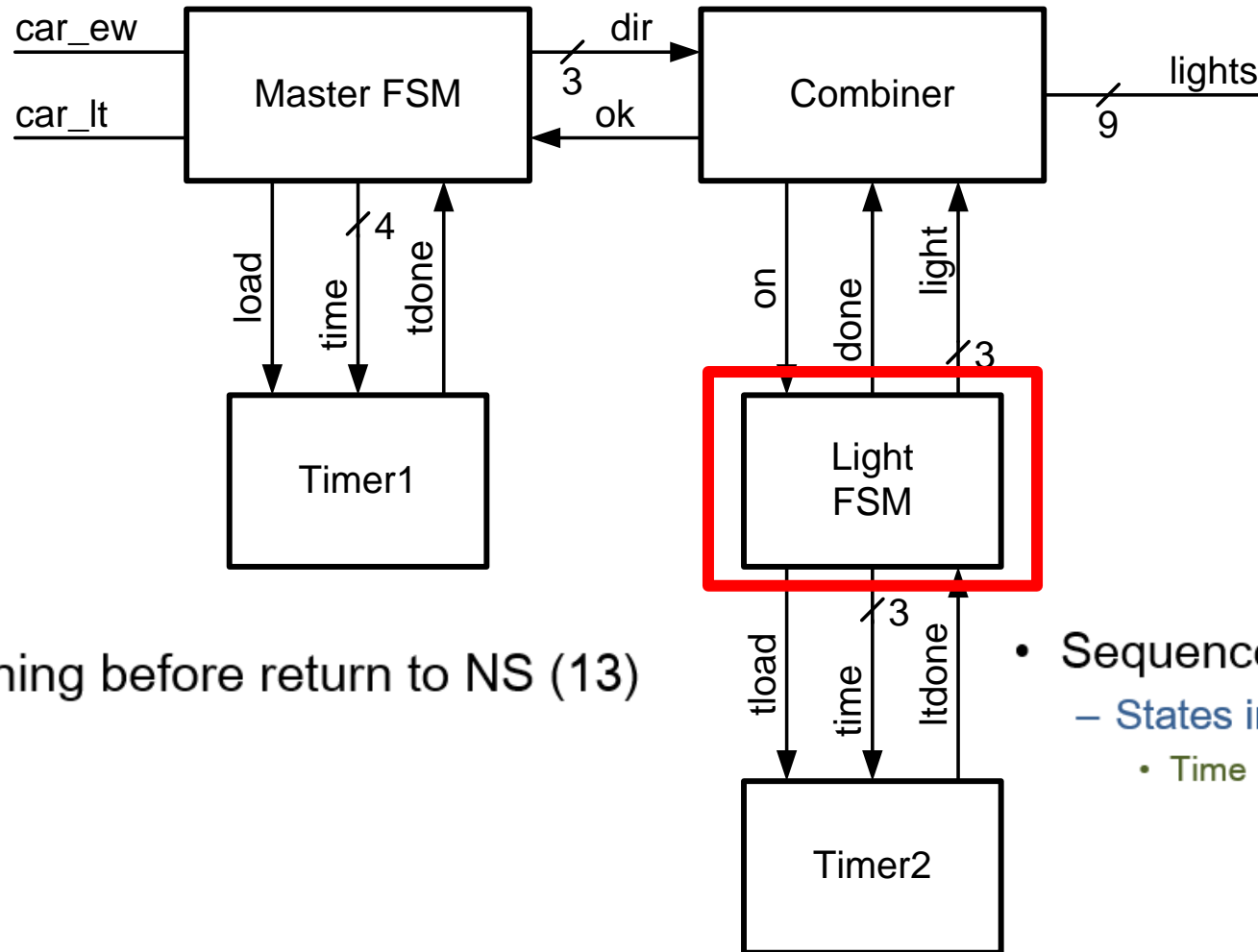

- Time remaining before return to NS (13)

- Sequences for NS, EW, LT (3)
 - States in each sequence Yellow, Red, Green (3)
 - Time in each state 9, 5, or 4 cycles (6)


State diagram of light FSM

 



- Sequences for NS, EW, LT (3)
 - States in each sequence Yellow, Red, Green (3)
 - Time in each state 9, 5, or 4 cycles (6)

On signal indicates that a green light is requested.

 Note. tdone here refers to the local timer signal in this light FSM



Light “handshake”

  

```

module TLC_Light(clk, rst, on, done, light) ;
    input clk, rst, on ;
    output done ;
    output [2:0] light ;
    reg [2:0] light ;
    reg done ;
    wire [`LWIDTH-1:0] state, next ; // current state, next state
    reg [`LWIDTH-1:0] next1 ;        // next state w/o reset
    reg tload ;
    reg [`TWIDTH-1:0] tin ;
    wire tdone ;


    // instantiate state register
    DFF #(`LWIDTH) state_reg(clk, next, state) ;

    // instantiate timer
    Timer timer(clk, rst, tload, tin, tdone) ;

    always @(state or rst or on or tdone) begin
        case(state)
            `L_RED: {tload, tin, light, done, next1} =
                {tdone & on, `T_GREEN, `RED, !tdone,
                 (tdone & on) ? `L_GREEN : `L_RED} ;
            `L_GREEN: {tload, tin, light, done, next1} =
                {tdone & !on, `T_YELLOW, `GREEN, tdone,
                 (tdone & !on) ? `L_YELLOW : `L_GREEN} ;
            `L_YELLOW: {tload, tin, light, done, next1} =
                {tdone, `T_RED, `YELLOW, 1'b1, tdone ? `L_RED : `L_YELLOW} ;
            default: {tload, tin, light, done, next1} =
                {tdone, `T_RED, `YELLOW, 1'b1, tdone ? `L_RED : `L_YELLOW} ;
        endcase
    end


    assign next = rst ? `L_RED : next1 ;
endmodule

```

 

依照timer時間變化紅綠燈
適時控制timer的倒數值，
決定紅綠燈秒數

The Combiner

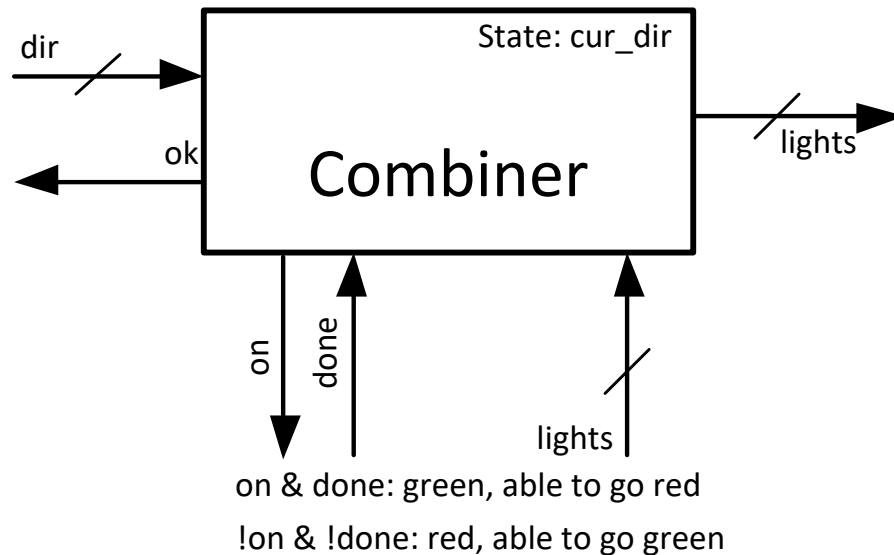

- Notify master when legal to change (green, able to go red)
 - $ok = on \ \& \ done$
- Trigger a red light when master changes direction
 - $on = (dir == cur_dir)$
- Update the current direction to input **dir** when all lights are red and able to go green
 - $next_dir = (!on \ \& \ !done) ?$
 $dir : cur_dir$
- Trigger a green light when **cur_dir** has been updated
 - $on = (dir == cur_dir)$
- Output red lights for the two directions that are not **cur_dir**

```

//-----
// Combiner -
//   dir - direction request from master FSM
//   ok  - acknowledge to master FSM
//   lights - 9-bits to control traffic lights {NS,EW,LT}
//-----
module TLC_Combiner(clk, rst, dir, ok , lights) ;
    input clk, rst ;
    input [1:0] dir ;
    output ok ;
    output [8:0] lights ;
    wire done ;
    wire [2:0] light ;
    reg [8:0] lights ;
    wire [1:0] cur_dir ;

    // current direction register
    DFF #(2) dir_reg(clk, next_dir, cur_dir) ;
    // light FSM
    TLC_Light lt(clk, rst, on, done, light) ;
    // request green from light FSM until direction changes
    wire on = (cur_dir == dir) ;
    // update direction when light FSM has made lights red
    wire [1:0] next_dir = rst ? 2'b0 : ((!on & !done) ? dir : cur_dir) ;
    // ok to take another change when light FSM is done
    wire ok = on & done ;

    // combine cur_dir and light to get lights
    always @(cur_dir or light) begin
        case(cur_dir)
            `M_NS: lights = {light, `RED, `RED} ;
            `M_EW: lights = {`RED, light, `RED} ;
            `M_LT: lights = {`RED, `RED, light} ;
            default: lights = {`RED, `RED, `RED} ;
        endcase
    end
endmodule

```

選到的方向，根據規則變化紅綠燈
其它沒選到的都紅燈

VLSI Signal Processing Lab.



Summary

- Factoring state machines
 - Separate state into multiple ‘orthogonal’ state variables
 - Each is simpler to handle (fewer states)
 - Total number of states is product of numbers of sub-states
 - “Factors out” repetitive sequences
 - Hierarchical structure