

Digital Circuits and Systems

Lecture 13 Interfaces, Interconnect, and Memory

Tian Sheuan Chang


資料要從一個模組傳到另一個模組，要如何溝通，告訴對方這是有效的資料？

Outline [Dally. Ch. 22. 24. 25]

- Interface Timing: sequencing the transfer of data
 - 安排資料怎麼傳
 - 從簡單到複雜的方式
- Interconnect
 - 實體電路的樣子
 - 從簡單到複雜的方式
- Memory
 - 先存起來，慢慢再用

Recap: System on a Chip (SOC)


Source: ARM

 

Recap: Breakdown of Modern SOC Design

- Core
 - CPU/DSPs/GPUs
 - Hardware accelerators (AI engine/video codec/MP3 codec)
 - Complex data path + FSMs (pipeline/parallel)
- Bus
 - Connect core and peripherals
 - MUX/arbiters
- Peripheral
 - Interface from/to the external
 - speech/audio, camera/display, I2S/I2C, GPIO
 - Serial to parallel, parallel to serial + FSM

Recap: An Example AMBA System

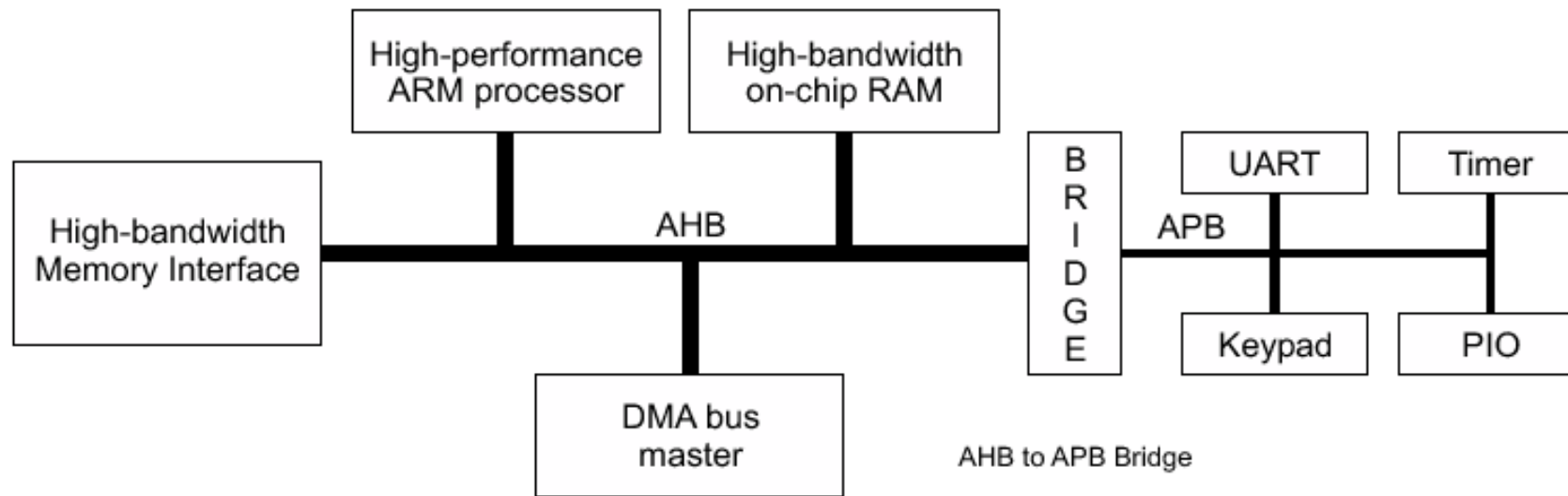

AMBA Advanced High-performance Bus (AHB)


- * High performance
- * Pipelined operation
- * Burst transfers
- * Multiple bus masters
- * Split transactions

AMBA Advanced Peripheral Bus (APB)

- * Low power
- * Latched address and control
- * Simple interface
- * Suitable for many peripherals


Recap: From C Array to Memory Access

Memory [125] = 0

 

Memory Write Operation



CPU = Memory [125]

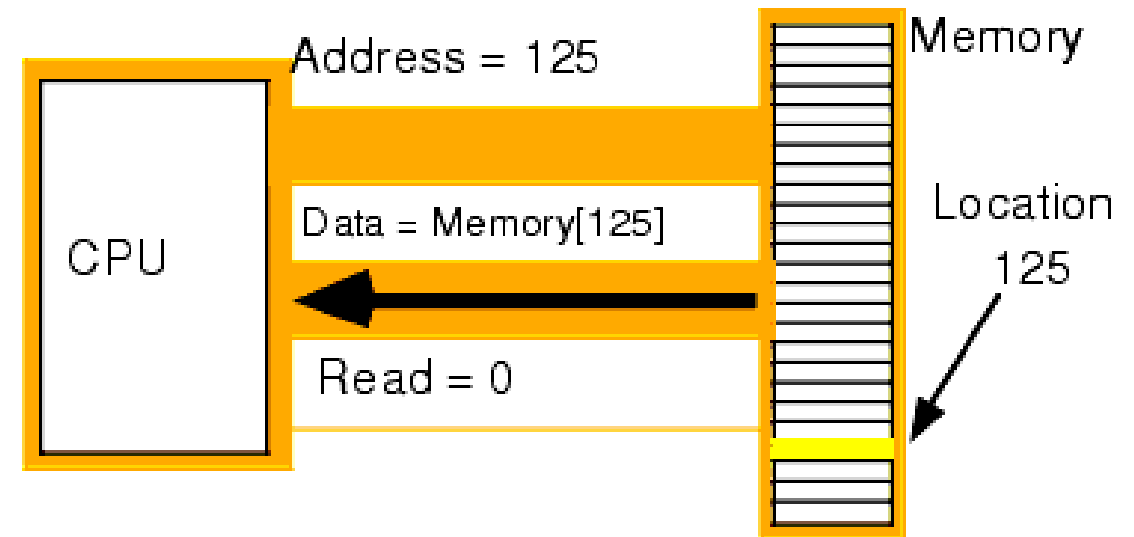

Memory Read Operation

Recap: How CPU access these I/O interface?

 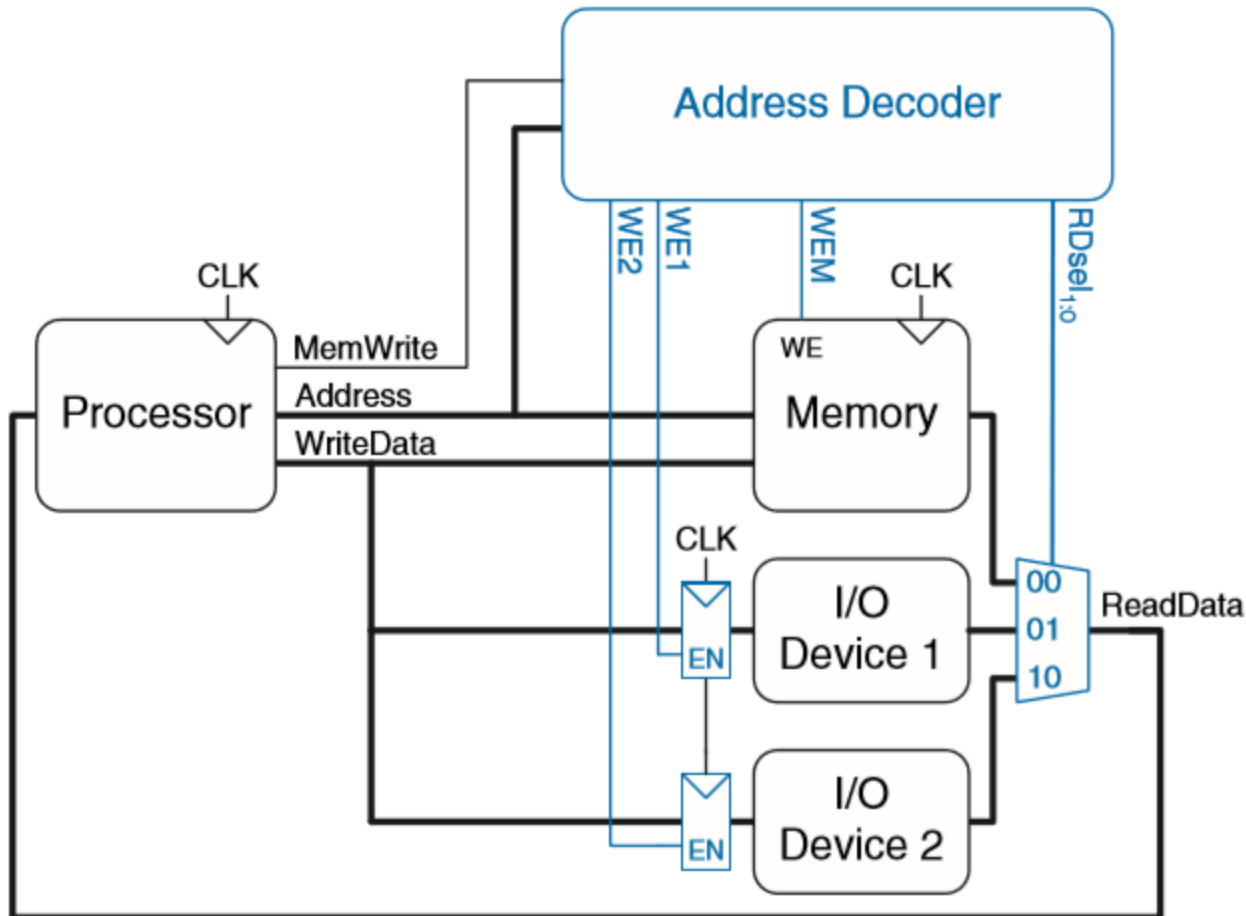
- Memory mapped I/O (treat other components as memory)



INTERFACE TIMING


Interface Timing

 - How do you pass data from one module to another?
 - Open loop: 資料送了就送了，有沒有收到是你家的事，繼續送下一筆
 - Flow control: 資料送了，要有通關訊號 或 回條，才送下一筆
 - Serialized: 通道狹窄，一次只能傳一個bit
 - 比較複雜的通常都是晶片外面溝通用，或大模組間使用，因為不確定高



簡單的方式

Always Valid Timing

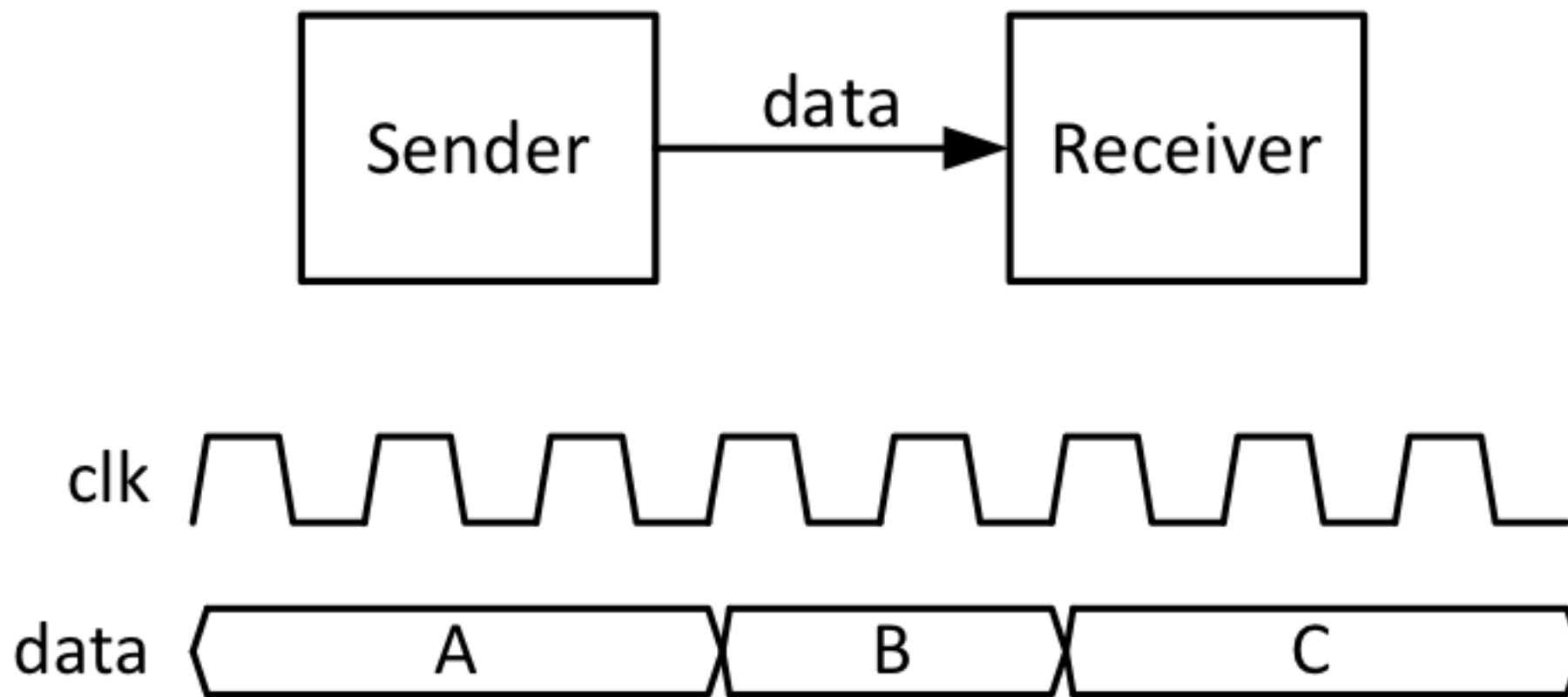


(通常都是這種，晶片內部用較多，確定性高)

Data is valid every cycle, and can be sampled by the receiver at any time

(c) 2005-2012 W. J. Dally

簡單的方式

Periodically Valid Timing

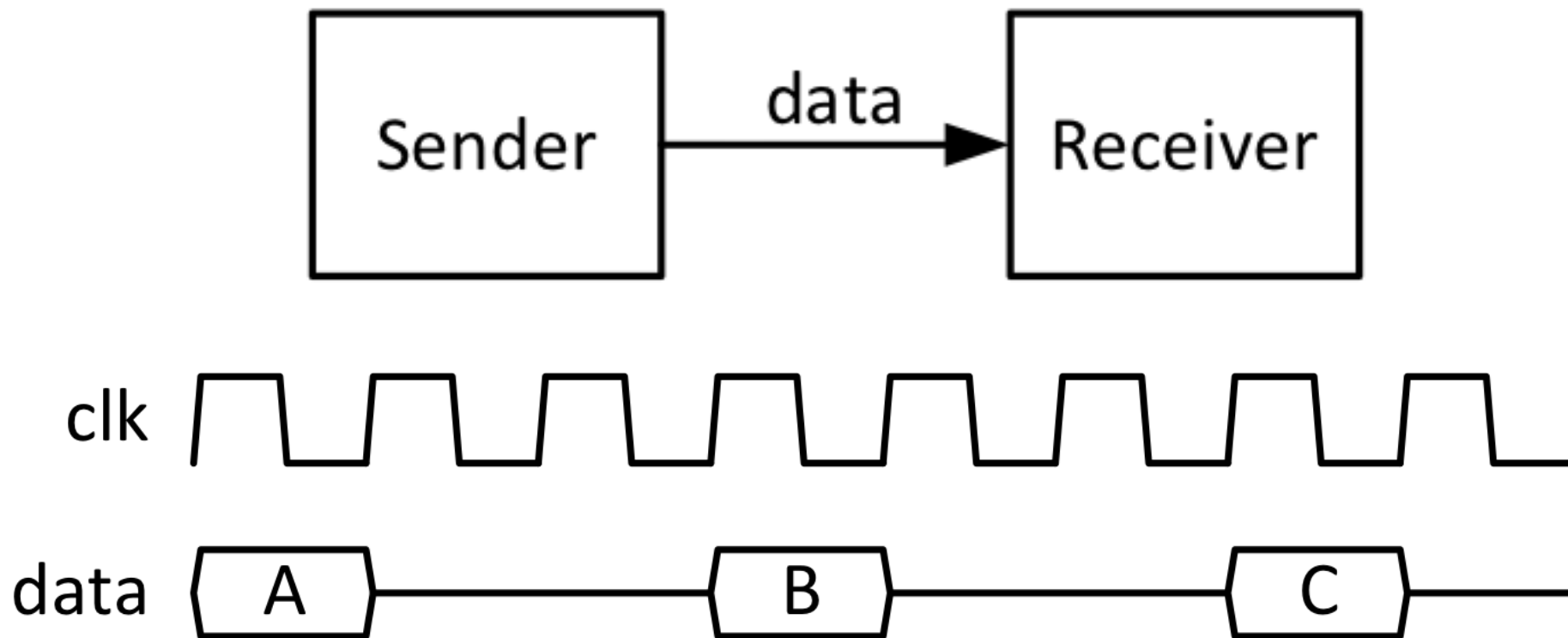


通常會有一個`data_valid` 訊號，表示資料在`data_valid == 1` 那段時間有效，可以讀，規則時就省略不規則出現會需要明白此訊號表示

No flow control, and values cannot be dropped or repeated

Need flow control to move the valid signal across clock domain


複雜的方式

Flow Control: ready-valid flow

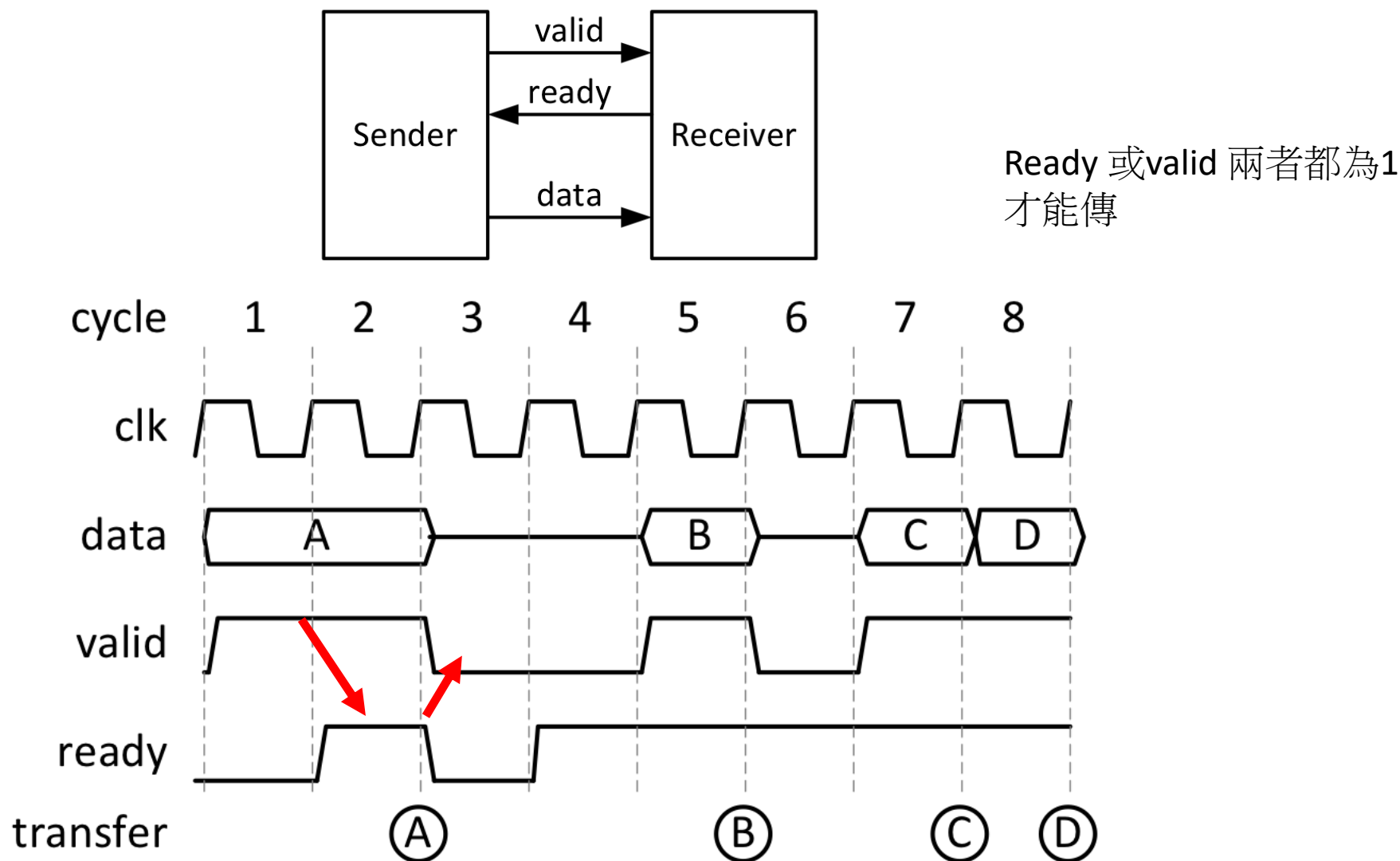


Flow-control

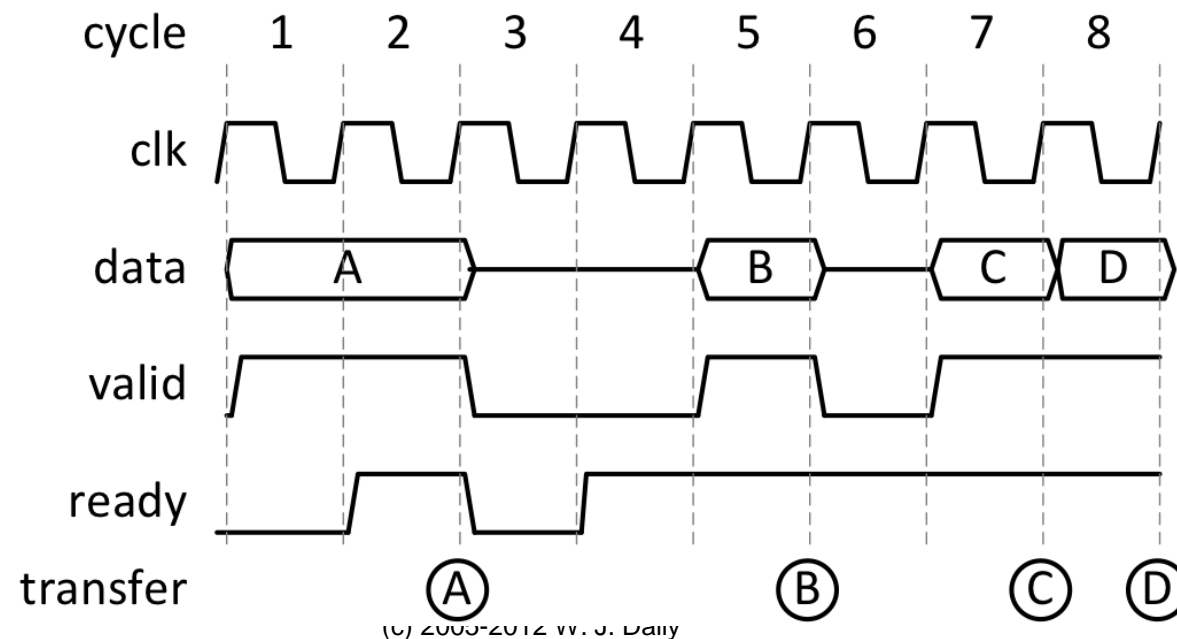- Valid – Tx has data available 傳送端資料是有效的
- Ready – Rx able to take data 通關訊號, 接收端可以收資料
- 特例
 - Push flow control – assume Rx always Ready
 - Pull flow control – assume Tx always Valid



複雜的方式 Serialization: USB, SATA, I²C, I²S

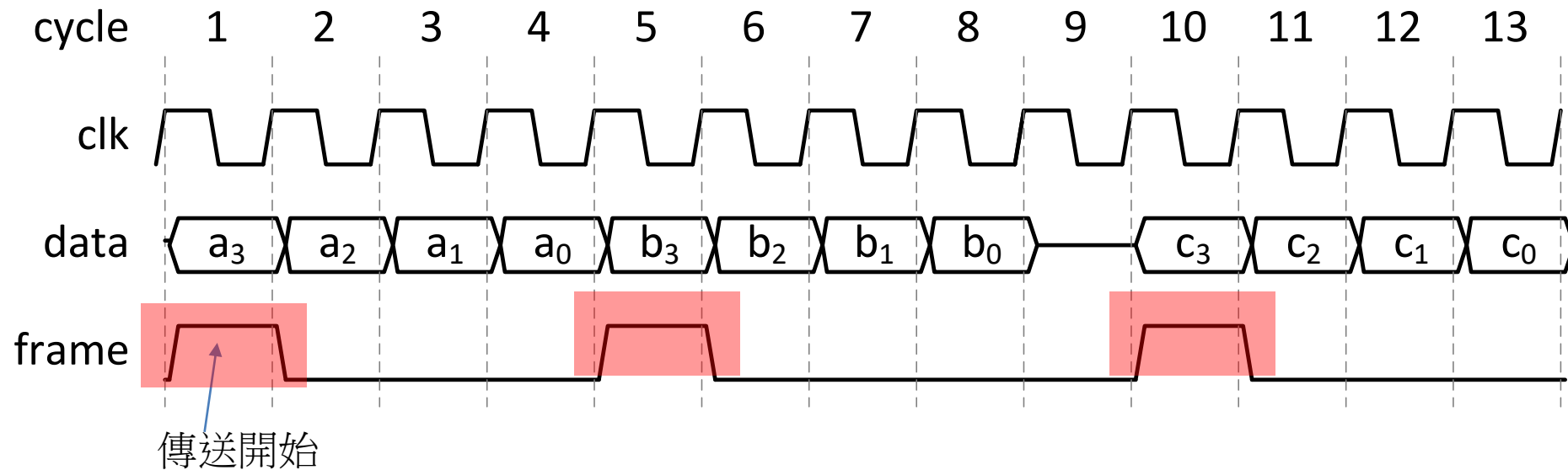


Frame signals start of new serial frame (in this case 4 words)

Flow control can be **at frame granularity** or **word granularity**

高頻或介面接腳數量有限狀況時，會用這個方法

Serialization with word granularity FC

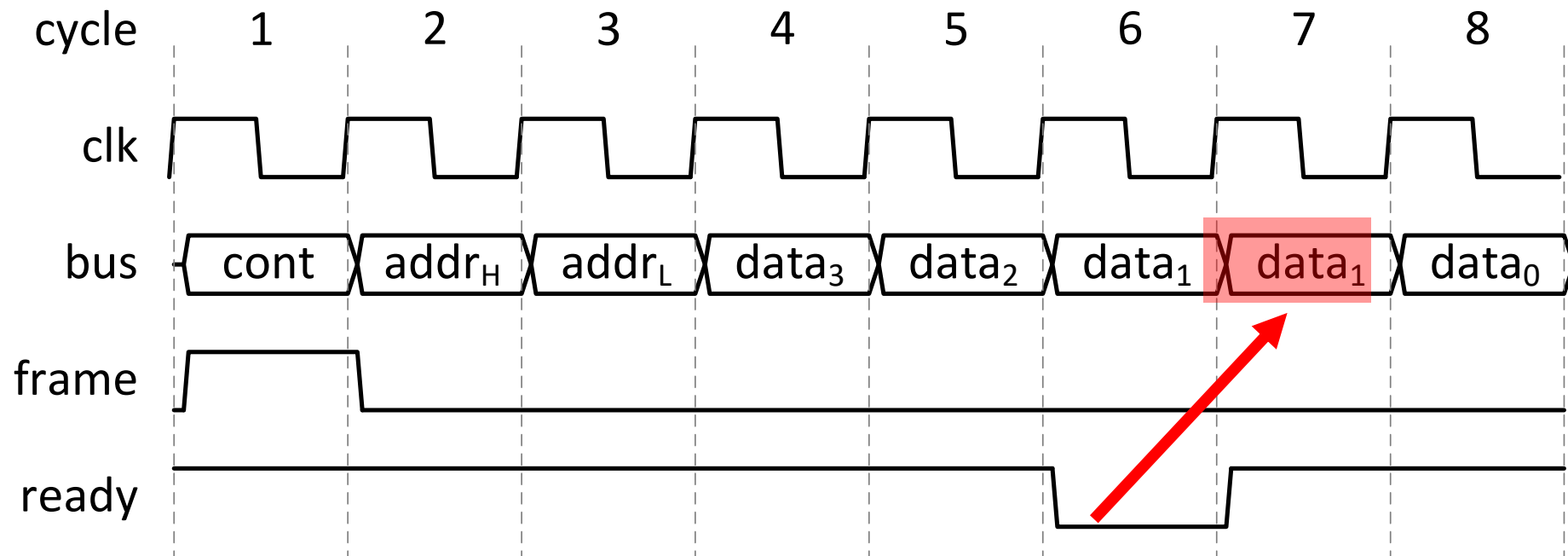


不能接收，資料要再延續下去

常見介面訊號

- Control
 - Read/write, sequential, non-sequential
- Address
 - 讀寫位置
 - 特別是用於bus or memory
- Data
 - 有時候會再細分成不同field，方便使用

An Example AMBA System

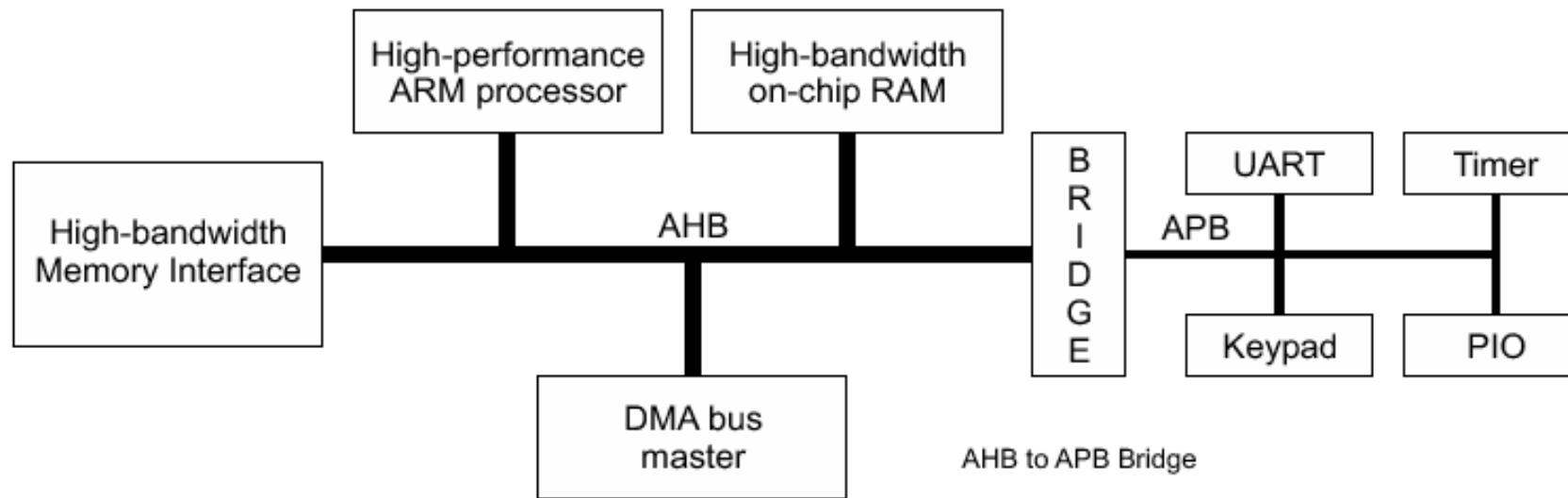


AMBA Advanced High-performance Bus (AHB)

- * High performance
- * Pipelined operation
- * Burst transfers
- * Multiple bus masters
- * Split transactions

AMBA Advanced Peripheral Bus (APB)

- * Low power
- * Latched address and control
- * Simple interface
- * Suitable for many peripherals


AHB Interconnect

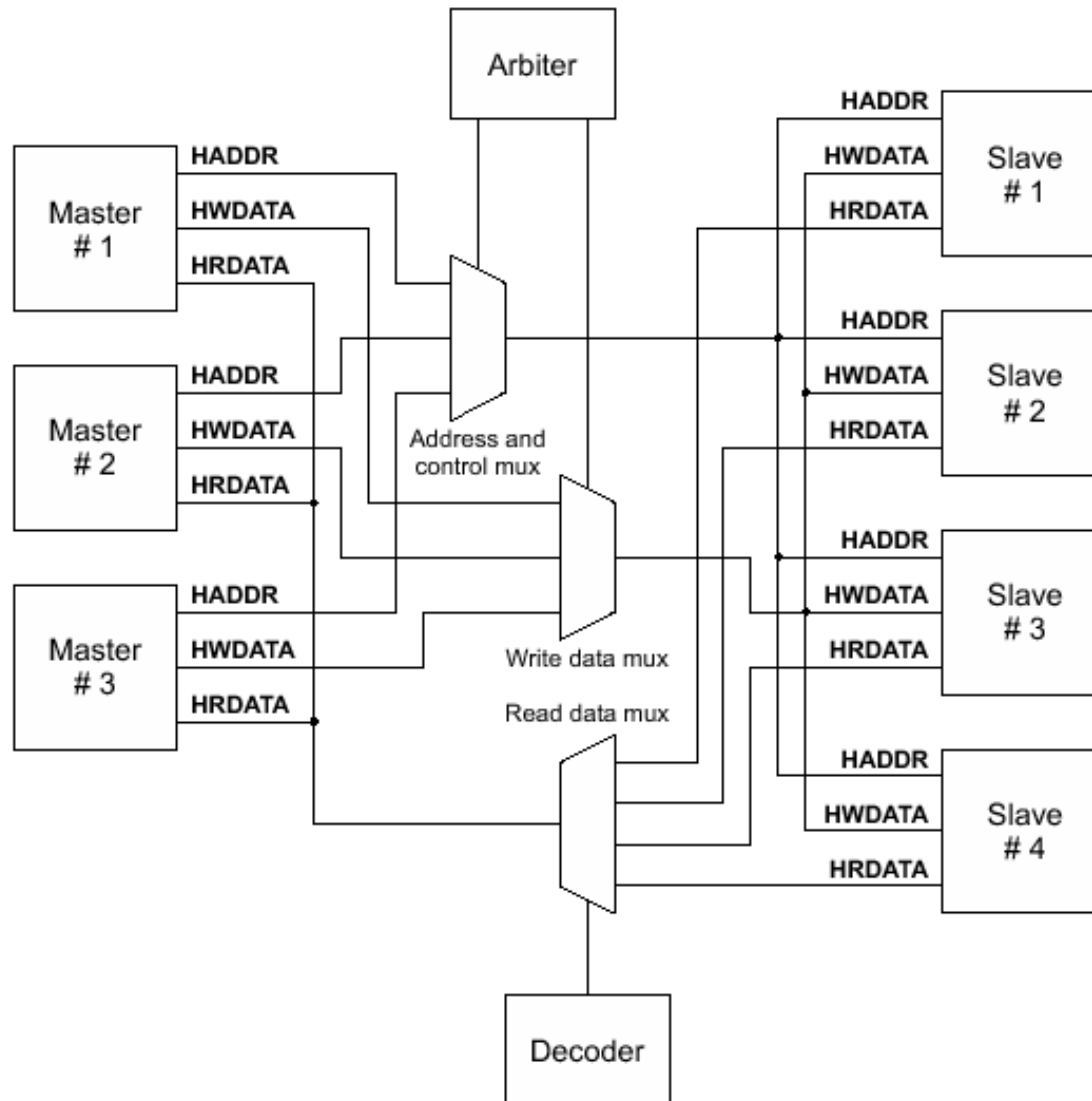

Basic components:

- Master
- Slave
- Arbiter
- Decoder
- Mux

AHB Simple Transfer

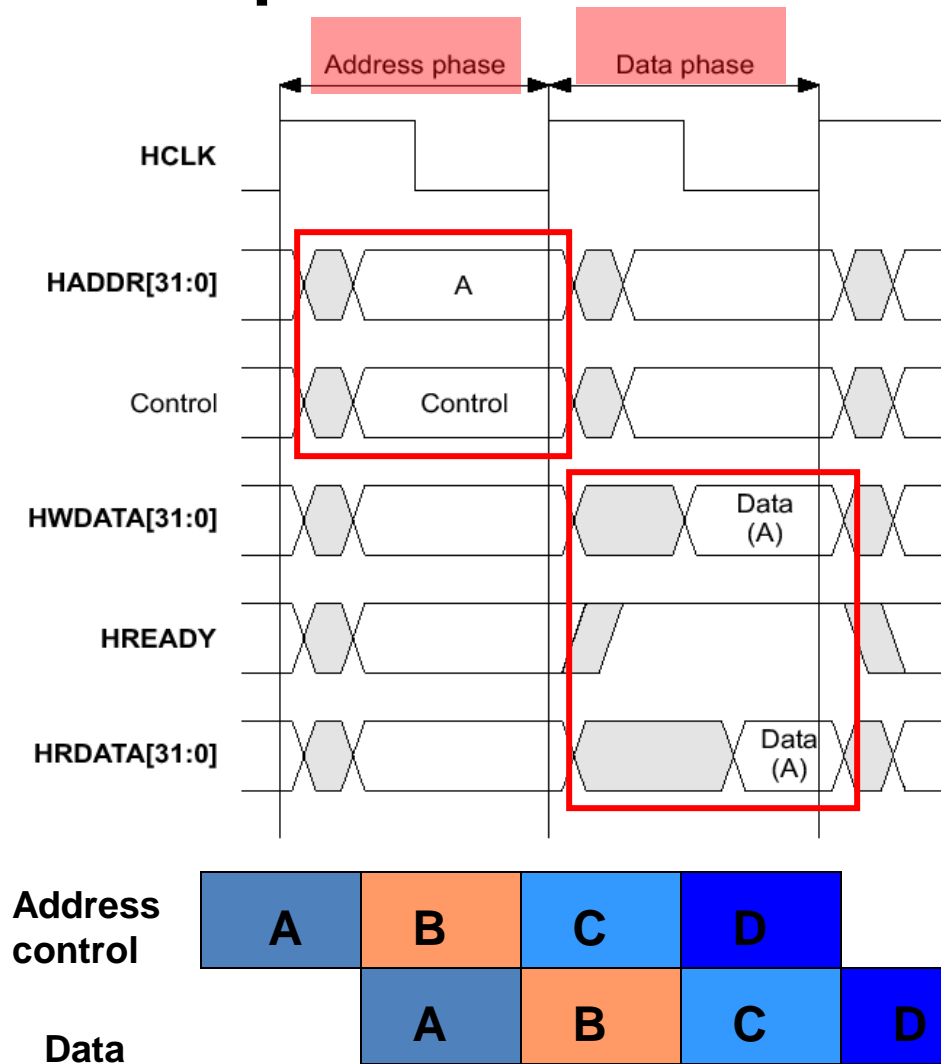


- **HCLK**: Reference for all AHB activity
- **HADDR**: 32 bit Address Bus
- **HWRITE**: Read/Write cycle
- **HWDATA**: Write Data Bus
- **HREADY**: Transfer complete response
- **HRDATA**: Read Data Bus

Two phases to complete an access as the pipeline



Address phase: lasts only a single cycle
Data phase: can be stretched for several cycles by slave

AHB Transfer with Wait States

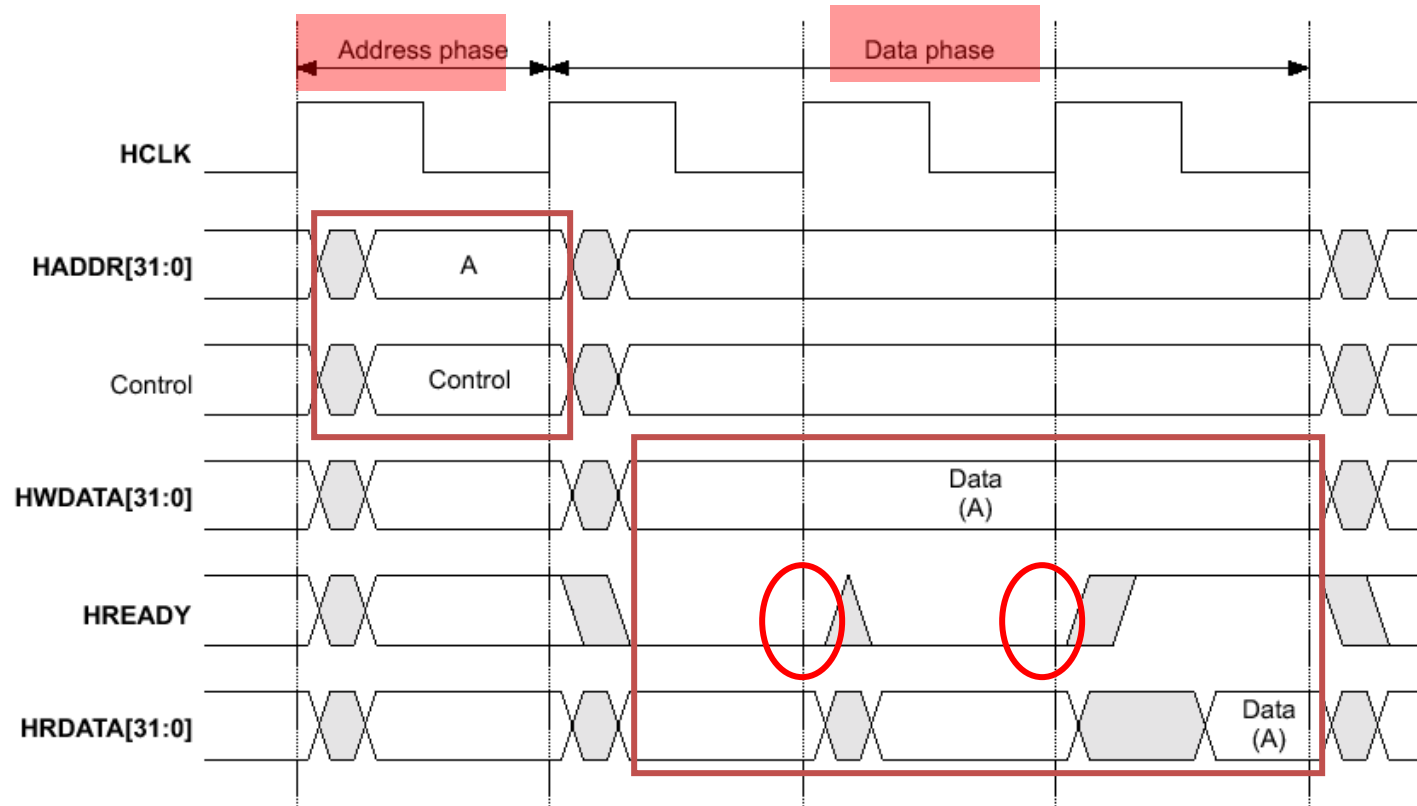

- * Access is stretched by slave which keep HREADY deassert
- * It is recommended, but not mandatory, that slave do not insert more than 16 wait states


Multiple Transfers

 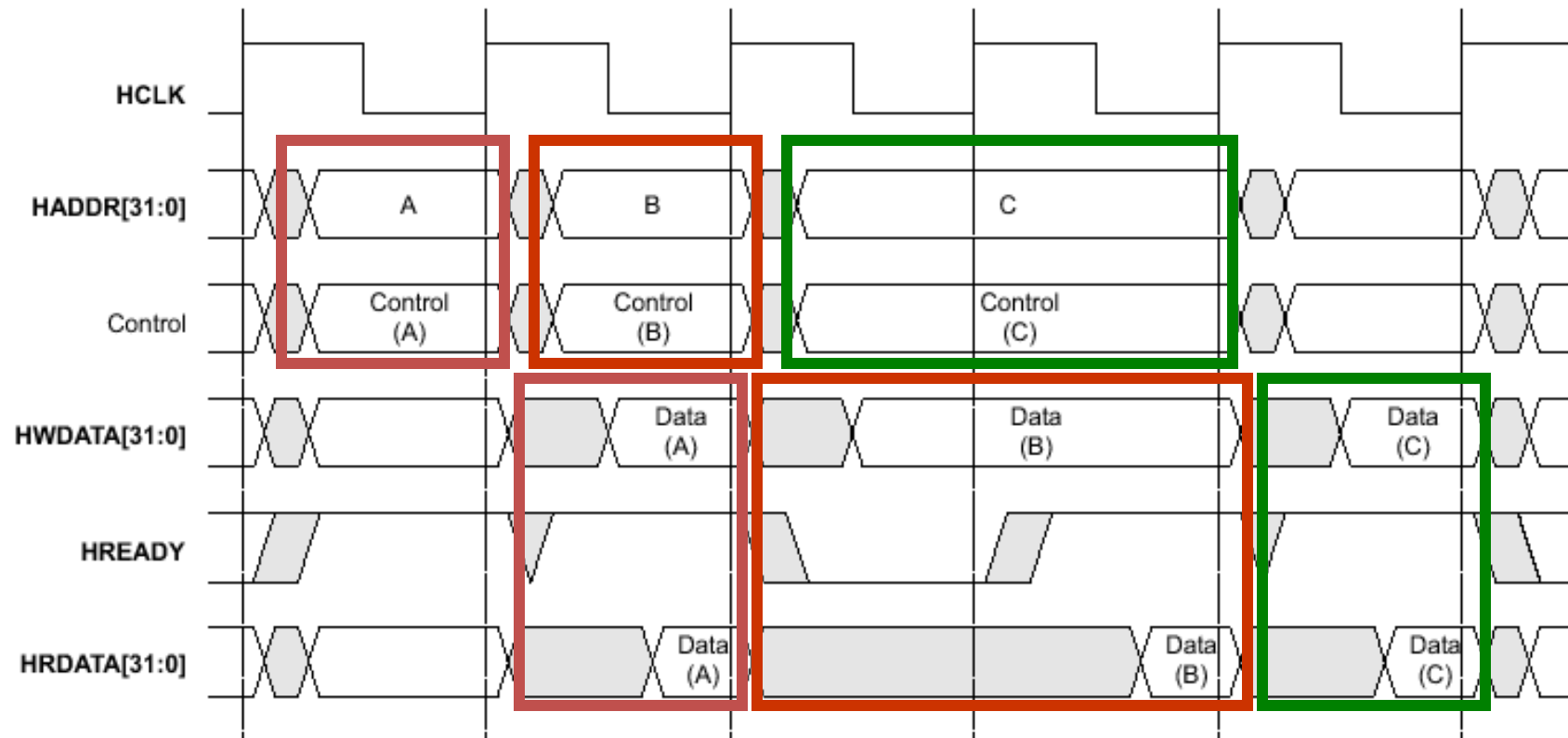

* Address phase of **C** is stretched because of stretched data phase of **B**


INTERCONNECTION

Interconnect 不只是一對一連接時，還能怎麼做？

 

- Many clients need to communicate
- Ad-hoc point-to-point wiring or shared interconnect
- Like a telephone exchange

1. Bus:

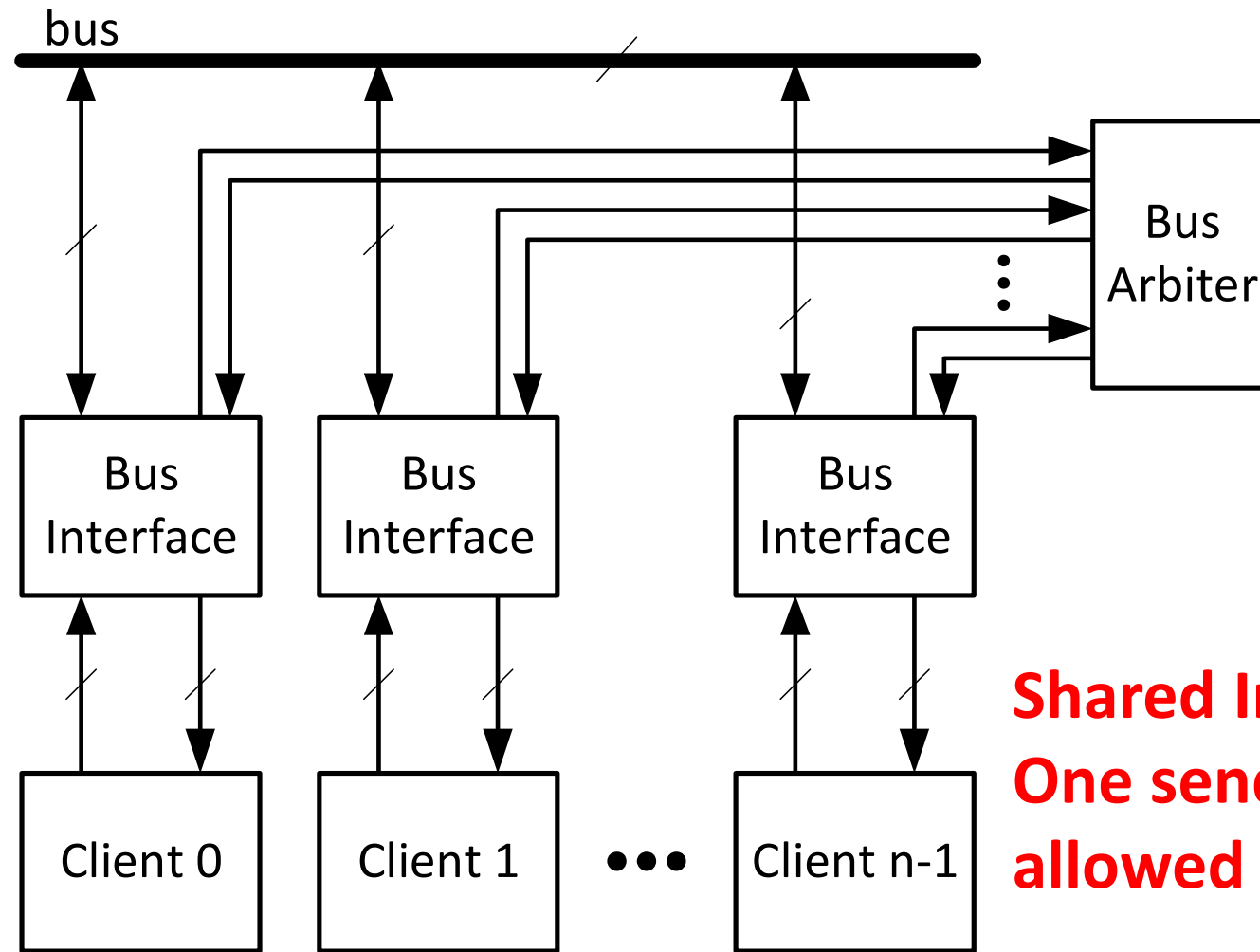


Shared Interconnect
One sender/receiver pair
allowed

Verilog for a simple bus interface

```
// Combinational Bus Interface
// t (transmit) and r (receive) in signal names are from the perspective of the bus
module BusInt(cr_valid, cr_ready, cr_addr, cr_data, // bus rx - to the bus
              ct_valid, ct_data,                  // bus tx - from the bus
              br_addr, br_data, br_valid,          // to the bus
              bt_addr, bt_data, bt_valid,          // from the bus
              arb_req, arb_grant,                  // the arbiter
              my_addr) ;                          // address of this interface

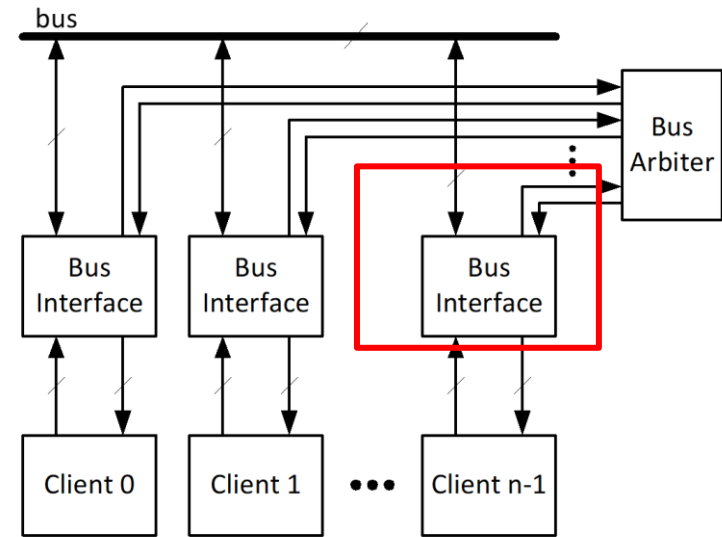parameter aw = 2 ; // address width
parameter dw = 4 ; // data width
input  cr_valid, arb_grant, bt_valid ;
output cr_ready, ct_valid, arb_req, br_valid ;
input  [aw-1:0] cr_addr, bt_addr, my_addr ;
output [aw-1:0] br_addr ;
input  [dw-1:0] cr_data , bt_data ;
output [dw-1:0] br_data, ct_data ;
```



```


// arbitration
wire arb_req = cr_valid ; //client data valid
wire cr_ready = arb_grant ;//client ready

// bus drive
// assumes bus ORs these signals with those from other interfaces
wire br_valid = arb_grant ; //client get grant to send data
wire [aw-1:0] br_addr = arb_grant ? cr_addr : 0 ; //address
wire [dw-1:0] br_data = arb_grant ? cr_data : 0 ; //data

// bus receive
wire ct_valid = bt_valid & (bt_addr == my_addr) ; //if bus address==myaddr,
wire [dw-1:0] ct_data = bt_data ;
endmodule


```

2. Crossbar Switch:

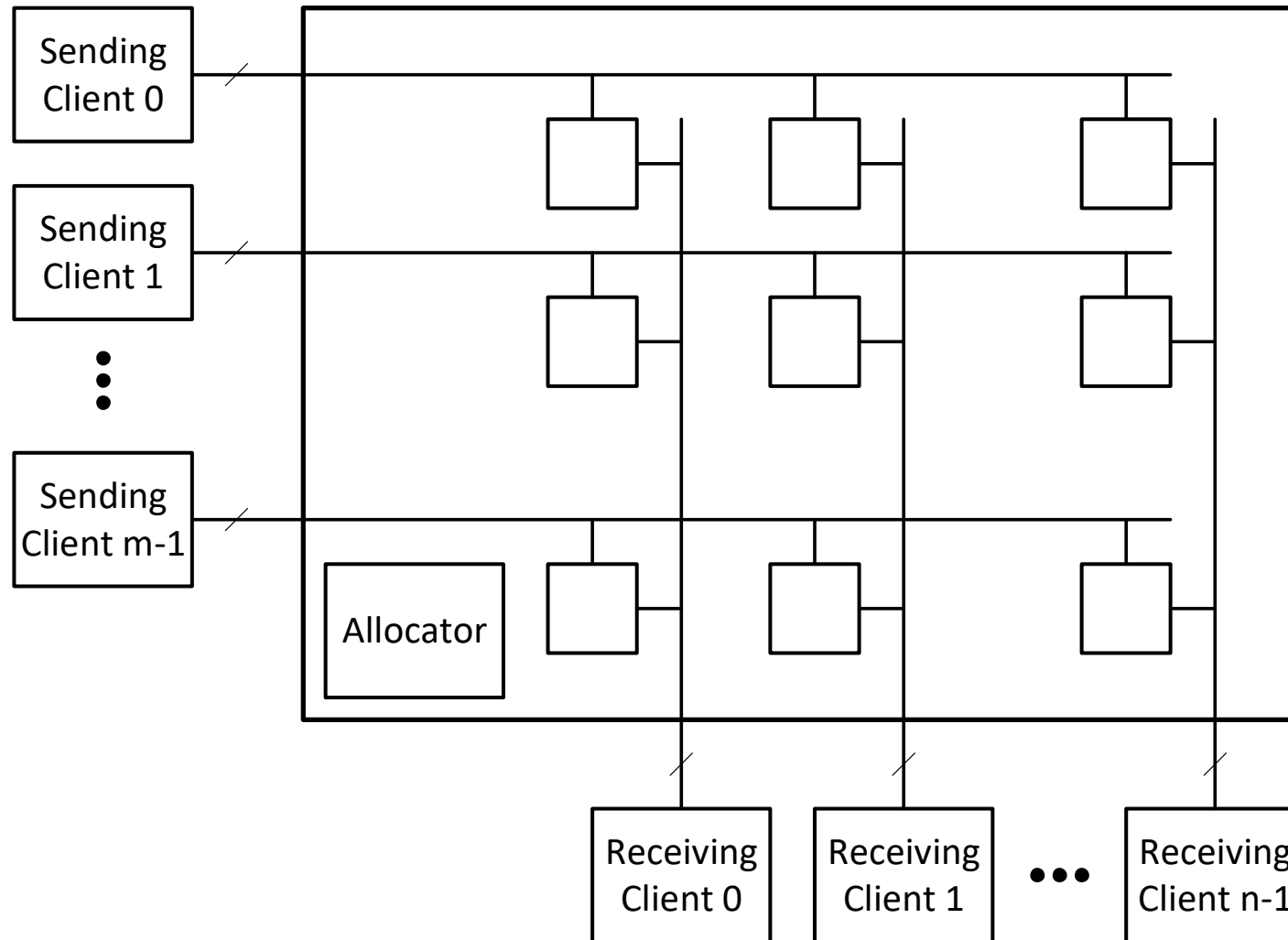


全連接型態
可同時多個傳送
只要目的不同
Multiple sender/receiver pairs

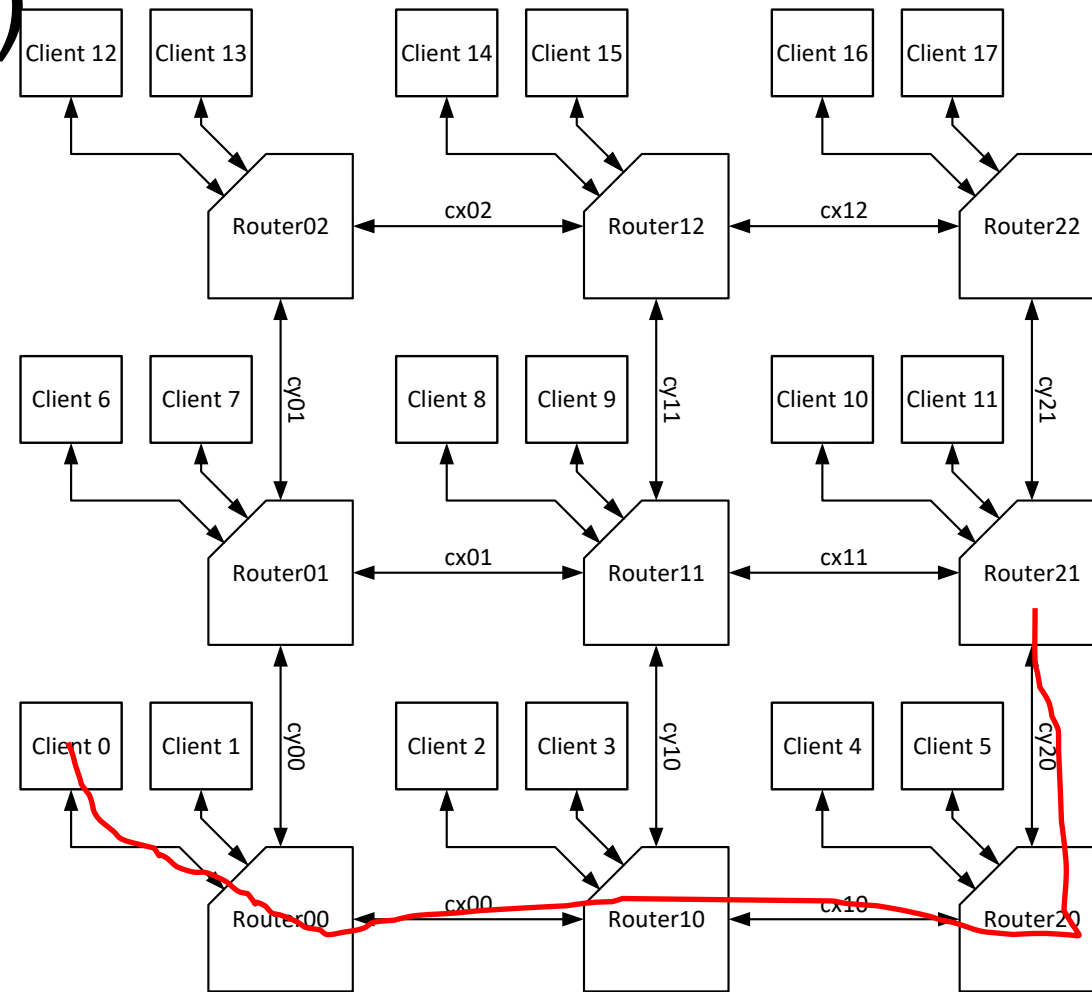3. Interconnection Networks (Network on Chip: NoC)



網路型
可以容忍更長時間延遲

Interconnection Networks

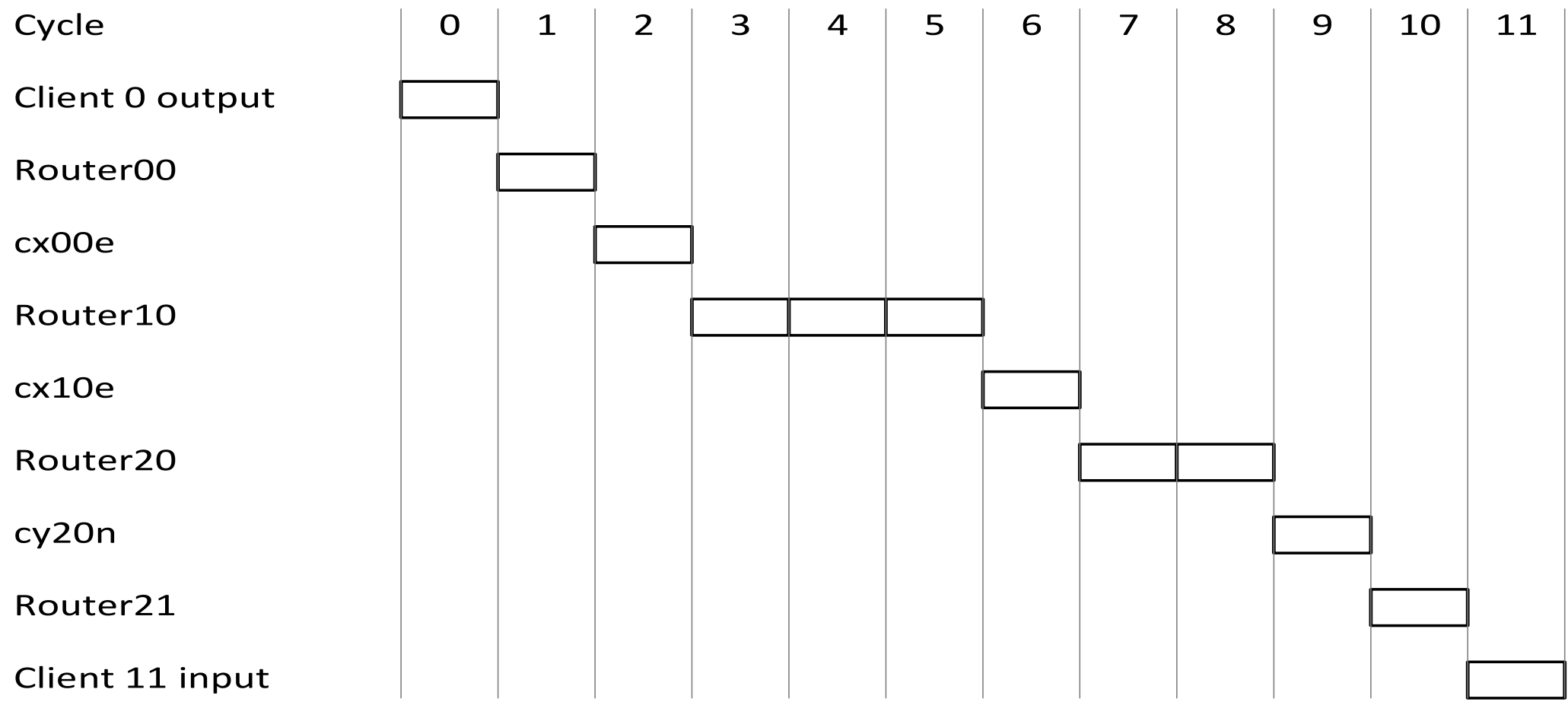


What factors determine which interconnect solution you pick?

- Bandwidth scalability
 - NoC > crossbar > bus
- Cost
 - Bus < crossbar < NoC

MEMORY

Memory

 


Capacity

Bandwidth


Latency

Granularity


SRAM

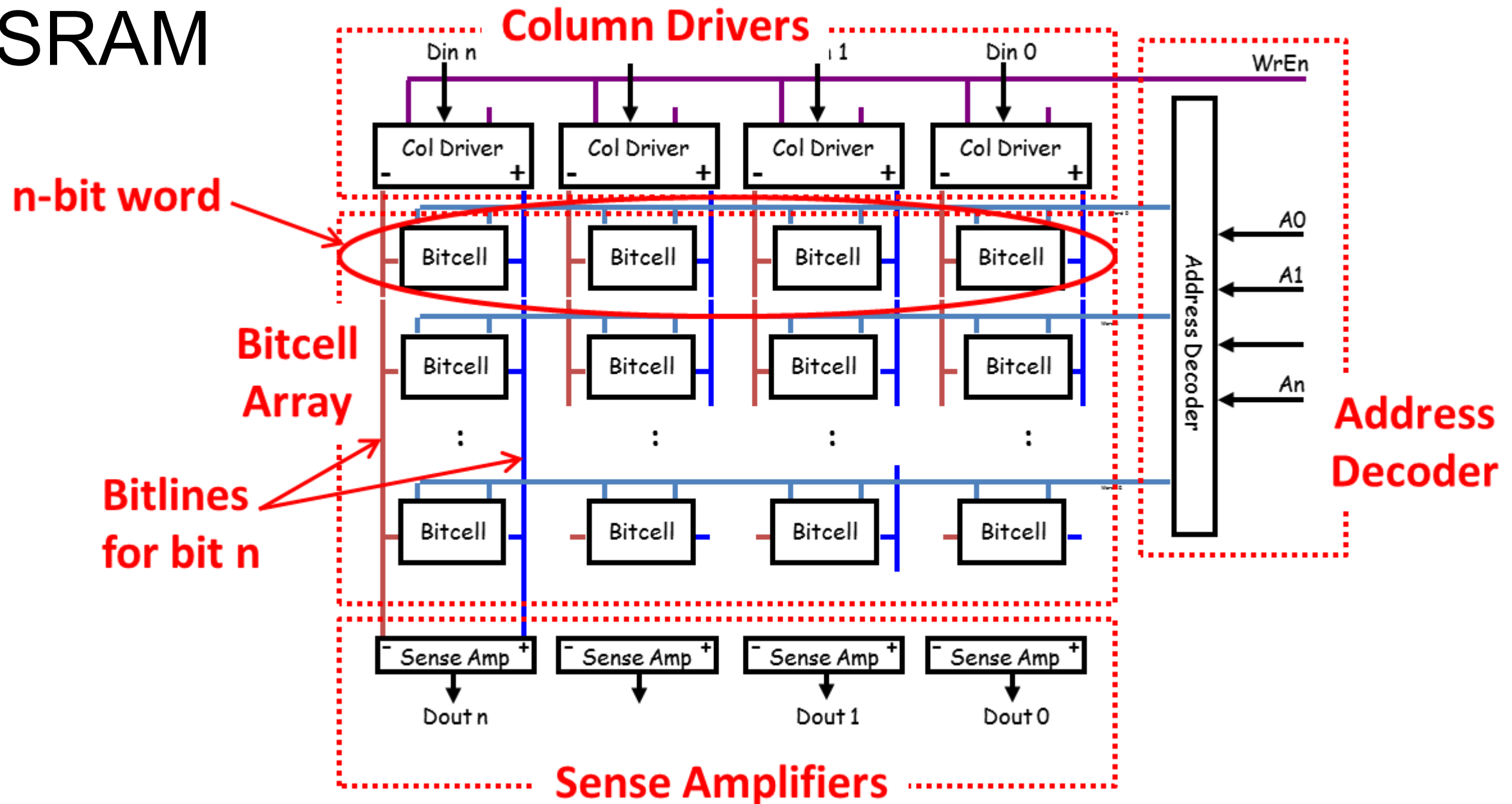

SRAM Primitive

 

DRAM Primitive

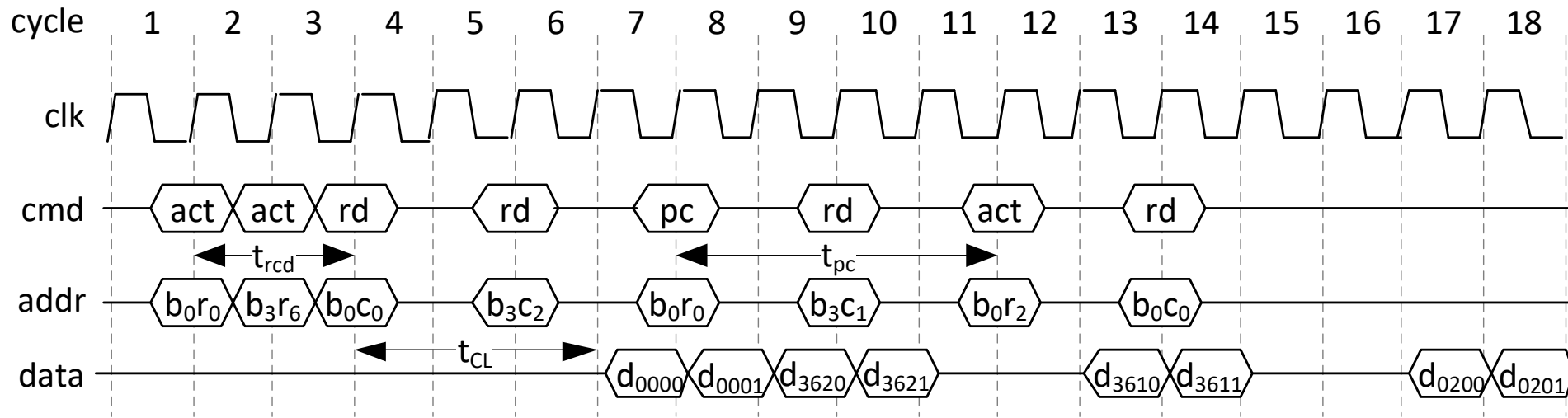


Address is split into Bank, row, column

三步驟存取: bank/row activation, column access, precharge


同一bank, changed to 不同row要先precharge

DRAM Operation

 


**如果一塊MEMORY大小不夠或
BANDWIDTH輸出入頻寬不夠，那怎麼辦？
一塊不夠，那就兩塊，或更多塊**

增加容量: Bit-Slicing

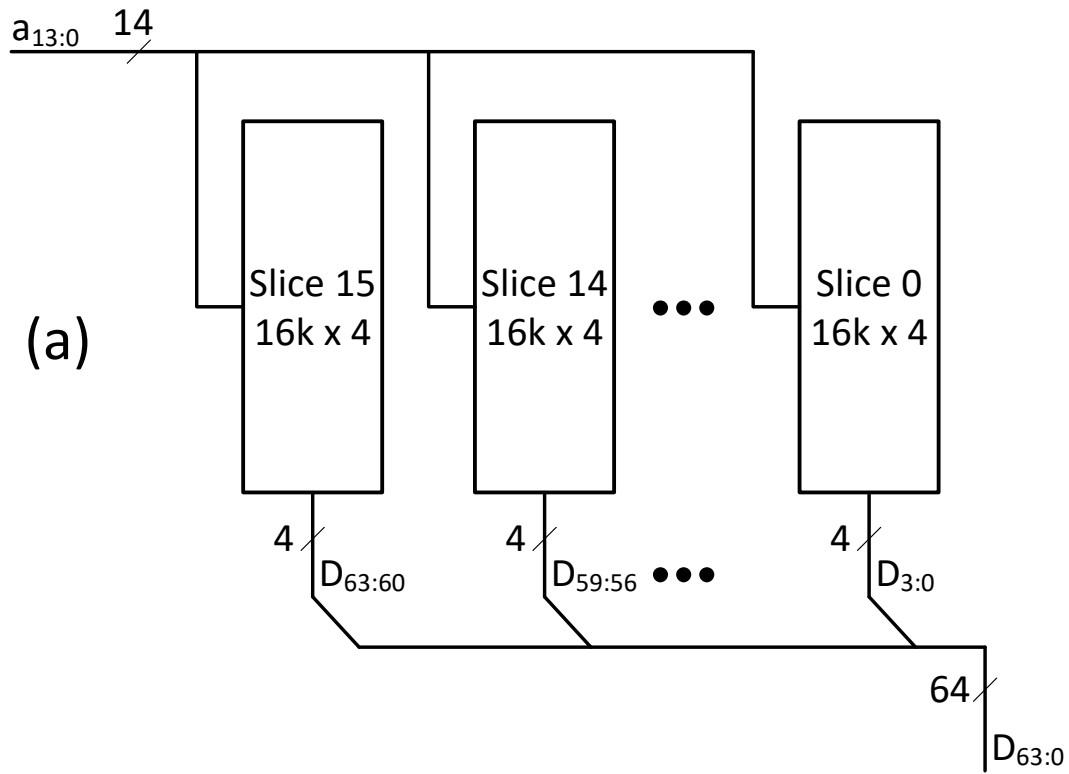


輸出入bitwidth可以增加
 $4\text{bit} \times 16 \Rightarrow 64\text{bit}$

增加容量: Banking

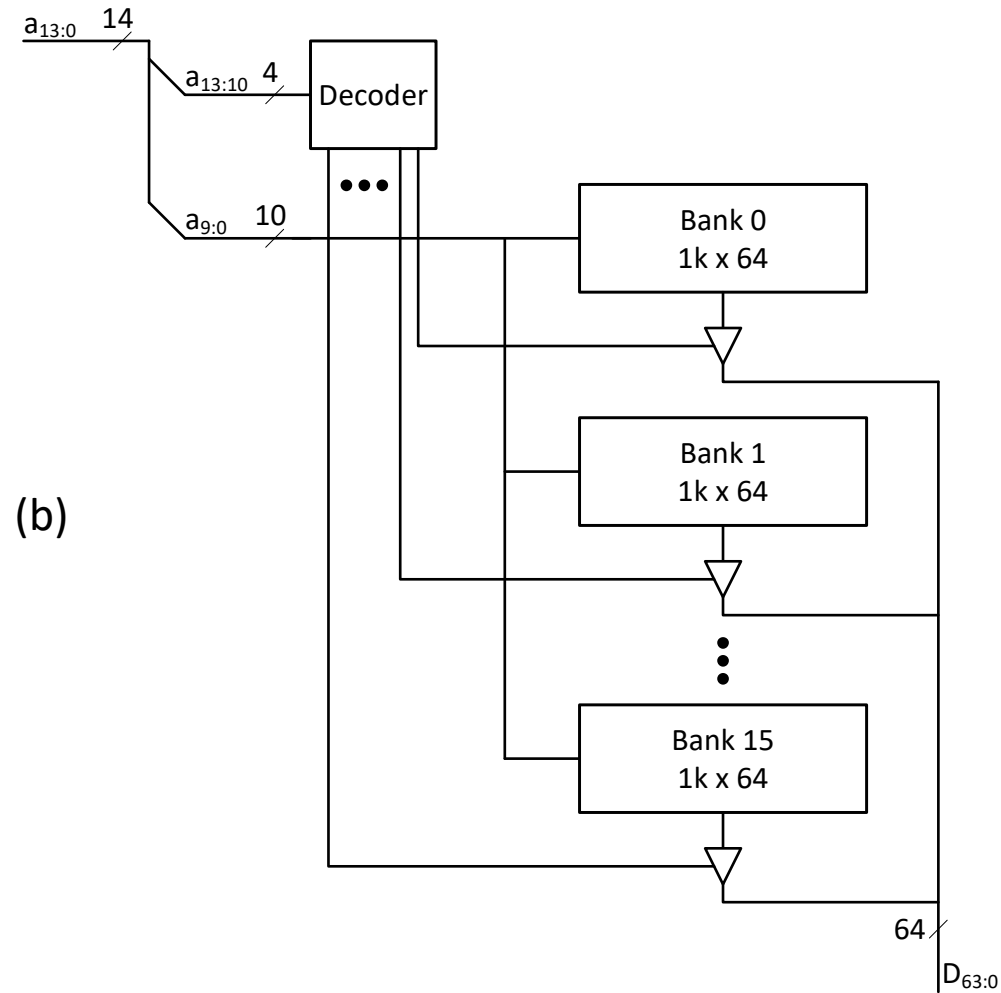


一次只讀寫一個，其他可以關掉省電

Bit slicing & banking

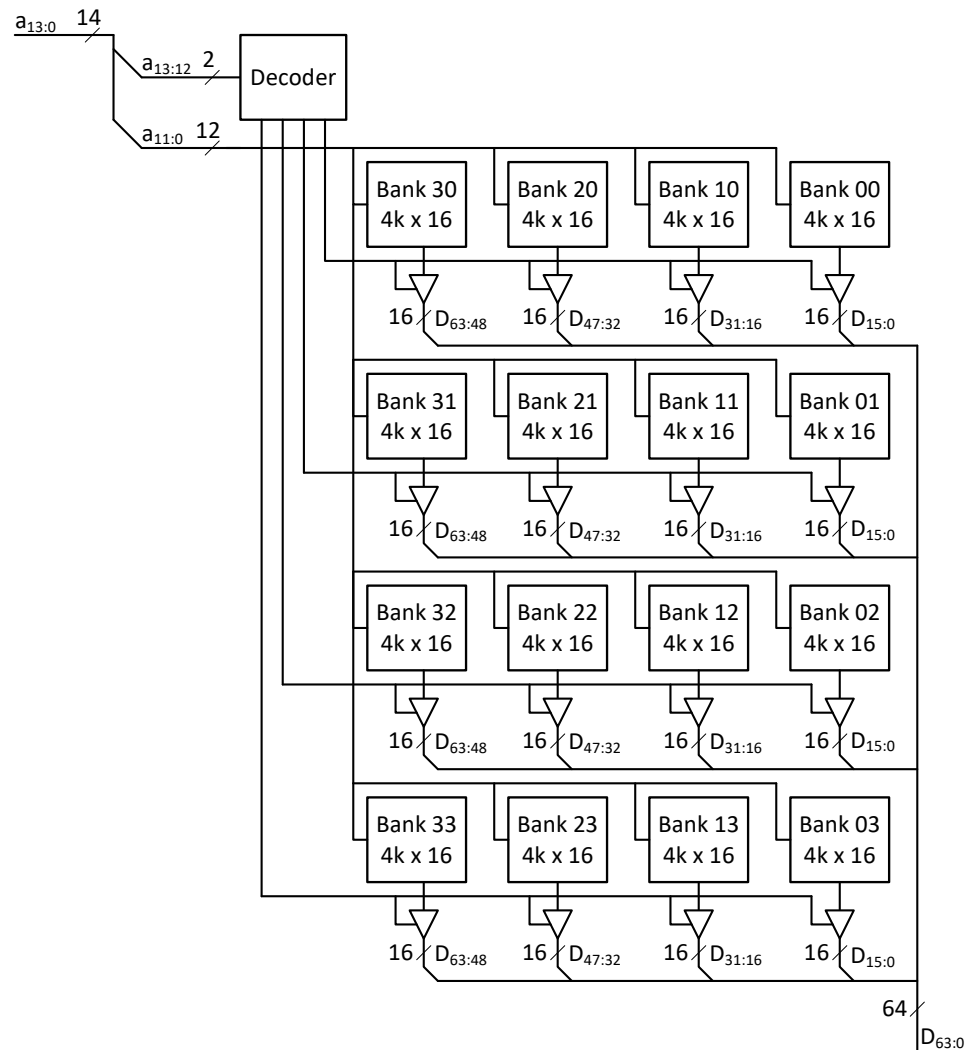

多個同時讀寫Interleaving

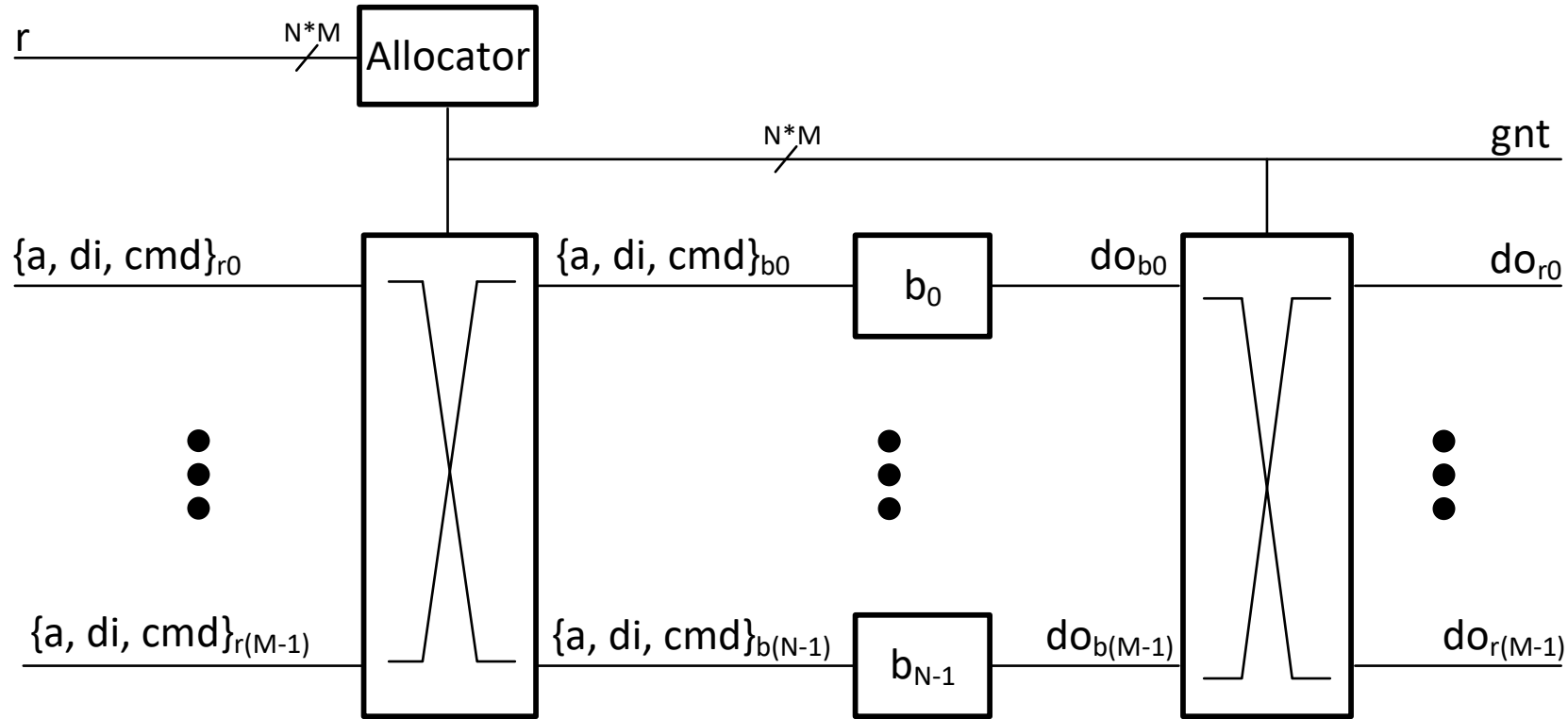

M request to N memory bank

Multiple bank 另種用法: 讀寫多個, 但位址不一樣, 有彈性

Avoid head-of-line blocking

| Time | Q0 | Q1 | Q2 | Q3 | G0 | G1 | G2 | G3 |
|------|---------|---------|---------|---------|----|----|----|----|
| 1 | 0,1,2,3 | 0,1,2,3 | 0,1,2,3 | 0,1,2,3 | Q0 | - | - | - |
| 2 | 1,2,3 | 0,1,2,3 | 0,1,2,3 | 0,1,2,3 | Q1 | Q0 | - | - |
| 3 | 2,3 | 1,2,3 | 0,1,2,3 | 0,1,2,3 | Q2 | Q1 | Q0 | - |
| 4 | 3 | 2,3 | 1,2,3 | 0,1,2,3 | Q3 | Q2 | Q1 | Q0 |
| 5 | - | 3 | 2,3 | 1,2,3 | - | Q3 | Q2 | Q1 |
| 6 | - | - | 3 | 2,3 | - | - | Q3 | Q2 |
| 7 | - | - | - | 3 | - | - | - | Q3 |

若只能照順序讀寫，會被卡住
使用率低


Table 24.2: With head of line blocking, the memory system does not have full throughput. Requests that can be granted are stuck behind requests waiting for a over-subscribed resource.

| Time | Q0 | Q1 | Q2 | Q3 | G0 | G1 | G2 | G3 |
|------|---------|---------|---------|---------|----|----|----|----|
| 1 | 0,1,2,3 | 0,1,2,3 | 0,1,2,3 | 0,1,2,3 | Q0 | Q1 | Q2 | Q3 |
| 2 | 1,2,3 | 0,2,3 | 0,1,3 | 0,1,2 | Q3 | Q0 | Q1 | Q2 |
| 3 | 2,3 | 0,3 | 0,1 | 1,2 | Q2 | Q3 | Q0 | Q1 |
| 4 | 3 | 0 | 1 | 2 | Q1 | Q2 | Q3 | Q0 |

不照順序讀寫，誰有空就去做
不會被卡住，使用率**100%**

Table 24.3: When the arbiter is able to see requests beyond the head of the full, the memory system has no head of line blocking. It achieves full throughput.

Hierarchy

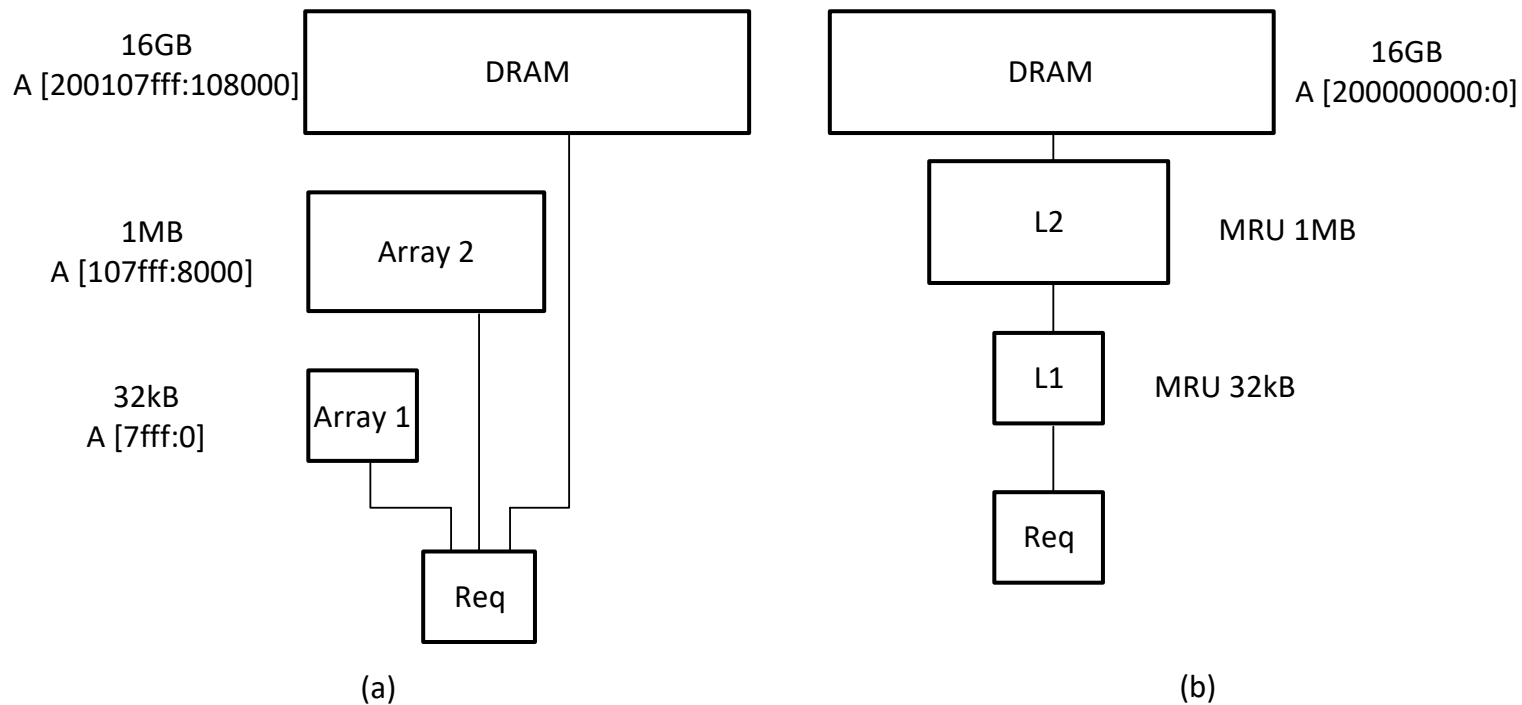

容量小的速度快，放在靠近**logic**附近，容量大的速度慢，放在比較遠的地方
可以搭配**cache**

Summary

- Interface timing
 - Convention about when data is transferred
 - When valid, when accepted
 - Open loop – always valid or periodic
 - Ready-valid flow-control, both ways, push, or pull
 - Serialization
- Interconnect
 - Allow any pair of clients to communicate
 - Bus, Crossbar, Network
- Memory
 - Capacity, bandwidth, latency, and granularity
 - SRAM and DRAM primitives
 - Bit-slice bank, or interleave to combine primitives
 - Hierarchy