

# Digital Circuits and Systems

## Lecture 12 Metastability and Synchronization Failure

---

Tian Sheuan Chang



(or When Good Flip-Flops go Bad)為什麼DFF會壞掉

# Outline [Dally Ch. 27/28]

- 壞掉的DFF
  - 當你違反setup time/hold time constraints時
- 對設計的影響與其解法
  - (何時最容易發生)



**壞掉的DFF => 變成震盪器了  
當你違反SETUP TIME/HOLD TIME  
CONSTRAINTS時**
  
# What happens when we violate setup and hold time constraints?




  
# Look at structure of CMOS latch



- Storage loop gets initialized with an ‘analog’ value
- Latch is a “time-to-voltage” converter



  
# Storage loop has a metastable state between 0 and 1



# Dynamics of $\Delta V$

  

 
# Metastable state of FF1 – 4007 Nand RS Latch






# Over time the waveform fills in

 


# Metastable state of 4011 Nand RS Latch


## What's going on here?

 


# Over time this waveform fills in too

 

# Actual circuit of 4011 Nand RS Latch

 


 □  $\bar{S}$ - $\bar{R}$  latch: **active-low** inputs for S & R




$\bar{S}$	$\bar{R}$	$Q$	$Q^+$	
1	1	0	0	Unchanged
1	1	1	1	
1	0	0	0	Reset to 0
1	0	1	0	
0	1	0	1	Set to 1
0	1	1	1	
0	0	0	—	Inputs not allowed
0	0	1	—	

# Initial state when both inputs are low

 


- When both inputs go high, it becomes a **6-stage ring oscillator**







Oscillation is **metastable**

 

# Oscillation is metastable

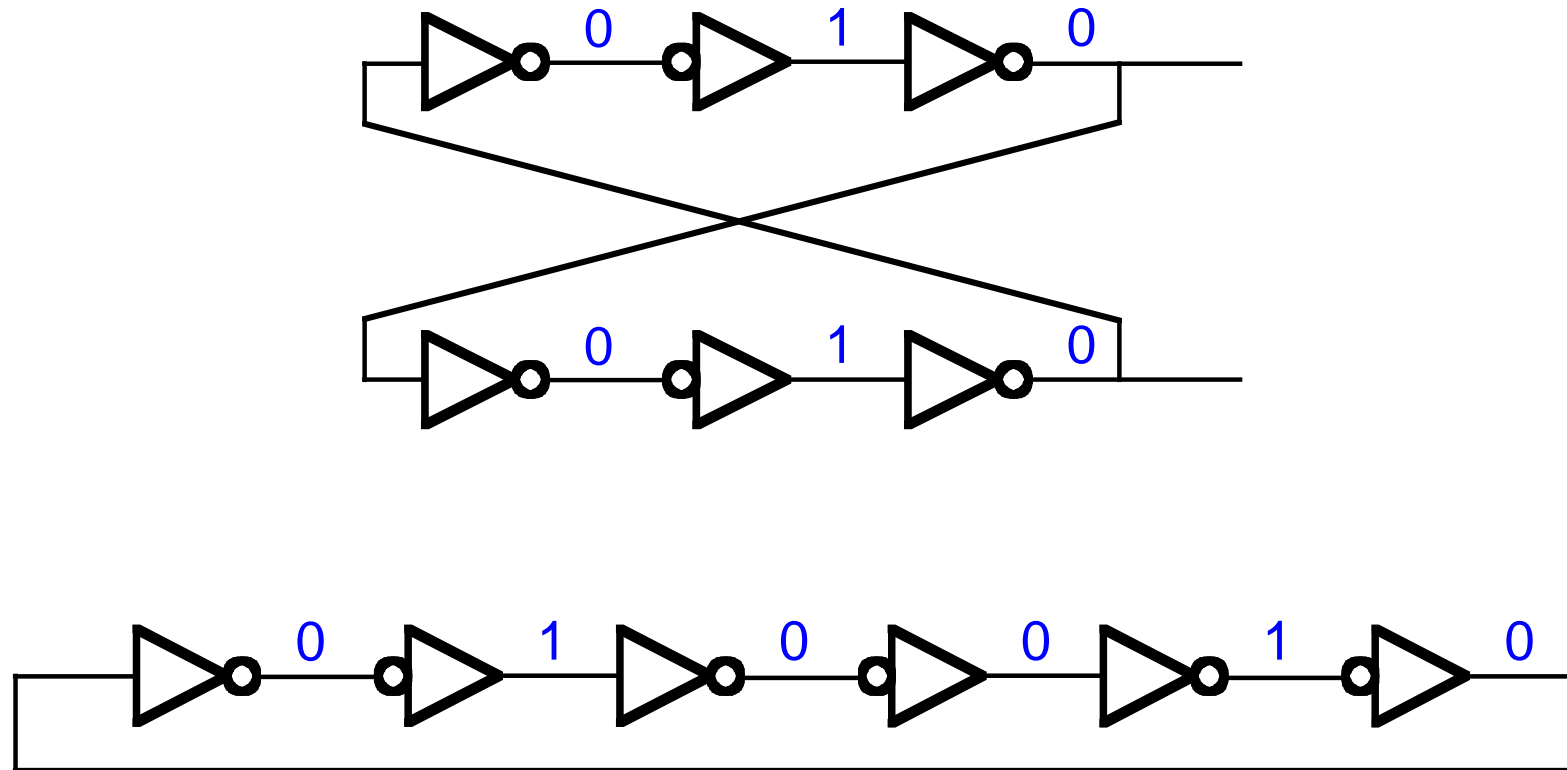

     
 
# If delays are balanced, ring sequences through six states repeatedly






# **對設計的影響 (何時最容易發生)**

# A Brute-Force Synchronizer

  

 
# What if *AW* is *still* in a metastable state when FF2 is clocked?




訊號根本不穩定  
會抓錯值

# 訊號跨越不同clock domain時，最容易發生

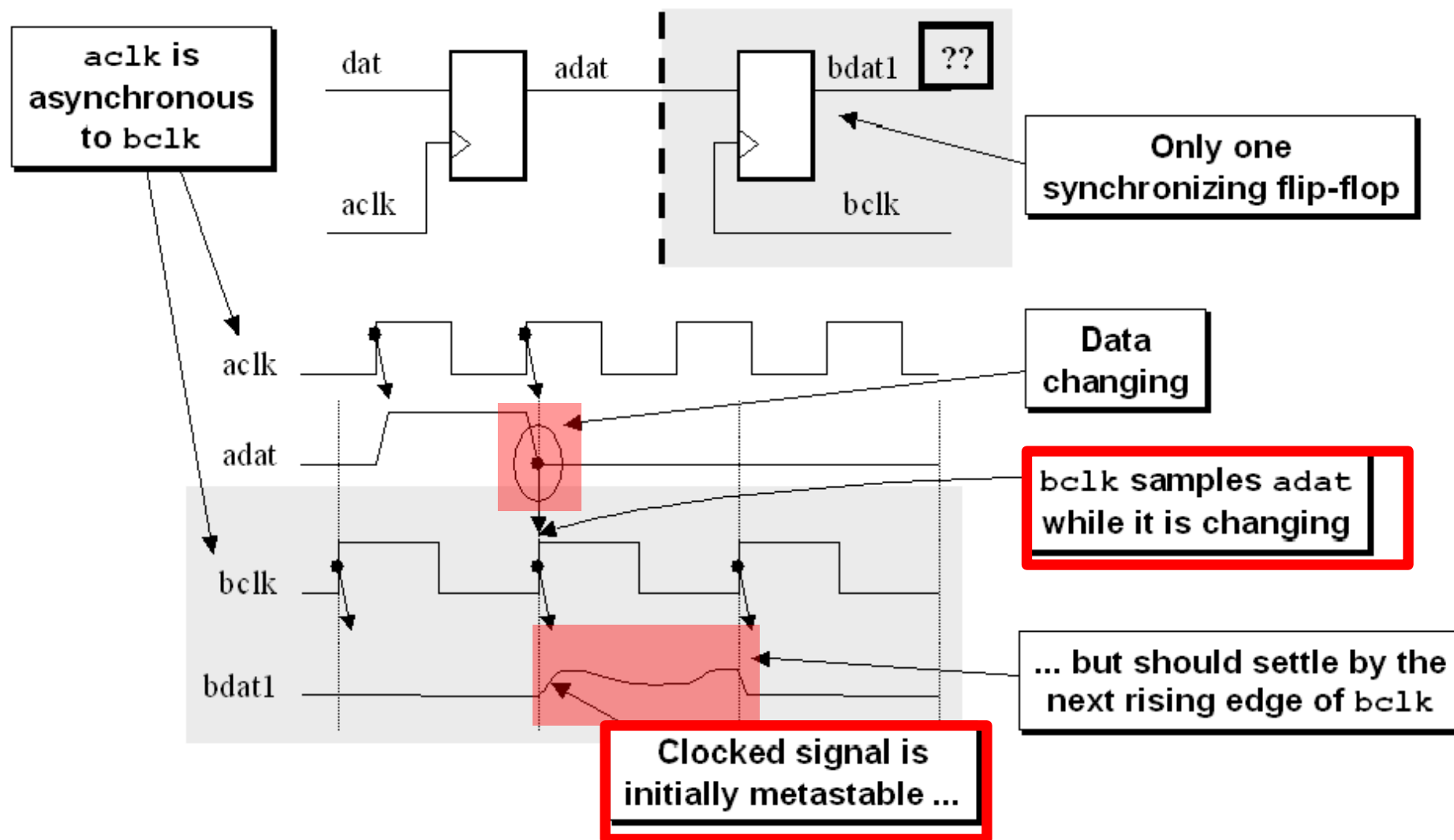
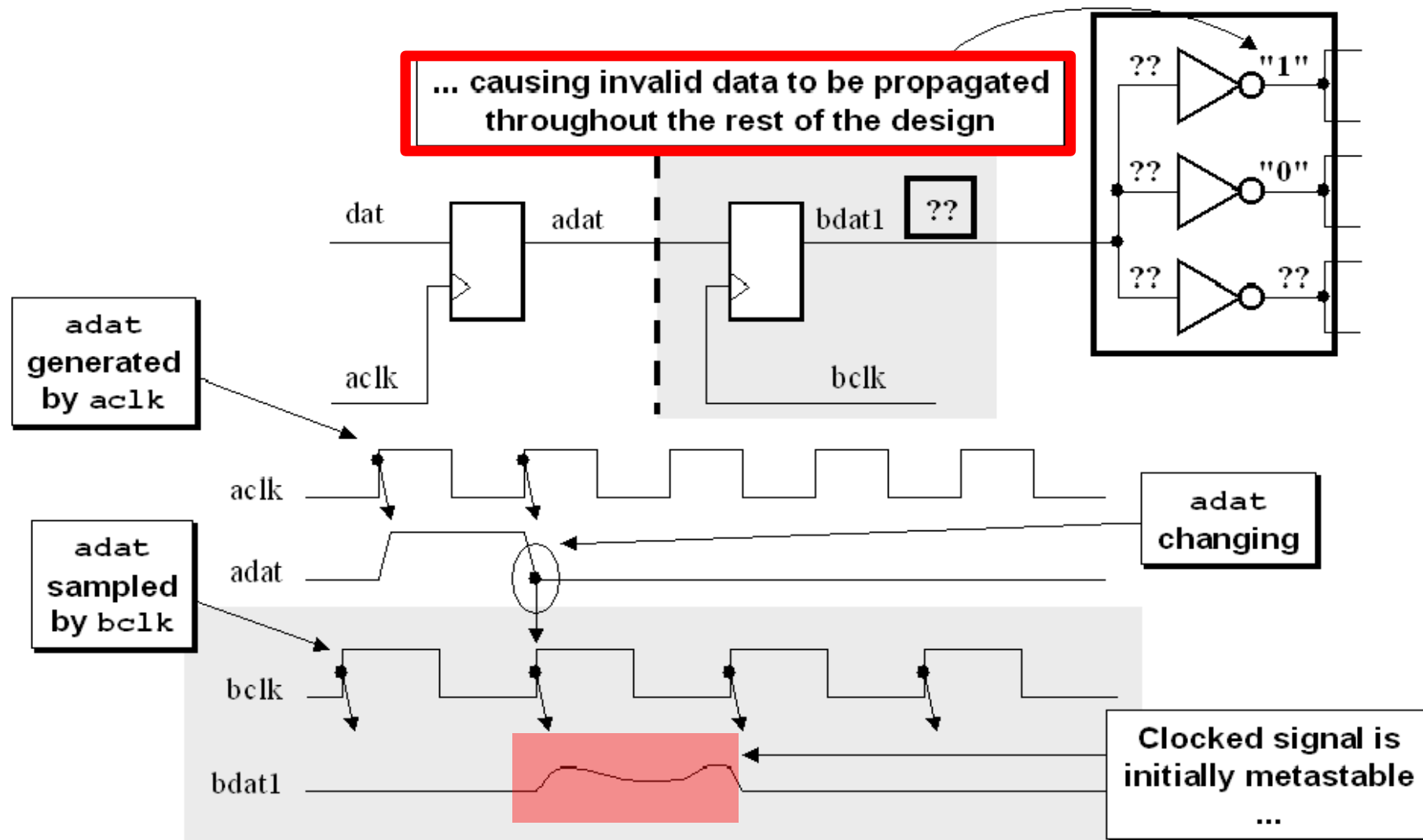
# Metastable bdat1 output propagating invalid data throughout the design



# 發生機率MTBF (mean time between failure)


$$MTBF = \frac{1}{f_{clk} * f_{data} * X}$$

The diagram illustrates the MTBF formula with three callout boxes: 'Synchronizing clock frequency' points to  $f_{clk}$ , 'Data changing frequency' points to  $f_{data}$ , and 'Other factors' points to  $X$ .


failures occur more frequently (shorter MTBF) in higher speed designs, or when the sampled data changes more frequently.  
越高頻或訊號變化越快，越容易產生錯誤

# 那設計要怎麼做?single bit case

超高頻設計，就用三個DFF串接

 


# 不良示範：沒經過register就送過去

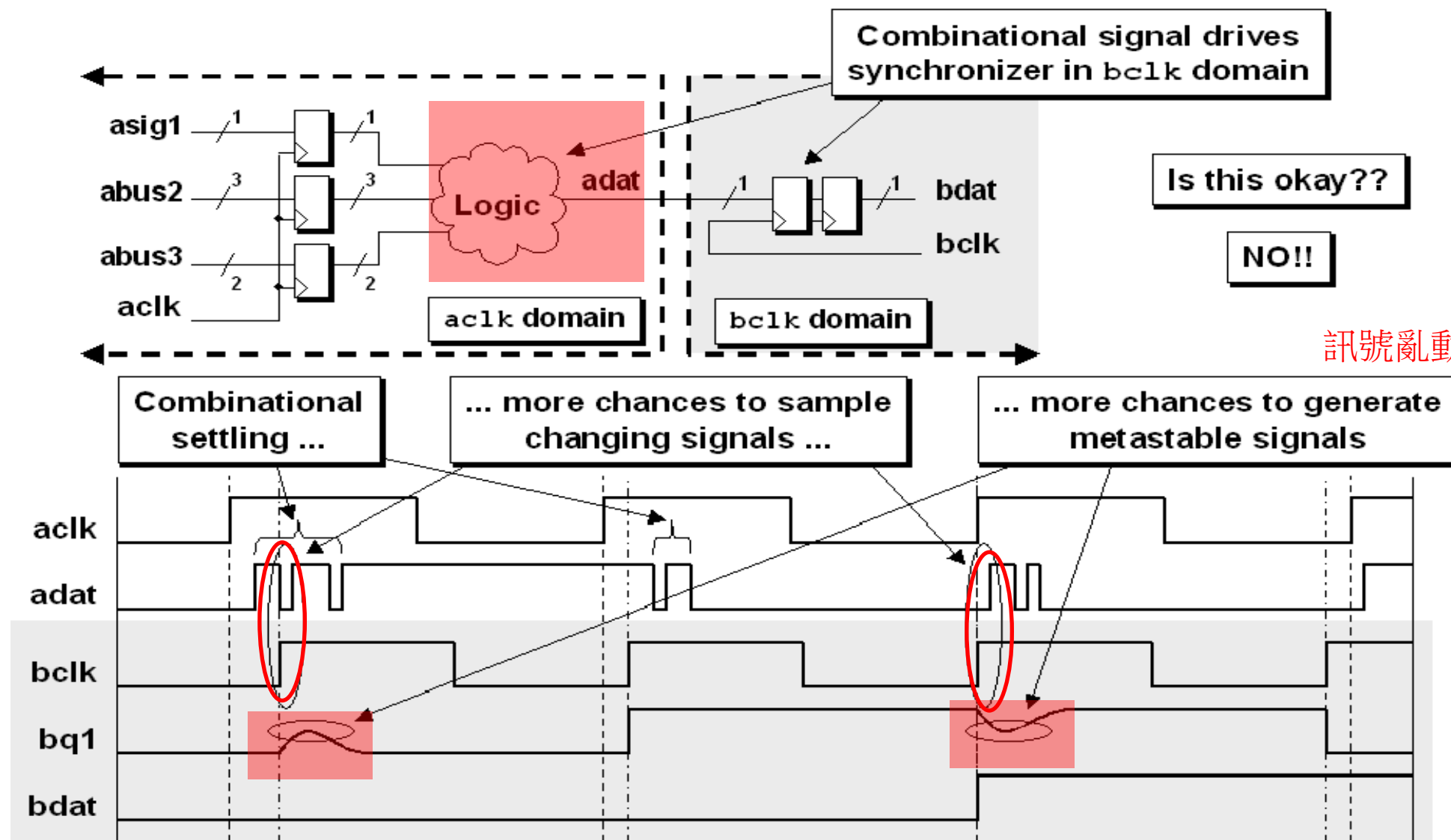

訊號亂動，抓錯機率高




# 優良設計

 


# 發送端訊號要怎麼給: 不能太短, 會被錯過

adat length < bclk cycle

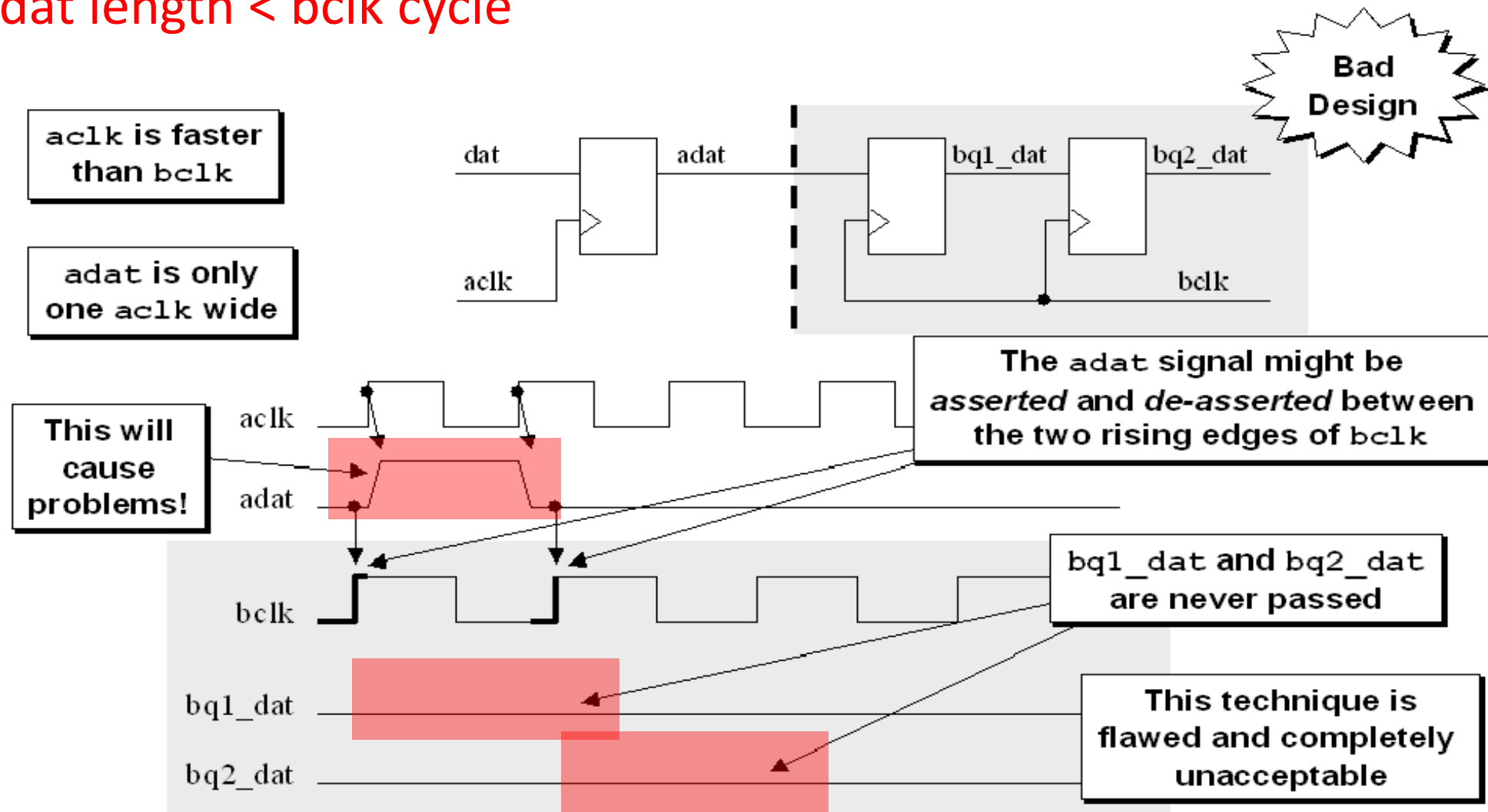
 
# 發送端訊號要怎麼給: 不夠長, 也會被錯過


adat length slightly larger than bclk cycle



"Open-Loop" solution

adat pulse should  
be 1-1/2 bclk  
periods in width

adat length  $\geq 1.5$  bclk cycle

 

訊號要夠長， $\geq 1.5X$  bclk


 


Figure 10 - Lengthened pulse to guarantee that the control signal will be sampled

# "Closed-Loop" solution

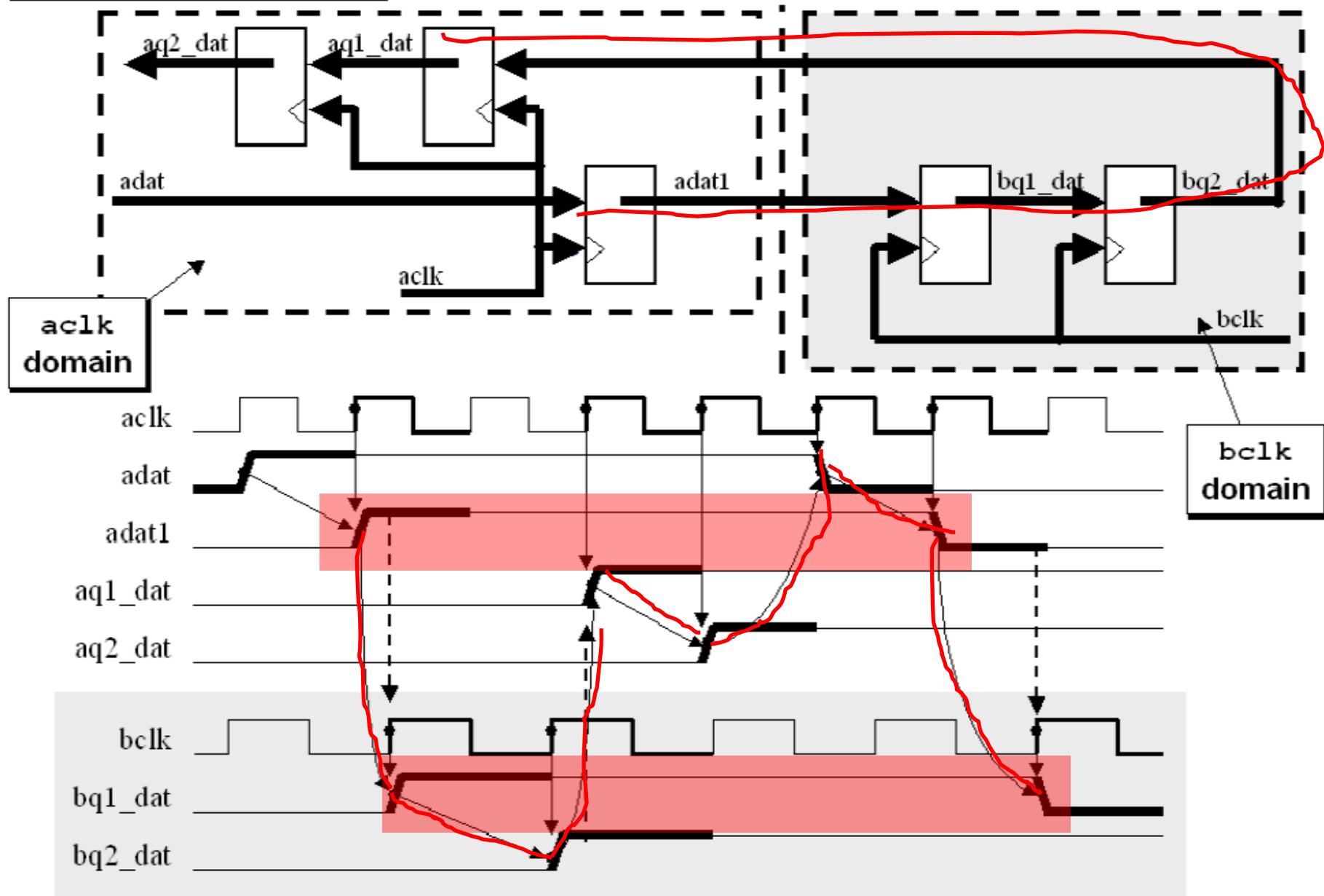

要寄有回條的掛號信


接收端回傳一個訊號，  
告訴發送端已經收到，  
發送端再關掉訊號

Figure 11 - Signal with feedback to acknowledge receipt

# 那設計要怎麼做? multi-bit case (control sig)

一次要對齊多個bit很難，容易錯位

個別傳過去

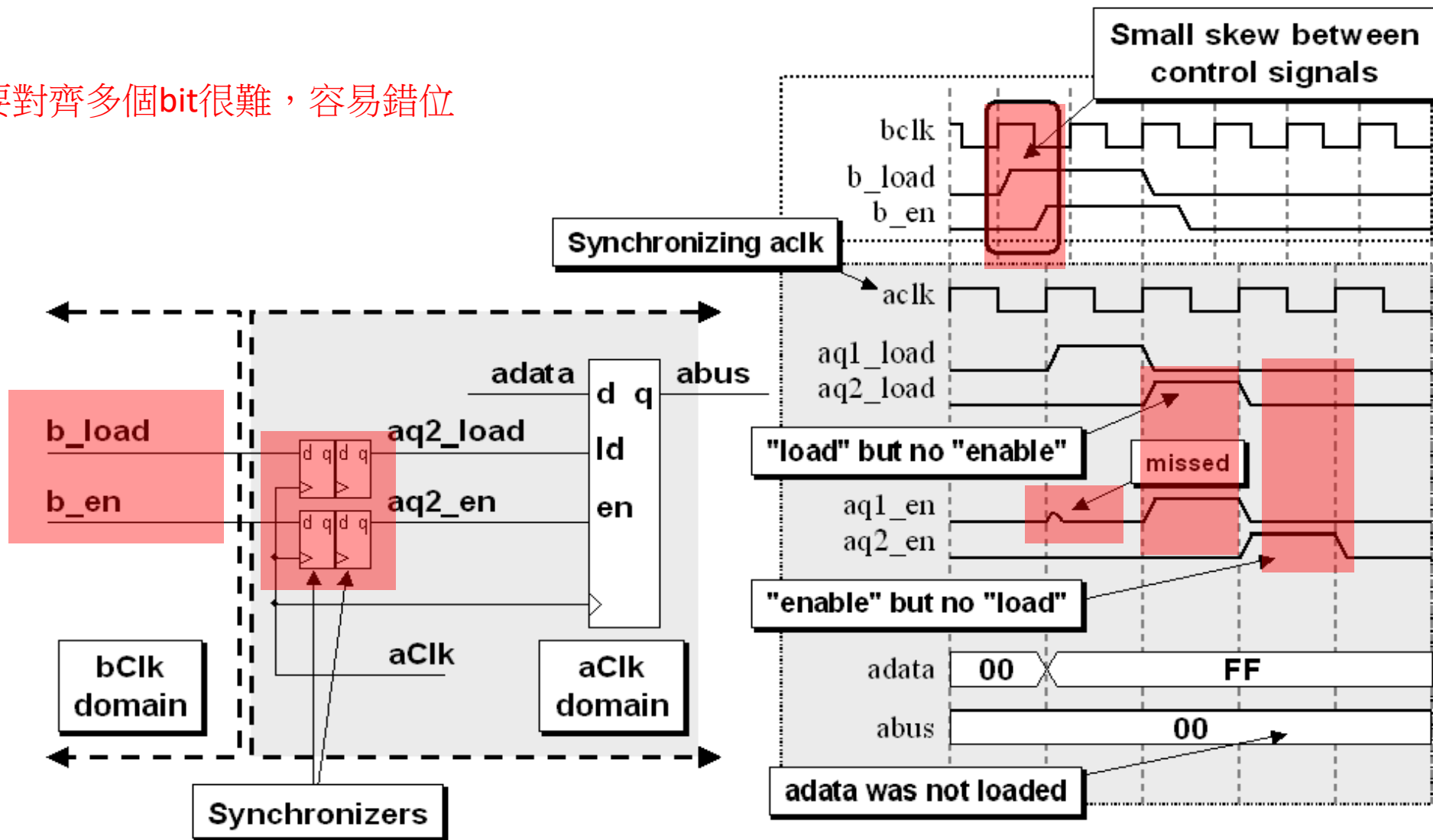


容易錯位

# 那設計要怎麼做? multi-bit case (control sig)



合併成單一控制訊號，比照單一bit去傳

合併成單一控制訊號

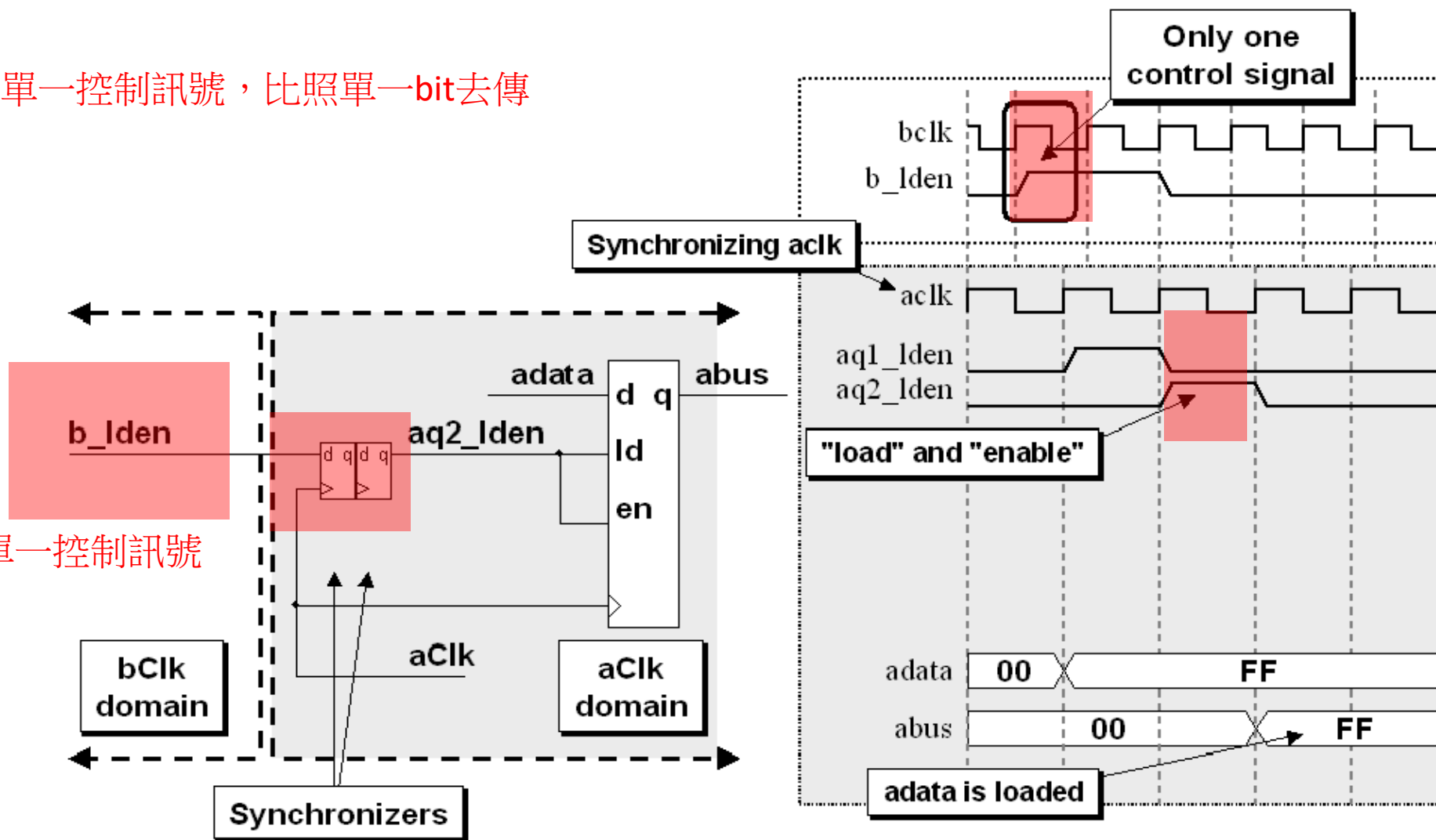

# 多個data bit 要傳，直接傳會出錯



One hot active low address decoder

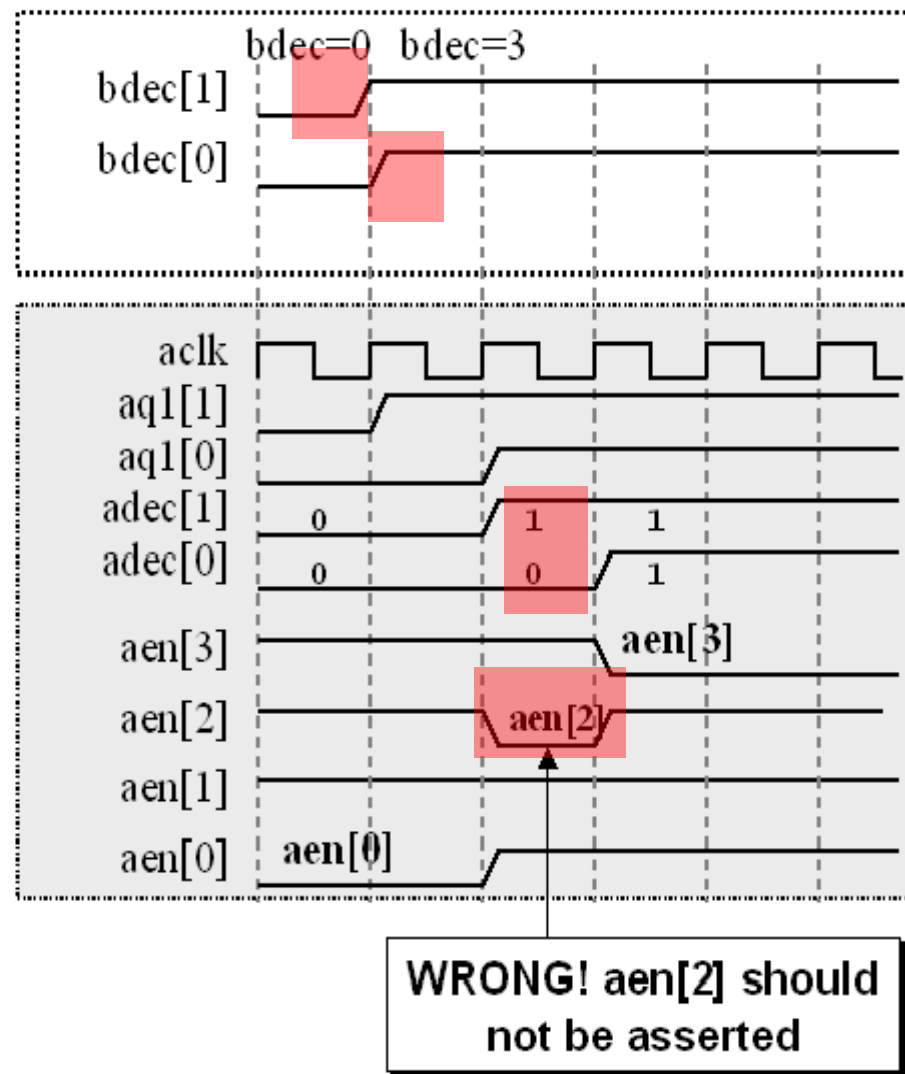 



# 用單一控制訊號過同步器，再去控制data

One hot active low address decoder

 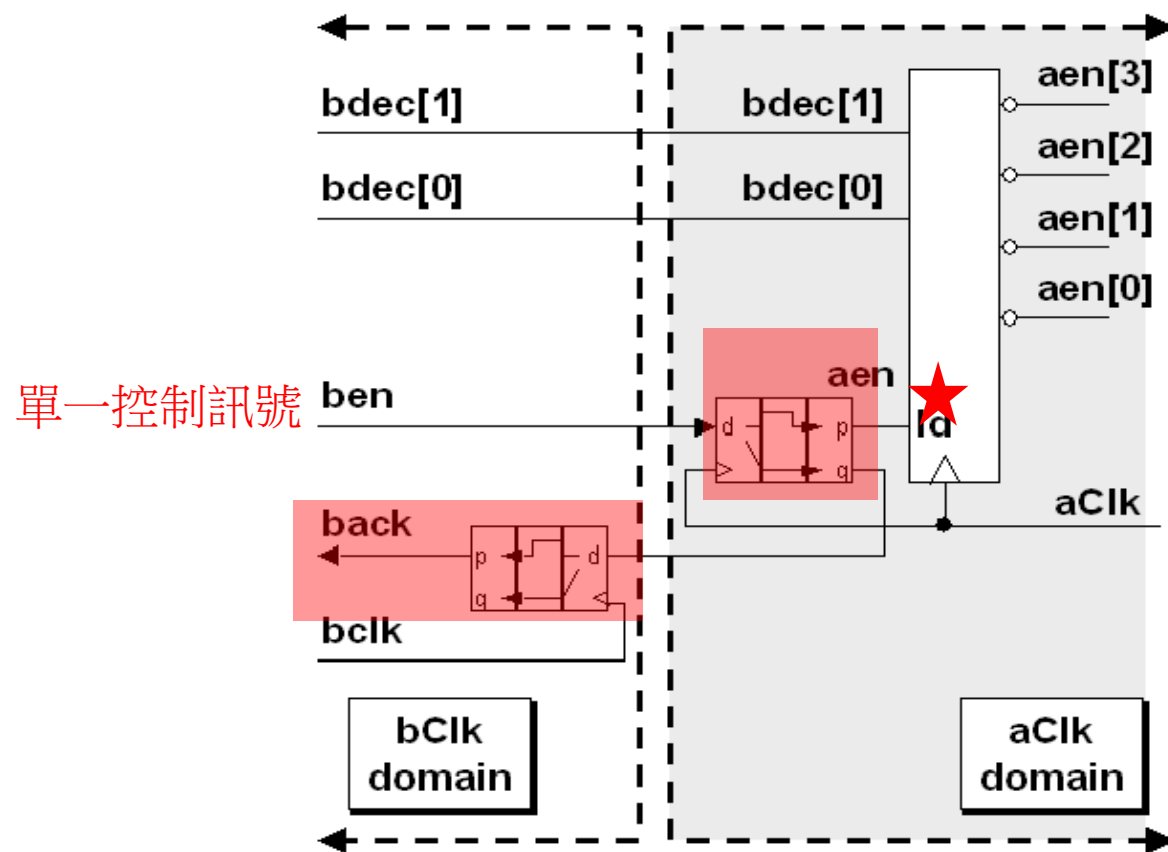

## 傳counter 值

Warning: The Surgeon General has determined that passing binary-coded and one-hot signals through a brute-force synchronizer can be hazardous to your circuits.

# Gray Code 是個好主意，一次只有一個bit變

Solution:

Use a Gray code counter

For all but the MSB:

```
next_b[i] = (b[i-1] & !(b[i-2:0])) ? !xor(b[n-1:i+1]) : b[i];
```

For the MSB:

```
next_b[i] = (b[i-2:0]) ? b[i] : b[i-1] ;
```

Can we use this Gray code for the head and tail pointers of our FIFO?

```

module GrayCount4(clk, rst, out) ;
    input clk, rst ;
    output [3:0] out ;
    wire [3:0] out, next ;

    DFF #(4) count(clk, next, out) ;

    assign next[0] = !rst & !(out[1]^out[2]^out[3]) ;
    assign next[1] = !rst & (out[0] ? !(out[2]^out[3]) : out[1]) ;
    assign next[2] = !rst & ((out[1] & !out[0]) ? !out[3] : out[2]) ;
    assign next[3] = !rst & (!(|out[1:0]) ? out[2] : out[3]) ;
endmodule

```

```
module gray2bin #(parameter SIZE = 4)
  (output logic [SIZE-1:0] bin,
   input logic [SIZE-1:0] gray);

  always_comb
    for (int i=0; i<SIZE; i++) bin[i] = ^(gray>>i);
endmodule
```

```
module bin2gray #(parameter SIZE = 4)
  (output logic [SIZE-1:0] gray,
   input logic [SIZE-1:0] bin);

  assign gray = (bin>>1) ^ bin;
endmodule
```

```
# xxxx
# 0000
# 0001
# 0011
# 0010
# 0110
# 0111
# 0101
# 0100
# 1100
# 1101
# 1111
# 1110
# 1010
# 1011
# 1001
# 1000
# 0000
# 0001
# 0011
# 0010
```