



Digital Circuits and Systems

Lecture 8 Model Dapath FSM

Tian Sheuan Chang

FSM 百百種，但大部分的next state 用counter 類簡單計算就可以，不用table


Outline [Dally ch. 16]

- Counter
 - Simple counter, up down counter
- Shift register
- Datapath and control partitioning
 - Vending machine example

COUNTER AS FSM



COUNTER 當FSM控制

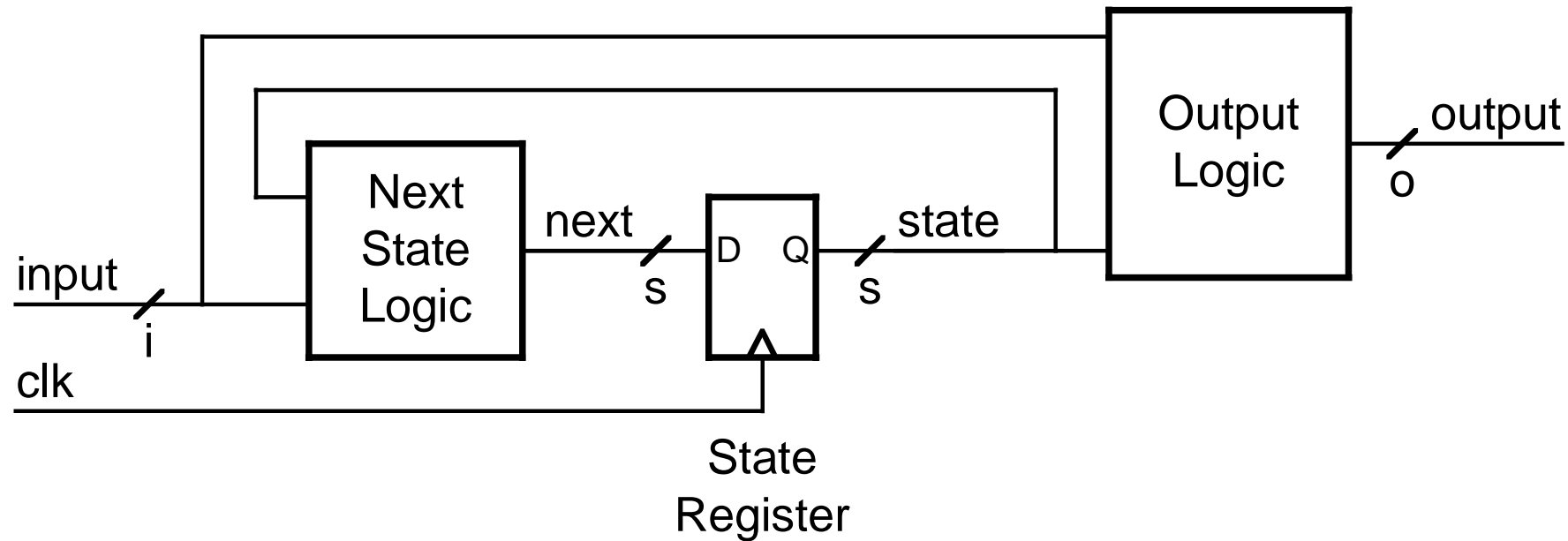An FSM is a state register and two functions




Counter 當FSM

  - Suppose you want to build an FSM with the following state diagram



第一種寫法：表格式 Table based

 

State	Next State	
	~rst	rst
0	1	0
1	2	0
2	3	0
⋮		
30	31	0
31	0	0

```

module Counter1(clk,rst,out) ;
  input  rst, clk ; // reset and clock
  output [4:0] out ;
  reg     [4:0] next ;

  DFF #(5) count(clk, next, out) ;//5-bit counter


  always_comb begin //any change
    casez({rst,out})
      6'b1?????: next = 0 ;
      6'd0: next = 1 ;
      6'd1: next = 2 ;
      6'd2: next = 3 ;
      ...
      6'd30: next = 31 ;
      6'd31: next = 0 ;
      default: next = 0 ;
    endcase
  end
endmodule

```

表格很好，但這個變化很規則，可以更簡單描述

```
next = r ? 0 : state + 1 ;
```

第二種寫法: 用算數作FSM Datapath FSM

 

```

module Counter(clk, rst, count) ;
  parameter n=5 ;
  input rst, clk ; // reset and clock
  output [n-1:0] count ;

  wire    [n-1:0] next = rst? 0 : count + 1 ;

  DFF #(n) count(clk, next, count) ;
endmodule
  
```

Make Table **Symbolic**

State	Next State	
	~rst	rst
0	1	0
1	2	0
2	3	0
▪ ▪ ▪		
30	31	0
31	0	0

State	Next State	
	~rst	rst
a	a+1	0

Alternate description (symbolic table)

```

module Counter1(clk,rst,out) ;
    input rst, clk ; // reset and clock
    output [4:0] out ;
    reg      [4:0] next ;

    DFF #(5) count(clk, next, out) ;

    always@(rst, out) begin
        casez({rst,out})
            6'b1?????: next = 0 ;
            6'd0: next = 1 ;
            6'd1: next = 2 ;
            6'd2: next = 3 ;
            6'd3: next = 4 ;
            6'd4: next = 5 ;
            6'd5: next = 6 ;
            6'd6: next = 7 ;
            ...
            6'd30: next = 31 ;
            6'd31: next = 0 ;
            default: next = 0 ;
        endcase
    end
endmodule

```

```

module Counter1(clk,rst,out) ;
    input rst, clk ; // reset and clock
    output [4:0] out ;
    reg      [4:0] next ;

    DFF #(5) count(clk, next, out) ;

    always@(rst, out) begin
        case(rst)
            1'b1: next = 0 ;
            1'b0: next = out+1 ;
        endcase
    end
endmodule

```

**Quiz: what's the difference
Between these 2 coding examples?**

Alternate description (symbolic table, ReWrite for coding Style)

```

module Counter1(clk,rst,out) ;
    input rst, clk ; // reset and clock
    output [4:0] out ;
    reg      [4:0] next ;
    reg      [4:0] out ;

    always@(posedge clk or posedge rst)
        if(rst) out <=0;
        else out <= next;

    always@(*) begin
        case({out})
            5'd0: next = 1 ;
            5'd1: next = 2 ;
            5'd2: next = 3 ;
            5'd3: next = 4 ;
            5'd4: next = 5 ;
            5'd5: next = 6 ;
            5'd6: next = 7 ;
            ...
            5'd30: next = 31 ;
            5'd31: next = 0 ;
        endcase
    end
endmodule

```

```

module Counter1(clk,rst,out) ;
    input rst, clk ; // reset and clock
    output [4:0] out ;
    reg      [4:0] next ;
    reg      [4:0] out ;

    always@(posedge clk or posedge rst)
        if(rst) out <=0;
        else out <= next;

    always@(*) begin
        next = out+1 ;
    end
endmodule

```



Quiz: what's the difference
Between these 2 coding examples?

Schematic: Counter as FSM


A simple counter

$\text{next_state} = \text{rst} ? 0 : \text{state} + 1$

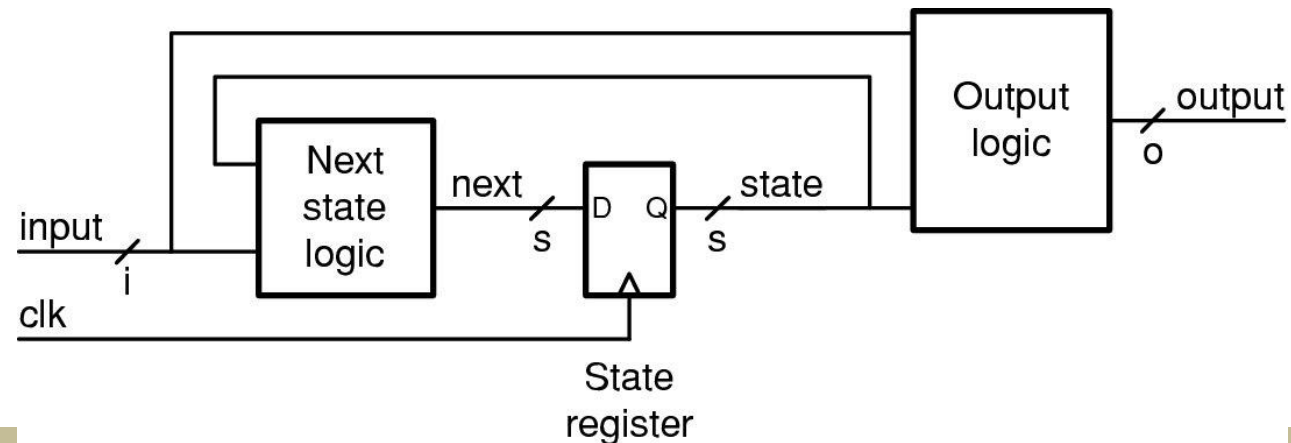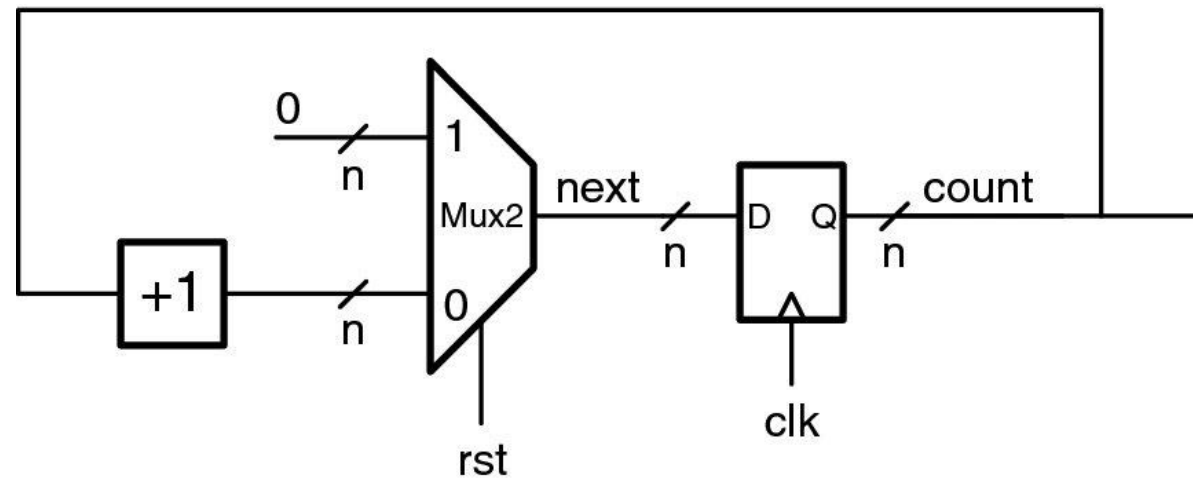MUX and D-FF can be replaced
By resettable D-FF



Sequential Datapath

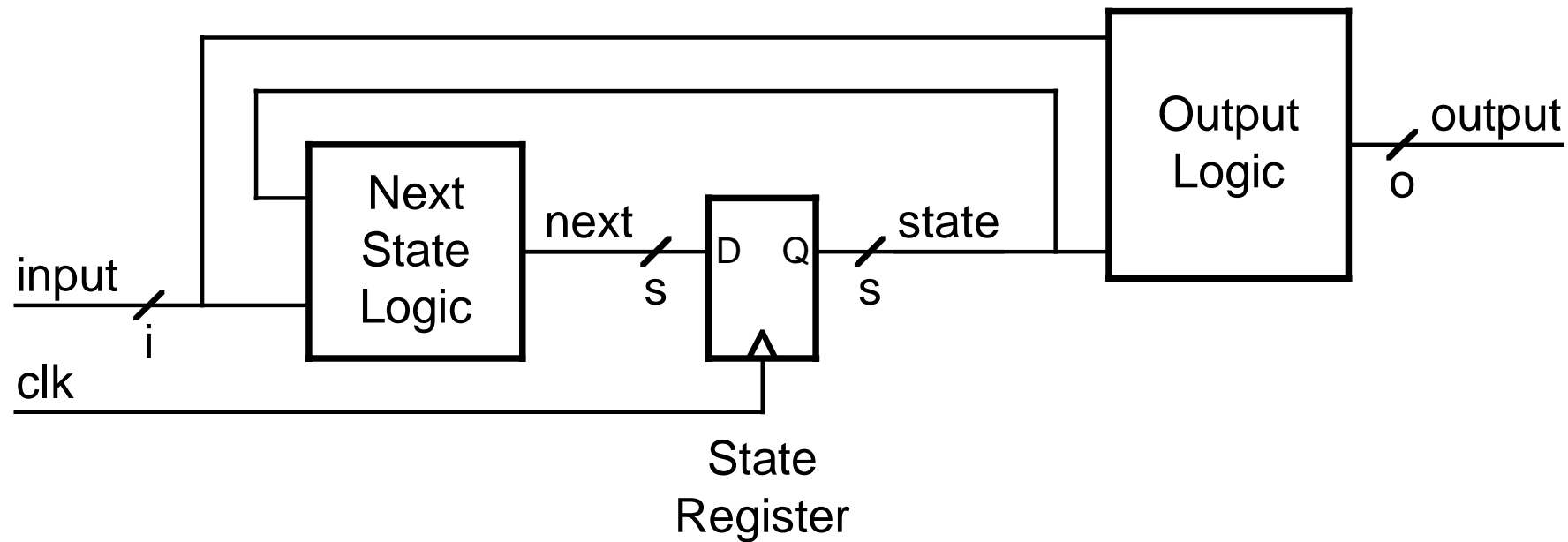

An Up/Down/Load (UDL) Counter

- A Deluxe Counter that can:
 - count up (increment)
 - count down (decrement)
 - be loaded with a value
- Up, down, and load guaranteed to be **one-hot**. **rst overrides**.

```
if rst, next_state = 0
if (!rst & up) next_state = state+1
if (!rst & down) next_state = state-1
if (!rst & load) next_state = in
else next_state = state
```

 


Table Version

State	Next State			
	rst	up	down	load
0	0	1	31	in
1	0	2	0	in
2	0	3	1	in
▪ ▪ ▪				
30	0	31	29	in
31	0	0	30	in

Symbolic Table Version

State	Next State				
	rst	up	down	load	
q	0	q+1	q-1	in	q

State	In	Rst	Up	Down	Load	Next
q	x	1	x	x	x	0
q	x	0	1	0	0	q+1
q	x	0	0	1	0	q-1
x	y	0	0	0	1	y
q	x	0	0	0	0	q

Up, down, and load guaranteed to be **one-hot**. **rst overrides**

```

module UDL_Count1(clk, rst, up, down, load, in, out) ;
  parameter n = 4 ;
  input clk, rst, up, down, load ;
  input [n-1:0] in ;
  output [n-1:0] out ;
  wire [n-1:0] out ;
  reg [n-1:0] next ;

```

```

DFF #(n) count(clk, next, out) ;

```

```

always_comb begin
  casez({rst, up, down, load})
    4'b1???: next = {n{1'b0}} ; //reset
    4'b0100: next = out + 1'b1 ;
    4'b0010: next = out - 1'b1 ;
    4'b0001: next = in ;
    4'b0000: next = out ;
    default: next = {n{1'bx}} ; //unknown
  endcase
end
endmodule

```

Up or down, 需要兩個加減法器, 可以更簡化嗎?

State	Next State				
	rst	up	down	load	else
q	0	q+1	q-1	in	q

[Check p.11 async rst](#)


```

module UDL_Count1(clk, rst, up, down, load, in, out) ;
    parameter n = 4 ;
    input clk, rst, up, down, load ;
    input [n-1:0] in ;
    output [n-1:0] out ;
    wire [n-1:0] out, outpm1 ;
    reg [n-1:0] next ;

```

```

DFF #(n) count(clk, next, out) ;

```

只用一個加減法器

```

assign outpm1 = out + {{n-1{down}},1'b1} ; // down ? -1 : 1

```

```

always@(rst, up, down, load, in, out, outpm1) begin
    casez({rst, up, down, load})
        4'b1???: next = {n{1'b0}} ;
        4'b01??: next = outpm1 ;
        4'b001?: next = outpm1 ;
        4'b0001: next = in ;
        default: next = out ;
    endcase
end
endmodule


```

把可以共用的資源提出來

Quiz: what's the difference
Between these 2 coding examples?

[Check p.11 async rst](#)

Schematic of UDL Counter

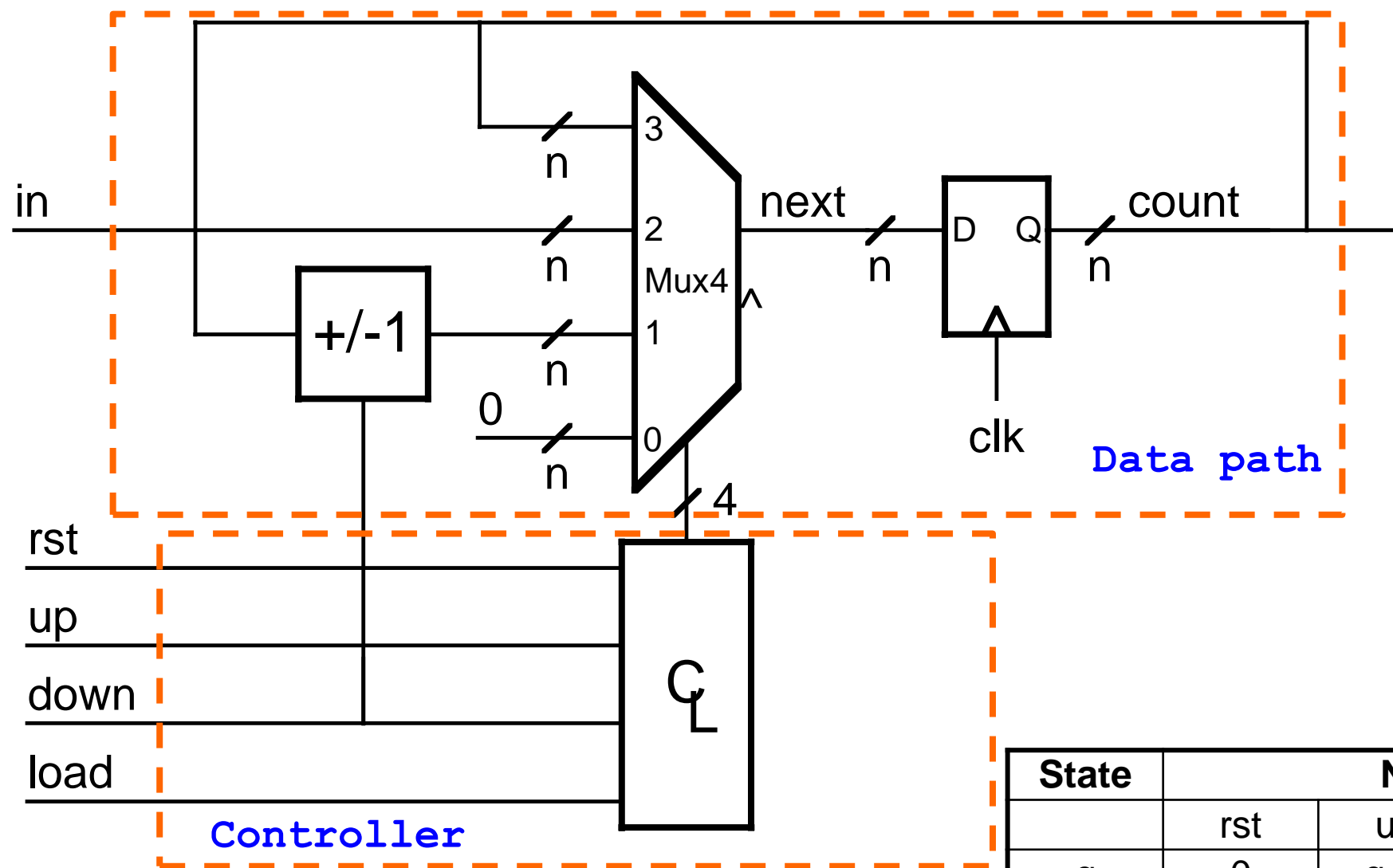

State	Next State				
	rst	up	down	load	else
q	0	q+1	q-1	in	q

EXERCISE- Divide by 3 with Data Path

- *Output: (out) goes high once for each third cycle that input (in) is high*
- Example
 - IN: 0101010011100
 - OUT: 0000001000010
 - Note one cycle delay
- Draw the data path
 - What arithmetic operators are demanded?
 - What are the inputs and outputs?
 - What are the control signals?
- How do we make the output go high in the same cycle as the third input 1?



Timer module (Set a Value and Decrease)



load – loads count

done – asserted when count = 0

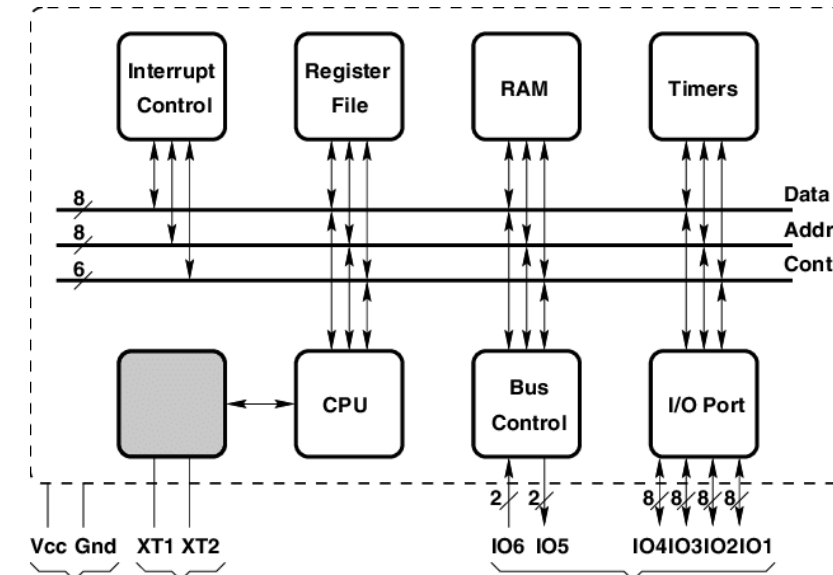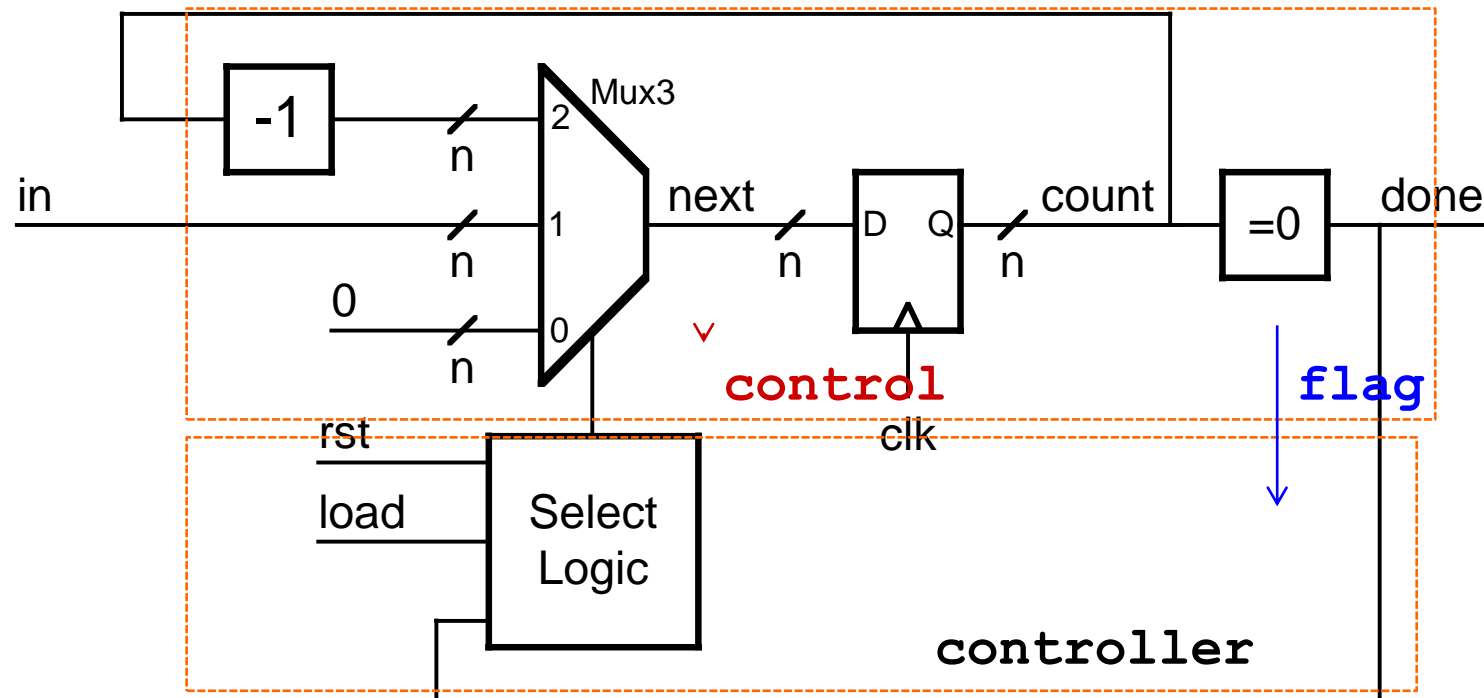count decrements unless load or done is true



8051

Data path: adder+mux+D-FF+comparator

Controller: combinational logic with inputs and flags

Exercise: realize divide-by-3 function on this module (Ex. 16.1)

```
module Timer(clk, rst, load, in, done) ;
    parameter n=4 ;
    input clk, rst, load ;
    input [n-1:0] in ;
    output done ;
    wire [n-1:0] count, next_count ;
    wire done ;

    DFF #(n) cnt(clk, next_count, count) ;

    always@(rst, load, in, out) begin
        casez({rst, load, done})
            3'b1?? : next_count = 0 ; // reset
            3'b001 : next_count = 0 ; // done
            3'b01? : next_count = in ; // load
            default: next_count = count-1'b1; // count down
        endcase
    end


    assign done = (count == 0) ;
endmodule
```

[Check p.11 async rst](#)

SHIFT REGISTERS

Shift Register (+ Shift left + Shift right)
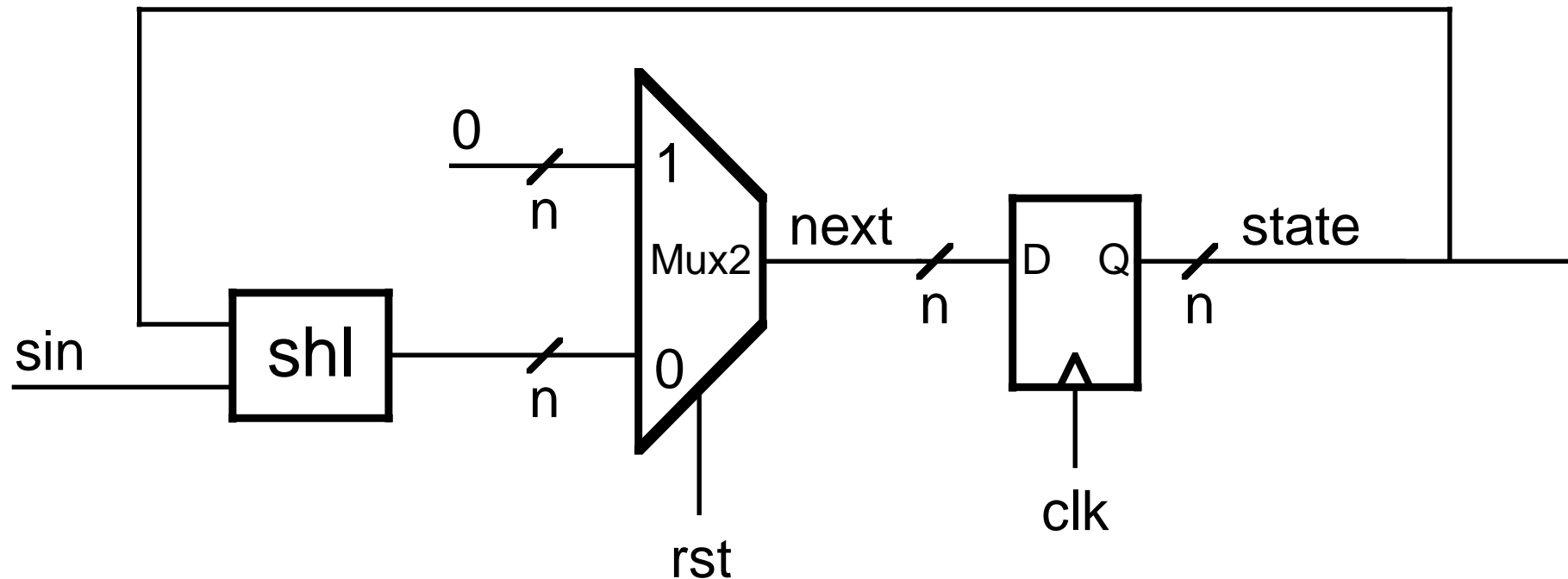
`next_state = rst ? 0 : {state[n-2:0],sin} ;`



Exercise: apply MUX to realize shl and shr, which can be merged with rst.

Quiz: what function can be achieved if D-FF's are connected serially with parallel data out?

```

module Shift_Register1(clk, rst, sin, out) ;
    parameter n = 4 ;
    input clk, rst, sin ;
    output [n-1:0] out ;

    wire [n-1:0] next = rst ? {n{1'b0}} : {out[n-2:0],sin} ;

    DFF #(n) cnt(clk, next, out) ;
endmodule

```

[Check p.11 async rst](#)

```

module Shift_Register1(clk, rst, sin, out) ;
    parameter n = 4 ;
    input clk, rst, sin ;
    output [n-1:0] out ;

    wire [n-1:0] next;
    assign next = {out[n-2:0],sin} ;
    always_ff@(posedge clk or posedge rst)
        if(rst) out <= {n{1'b0}} ;
        else out <= next;

endmodule

```

A better coding style


```
module LRL_Shift_Register1(clk, rst, left, right, load, sin, in,
out) ;
    parameter n = 4 ;
    input clk, rst, left, right, load, sin ;
    input [n-1:0] in ;
    output [n-1:0] out ;
    reg [n-1:0] next ;
    reg [4:0] out ;

    always_ff@(posedge clk or posedge rst)
        if(rst) out <=0;
        else out <= next;

    always_comb begin
        casez({left,right,load})
            3'b1??: next = {out[n-2:0],sin} ; // left
            3'b01?: next = {sin,out[n-1:1]} ; // right
            3'b001: next = in ; // load
            default: next = out ; // hold
        endcase
    end
endmodule
```


DATAPATH AND CONTROL PARTITIONING

所有數位設計都可拆成資料流計算與控制兩部分

Datapath/Control Partitioning

Datapath – determined by a function – e.g., mux, arithmetic, ...

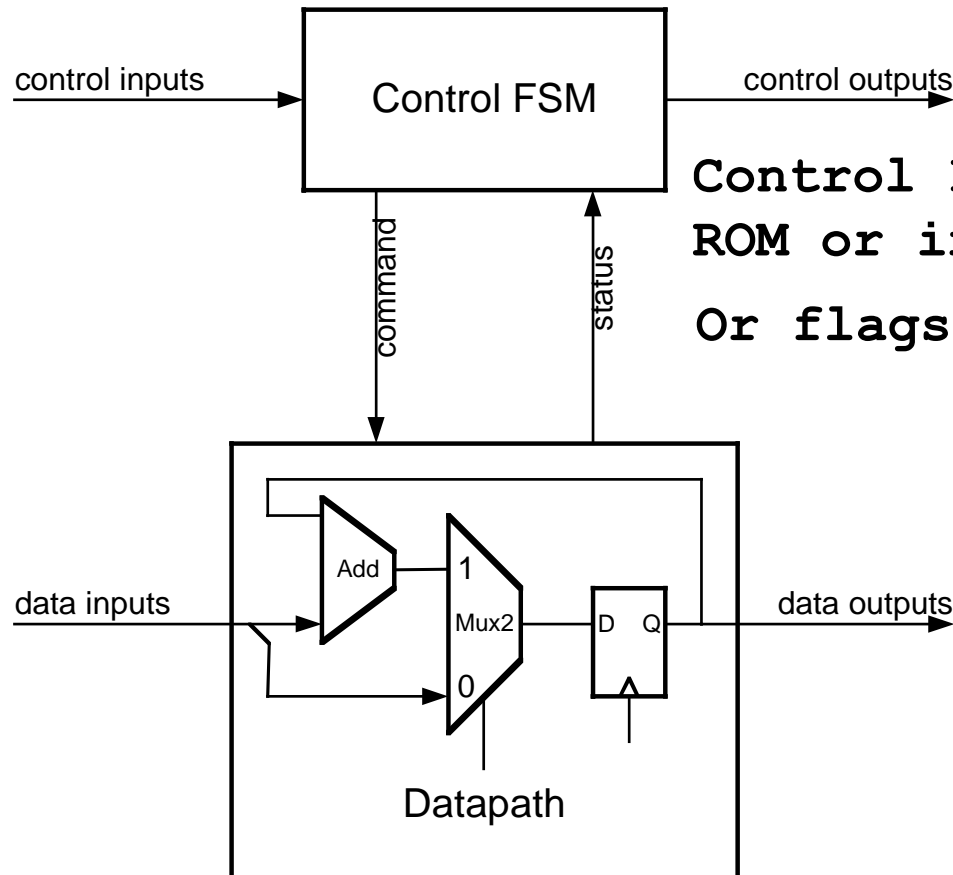Control – determined by state diagram or state table



Control FSM can be realized by
ROM or instruction memory
Or flags

- 規格

- The vending machine accepts *nickels, dimes, and quarters*. Whenever a coin is deposited into the coin slot, a pulse appears for one clock cycle on one of *three lines indicating the type of coin: nickel, dime, or quarter*.
- The price of the item is set on an n-bit switch internal to the machine (in units of nickels), and is input to the controller on the n-bit signal *price*.
- When sufficient coins have been deposited to purchase a soft drink, the status signal *enough* is asserted. Any time *enough* is asserted and the user press a *disperse* button; signal *serve* is asserted for exactly one cycle to serve the soft drink. After asserting serve, the FSM must wait until signal *done* is asserted, indicating that the mechanism has finished serving the soft drink.

- After serving, the machine returns change (if any) to the user. It does this one nickel at a time, asserting the signal **change**, for exactly one cycle and waiting for signal **done** to indicate that a nickel has been dispensed before dispensing the next nickel or returning to its original state. Any time the signal **done** is asserted, we must wait for done to go low before proceeding.

Consider a vending machine controller


- 規格
 - Receives coins (nickel, dime, quarter) and accumulates sum 算錢
 - When “dispense” button is pressed serves a drink if enough coins have been deposited 給飲料
 - Then returns change – one nickel at a time. 找零
- 如何設計
 - 給定規格，先定義出資料流計算(datapath)部分和控制訊號(state diagram)兩部分
 - //given system specs, you need to define both operations (data path) and control signals (state diagram)
- Partition task
 - Datapath – keep track of amount owed user 算錢
 - Control – keep track of sequence – deposit, serve, change 動作流程

先處理 Datapath: data state


- Data state:
 - amount of money 目前投了多少錢 (in unit of nickels): *amount*
- 影響amount的運算
 - Reset: $\text{amount} = 0$;
 - Deposit a coin: $\text{amount} = \text{amount} + \text{value}$
 - Value = 1, 2, 5 for a nickel, dime, or quarter
 - Return one nickel of change: $\text{amount} = \text{amount} - 1$
 - Otherwise: no change

再處理control part: data 改變的時間點

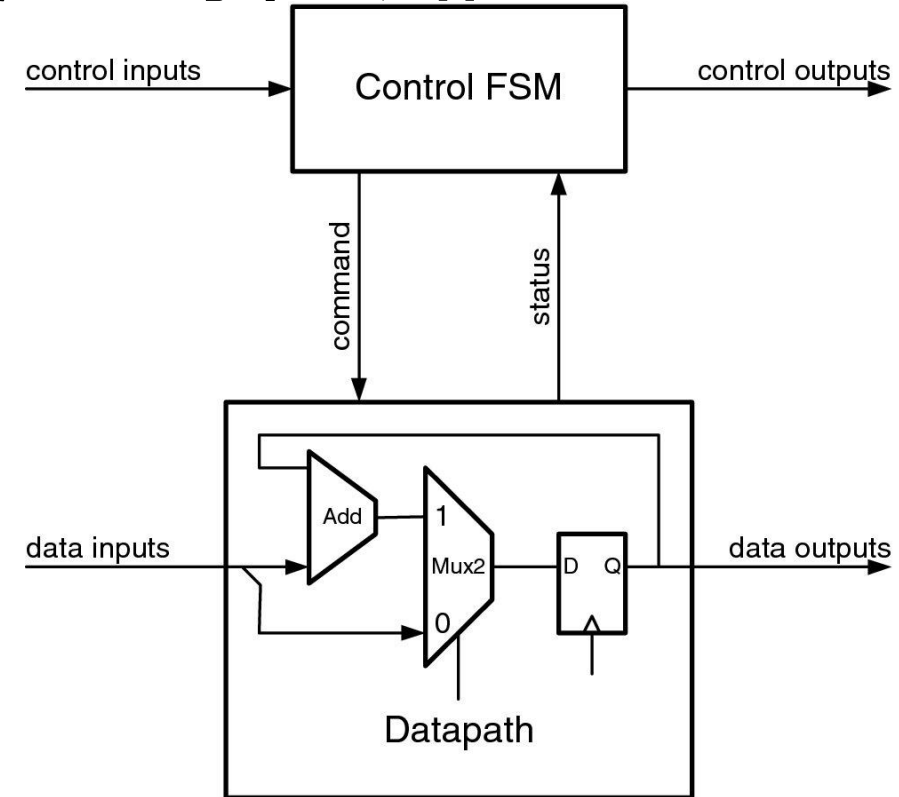- 先確定輸出入
- 輸入
 - 資料 : (nickel, dime, quarter), price
 - 動作: dispense, done
 - 系統: rst, clk
- 輸出
 - serve, change
- 內部Status/command signal
 - Status: enough, zero
 - Command: 決定state時一起看



再處理control part :State diagram

 

- In this diagram, edges from a state to itself are omitted. If the conditions on all edges leading out of the current state are not satisfied, the FSM stays in that state.

```
module VendingMachine(clk, rst, nickel, dime, quarter, dispense, done, price,
    serve, change) ;
```

```
parameter n = `DWIDTH ;
```

```
input clk, rst, nickel, dime, quarter, dispense, done ;
```

```
input [n-1:0] price ;
```

```
output serve, change ;
```

```
wire serve, change;
```

```
//internal signals
```

```
wire enough, zero;
```

```
//variable declaration
```

```
logic [2:0] value;
```

```
logic [n-1:0] amount;
```

```
assign value = nickel ? 1 : (dime ? 2 : 5));
```

```
assign zero = amount == 0;
```

```
assign enough = amount >= price;
```

```
always_ff @(posedge clk or posedge rst)
```

```
    if(rst) amount <= 0;
```

```
    else amount <= amount_nxt;
```

- Data state:
 - amount of money 目前投了多少錢 (in unit of nickels): *amount*
- 影響amount的運算
 - Reset: amount = 0;
 - Deposit a coin: amount = amount + value
 - Value = 1, 2, 5 for a nickel, dime, or quarter
 - Return one nickel of change: amount = amount - 1
 - Otherwise: no change

```
//state machine
```

```
parameter [2:0] DEPOSIT = 0,  
                SERVE1  = 1,  
                SERVE2  = 2,  
                CHANG1  = 3,  
                CHANG2  = 4;
```

```
reg [2:0] state, state_nxt;
```

```
always_ff @(posedge clk or posedge rst)  
    if(rst == 1) state <= DEPOSIT;  
    else state <= state_nxt;
```

```
always_comb begin
```

```
    amount_nxt = amount;
```

```
    state_nxt = DEPOSIT;
```

```
    serve = 0;
```

```
    change = 0;
```

```
case(state)
```

```
    DEPOSIT: begin
```

```
        if(dispense & enough) state_nxt = SERVE1;
```

```
        else state_nxt = DEPOSIT;
```

```
        amount_nxt = amount + value;
```

```
        if(dispense & enough) serve = 1; //when from DEPOSIT to SERVE1
```

```
    end
```


```
    SERVE1: begin
```

```
        if(done) state_nxt = SERVE2;
```

```
        else state_nxt = SERVE1;
```

```
        amount_nxt = amount - price;
```

```
    end
```

 

SERVE2: **begin**

```

if(~done & zero)      state_nxt = DEPOSIT;
else if(~done & ~zero) state_nxt = CHANG1;
else                  state_nxt = SERVE2;

```

```

if(~done & ~zero) change = 1; //when from SERVE2 to CHANG1

```

end

CHANG1: **begin**

```

if(done) state_nxt = CHANG2;
else     state_nxt = CHANG1;

```

```

amount_nxt = amount - 1;

```

end

CHANG2: **begin**

```

if(~done & ~zero)  state_nxt = CHANG1;
else if(~done & zero) state_nxt = DEPOSIT;
else              state_nxt = CHANG2;


```

end


endcase

end

endmodule

 

Block diagram of data path

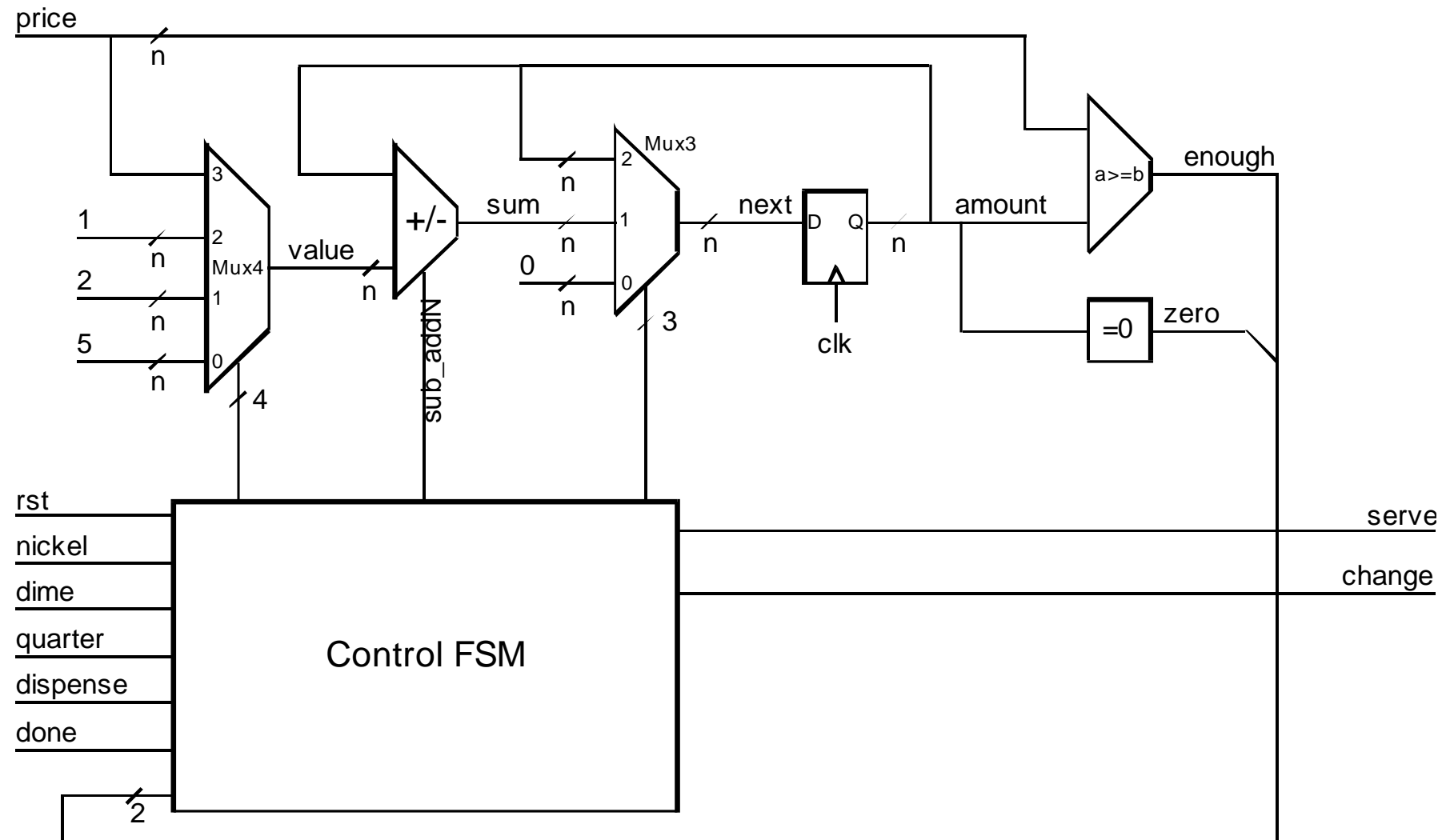

```
//-----
// VendingMachine - Top level module
// Just hooks together control and datapath
//-----
module VendingMachine(clk, rst, nickel, dime, quarter, dispense, done, price,
                     serve, change) ;
    parameter n = `DWIDTH ;
    input clk, rst, nickel, dime, quarter, dispense, done ;
    input [n-1:0] price ;
    output serve, change ;

    wire enough, zero, sub ;
    wire [3:0] selval ;
    wire [2:0] selnext ;

    //define control generator
    VendingMachineControl vmc(clk, rst, nickel, dime, quarter, dispense, done,
                             enough, zero, serve, change, selval, selnext, sub) ;

    //define data path
    VendingMachineData #(n) vmd(clk, selval, selnext, sub, price, enough, zero) ;
endmodule
```

Another coding style: in two modules

```
//-----
module VendingMachineControl(clk, rst, nickel, dime, quarter, dispense,
done,
    enough, zero, serve, change, selval, selnext, sub) ;
input clk, rst, nickel, dime, quarter, dispense, done, enough, zero ;
output serve, change, sub ;
output [3:0] selval ;
output [2:0] selnext ;
wire [`SWIDTH-1:0] state, next ; // current and next state
reg [`SWIDTH-1:0] next1 ; // next state w/o reset

// outputs
wire first ; // true during first cycle of serve1 or changel
wire serve1 = (state == `SERVE1) ;
wire changel = (state == `CHANGE1) ;
wire serve = serve1 & first ;
wire change = changel & first ;

// datapath controls
wire dep = (state == `DEPOSIT) ;
// price, 1, 2, 5
wire [3:0] selval = {(dep & dispense),
                    ((dep & nickel) | change),
                    (dep & dime),
                    (dep & quarter)} ;

// amount, sum, 0
wire selv = (dep & (nickel | dime | quarter |
                    (dispense & enough))) |
            (change) ;
wire [2:0] selnext = {(selv | rst),selv,rst} ;

// subtract
wire sub = (dep & dispense) | change ;

// only do actions on first cycle of serve1 or changel
wire nfirst = !(serve1 | changel) ;
DFF #(1) first_reg(clk, nfirst, first) ;

// state register
DFF #(`SWIDTH) state_reg(clk, next, state) ;

// next state logic
always @(state or zero or dispense or done or enough) begin
    casex({dispense, enough, done, zero, state})
        {4'b11xx,`DEPOSIT}: next1 = `SERVE1 ; // dispense & enough
        {4'b0xxx,`DEPOSIT}: next1 = `DEPOSIT ;
        {4'b0xx,`DEPOSIT}: next1 = `DEPOSIT ;
        {4'bxx1x,`SERVE1}: next1 = `SERVE2 ; // done
        {4'bxx0x,`SERVE1}: next1 = `SERVE1 ;
        {4'bxx01,`SERVE2}: next1 = `DEPOSIT ; // ~done & zero
        {4'bxx00,`SERVE2}: next1 = `CHANGE1 ; // ~done & ~zero
        {4'bxx1x,`SERVE2}: next1 = `SERVE2 ; // done
        {4'bxx1x,`CHANGE1}: next1 = `CHANGE2 ; // done
        {4'bxx0x,`CHANGE1}: next1 = `CHANGE1 ; // ~done
        {4'bxx00,`CHANGE2}: next1 = `CHANGE1 ; // ~done & ~zero
        {4'bxx01,`CHANGE2}: next1 = `DEPOSIT ; // ~done & zero
        {4'bxx1x,`CHANGE2}: next1 = `CHANGE2 ; // done
    endcase
end

// reset next state
assign next = rst ? `DEPOSIT : next1 ;
endmodule
```



```

module VendingMachineData(clk, selval, selnext, sub, price, enough, zero) ;
    parameter n = 6 ;
    input clk, sub ;
    input [3:0] selval ; // price, 1, 2, 5
    input [2:0] selnext ; // amount, sum, 0
    input [n-1:0] price ; // price of soft drink - in nickels
    output enough ; // amount > price
    output zero ; // amount = zero

    wire [n-1:0] sum ; // output of add/subtract unit
    wire [n-1:0] amount ; // current amount
    wire [n-1:0] next ; // next amount
    wire [n-1:0] value ; // value to add or subtract from amount
    wire ovf ; // overflow - ignore for now

    // state register holds current amount
    DFF #(n) amt(clk, next, amount) ;

    // select next state from 0, sum, or hold
    Mux3 #(n) nsmux({n{1'b0}}, sum, amount, selnext, next) ;


    // add or subtract a value from current amount
    AddSub #(n) add(amount, value, sub, sum, ovf) ;

    // select the value to add or subtract
    Mux4 #(n) vmux(`QUARTER, `DIME, `NICKEL, price, selval, value) ;

    // comparators
    wire enough = (amount >= price) ;
    wire zero = (amount == 0) ;
endmodule

```

Waveforms for vending machine

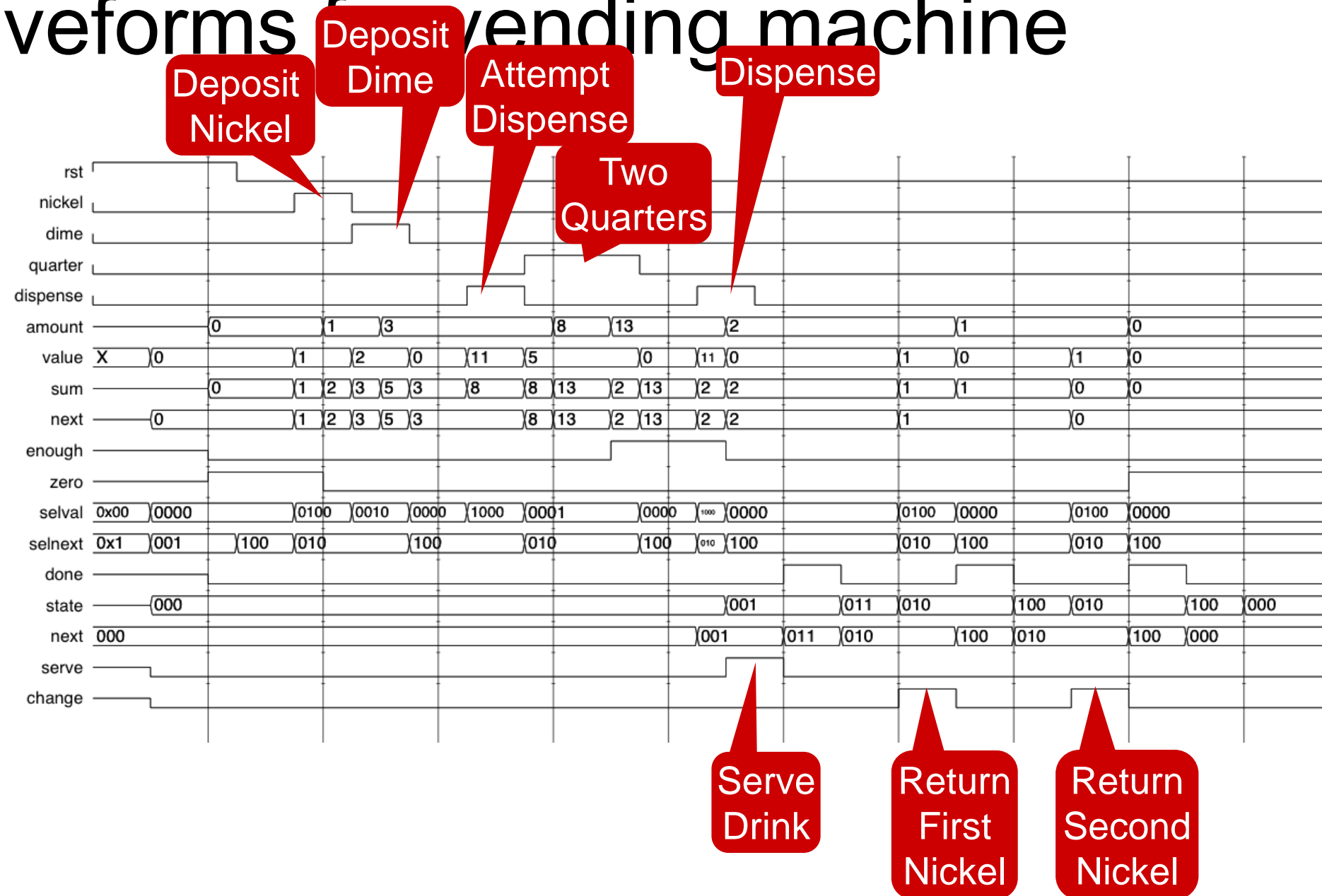

Summary

- Datapath state machines
 - Next state function specified by an expression, not a table
 - $\text{next} = \text{rst} ? 0 : (\text{inc} ? \text{next} + 1 : \text{next}) ;$
 - Common “idioms”
 - Counters
 - Shift registers
- Datapath and control partitioning
 - Divide state space into control (deposit, serve, change) and data
 - FSM determines control state
 - Datapath computes amount
 - Status and control signals
 - Special case of factoring
- Lead to an arithmetic and logic unit (ALU) in processor designs